

# *Designing Microphone Preamplifiers*

By Gary K. Hebert  
129<sup>th</sup> AES Convention  
San Francisco CA, November 2010


**THAT** Corporation

# The Tutorial Overview

## ***Section 1*** ***Support Circuitry***

## ***Section 2*** ***The Amplifier***

# Simple Block Diagram

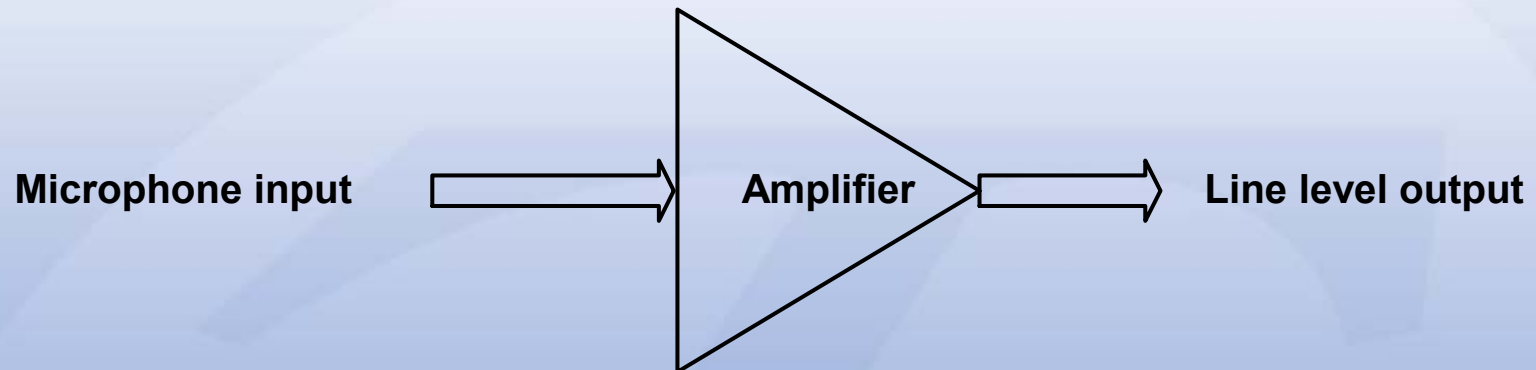

**Microphone signal levels vary widely due to:**

- Microphone sensitivity
- Source SPL
- Proximity to source

**Line level outputs are somewhat more constrained:**

- “Standard” maximum operating levels include 24, 18, 15 dBu
- A/D converter input levels are approximately 8 dBu or 2 Vrms differential

# Typical Requirements

## Gain

- Up to 40 dB covers the majority of close-mic'd applications
- Some situations require more than 70 dB
- Variability of input levels requires adjustable gain over a very wide range

## Phantom Power

- Required for many microphones
- Standardized in IEC EN 61938  
48 Volts +/- 4V at up to 10 mA per microphone
- On / off control

## Input Pad

- Can allow higher input signal levels, at the expense of noise
- May be required depending on minimum gain and supply rails
- 20 dB is common

## Resistant to common mode noise and RFI

## Reliable

# Preamplifier Technologies

## Transformer-Coupled Vacuum Tube

- Robust
- Colorful
- Costly

## Transformer-Coupled Solid State


- Also Robust
- Performance can be excellent
- Cost can be high

## Transformerless Solid State

- More vulnerable
- Performance can be excellent
- Cost ranges from very low to high


**Transformerless solid state designs are the focus today**

# Amplifier Input Bias Current

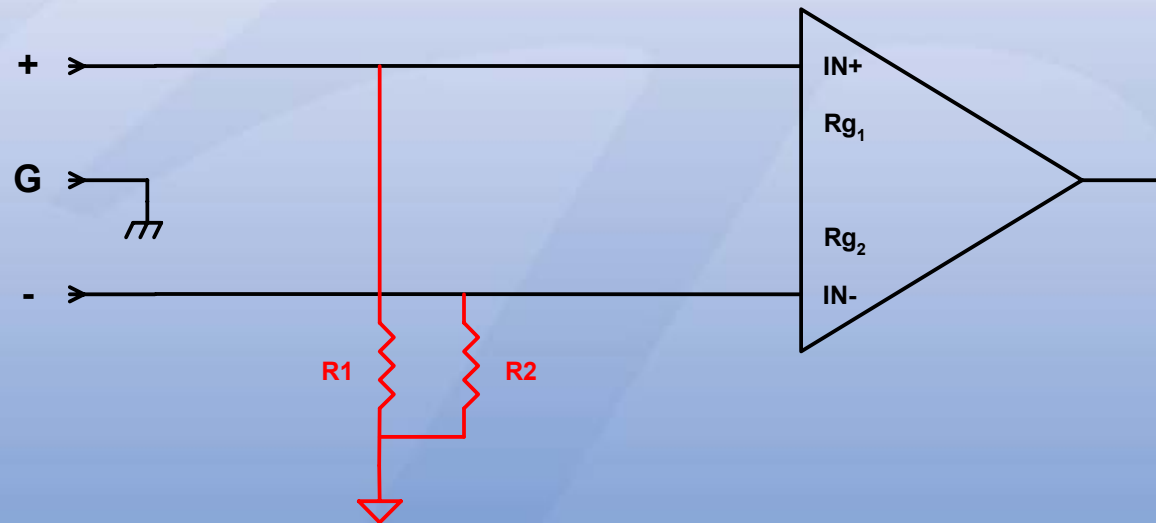

**Must provide a DC current path to supply the amplifier input bias current**

# Gain Control

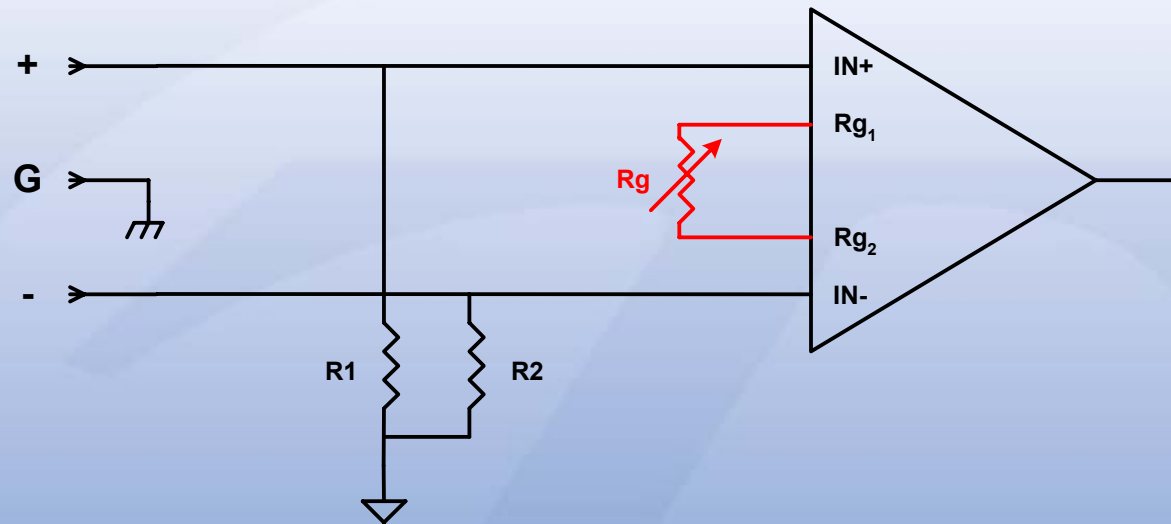

The amplifier is often designed to vary gain using a single variable resistor ( $R_g$ )


## Manually controlled options

- Potentiometer with continuous control over a defined range
- Switched resistor network with a fixed number of steps and gain settings

## Digitally controlled options

- Digitally switched resistor network with a predetermined number of steps
- Switches are either relays or silicon devices
- Both discrete and integrated circuit solutions are available


# Phantom Power

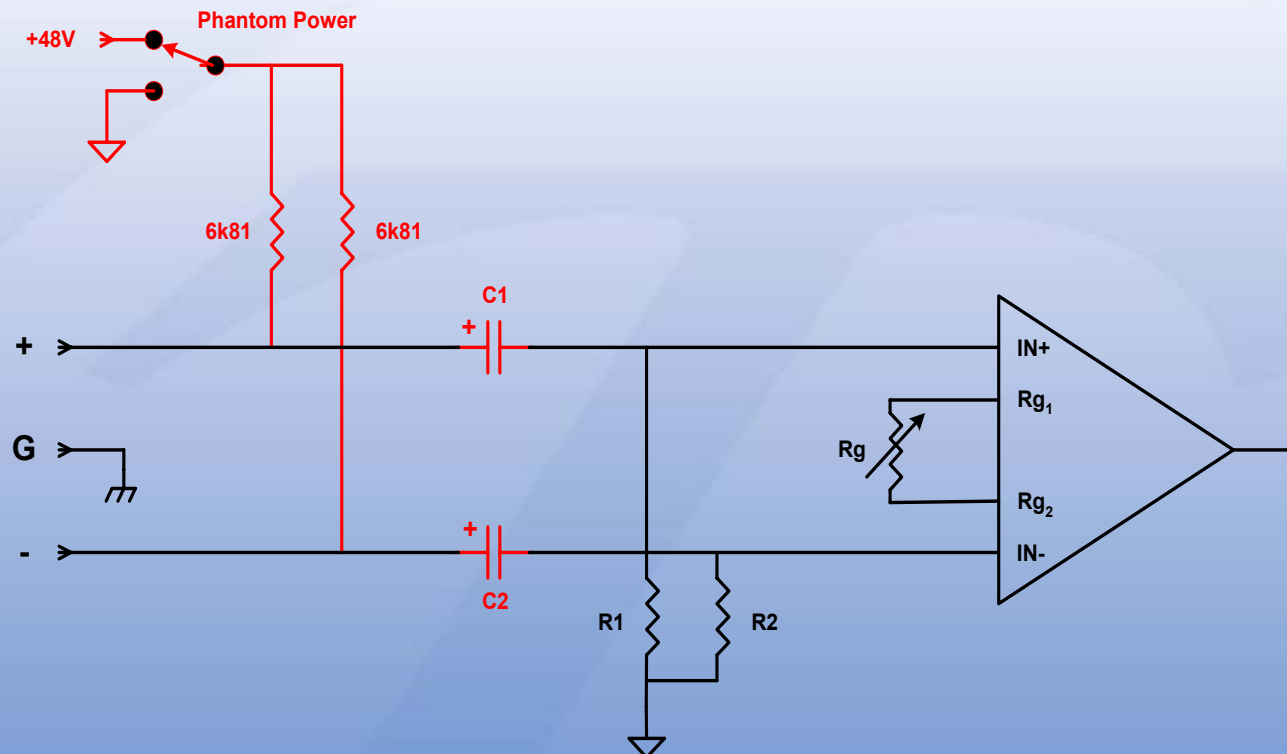

- C1 and C2 required to block the 48 V from the amplifier inputs
- 6.81k series resistors are specified in the standards for 48V phantom power
- On/Off is available via a
  - Simple mechanical switch in manual applications
  - Relay or silicon switch in digitally controlled systems




# Input Pad

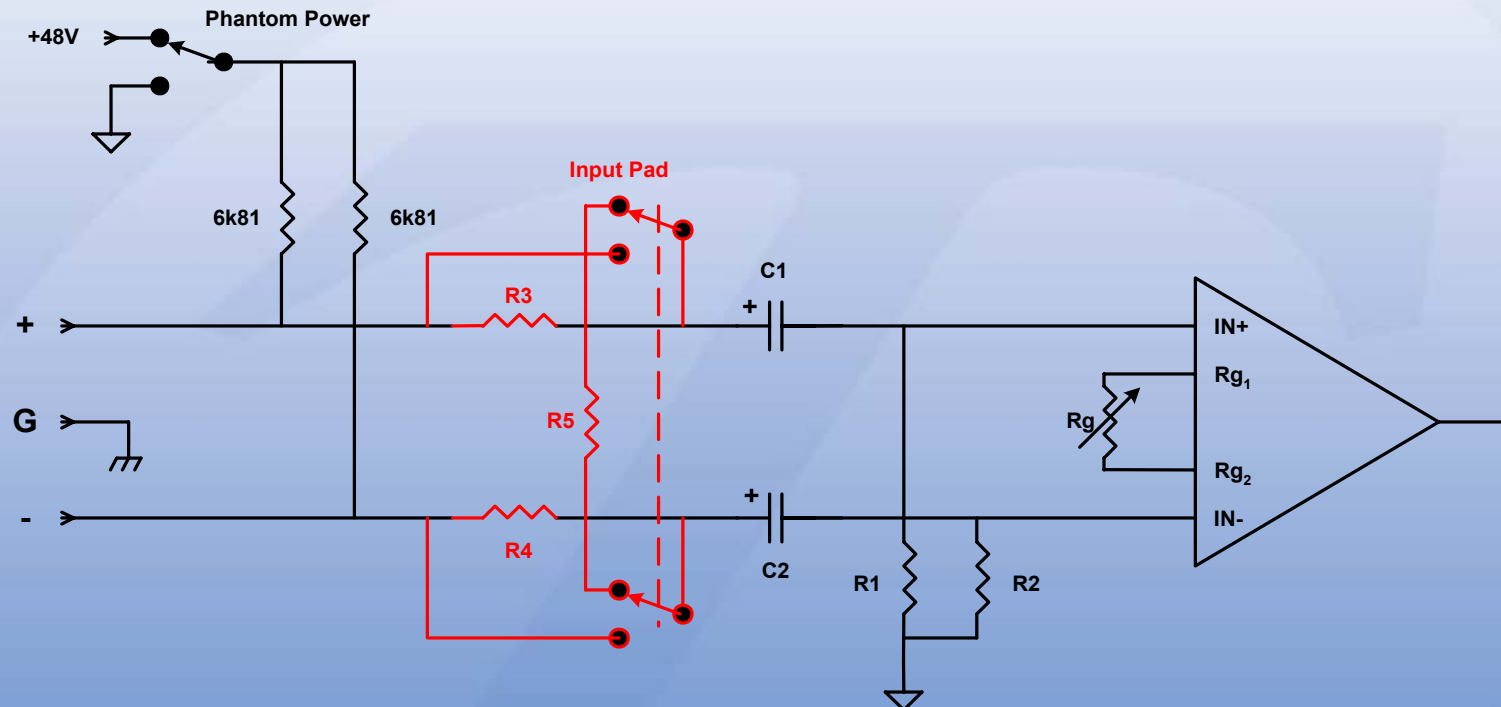

- Input pad is simply a signal attenuator prior to the amplifier
- This is a differential-only pad, it does not attenuate common-mode signals


# "Complete" Microphone Preamp

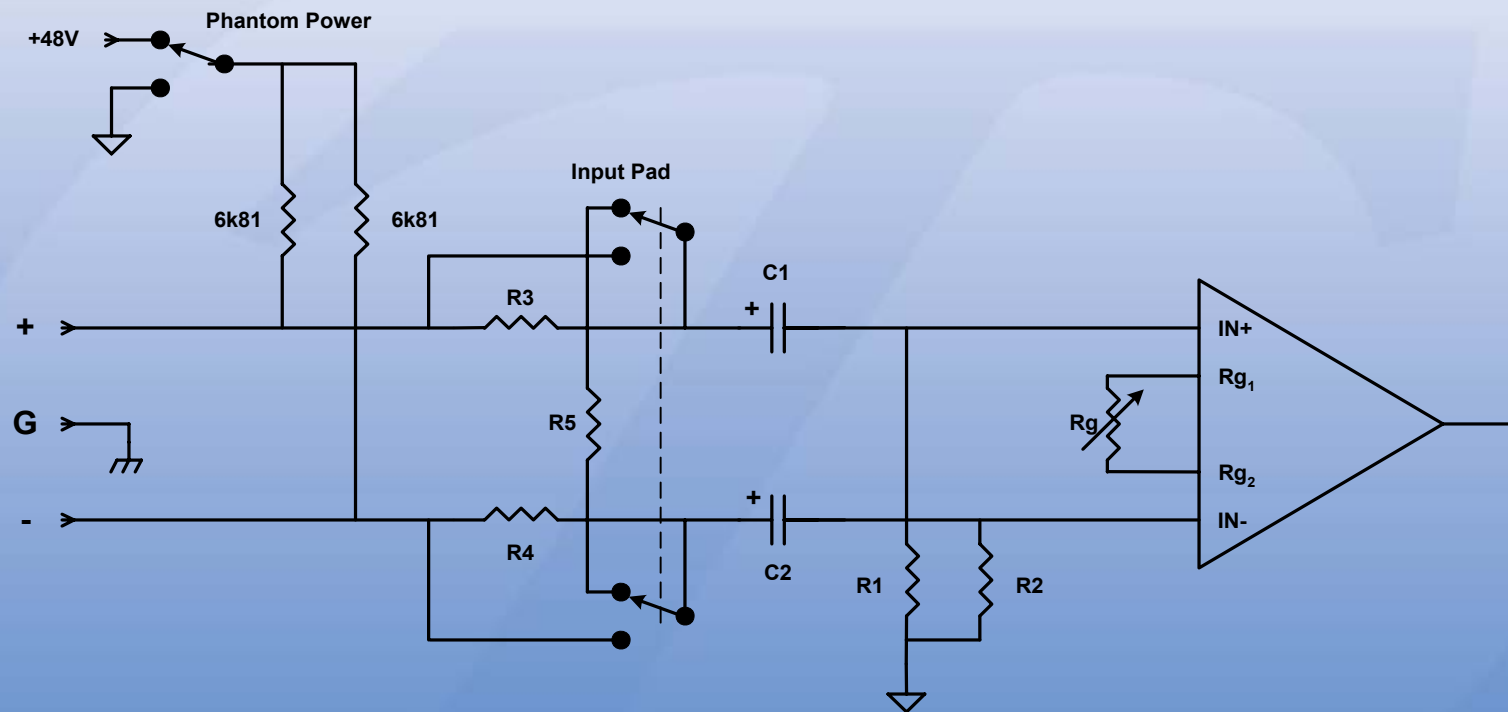

*It would be nice to say “that’s all there is”  
but.....*


*there are gremlins in the details!!*

# DC Offset Changes

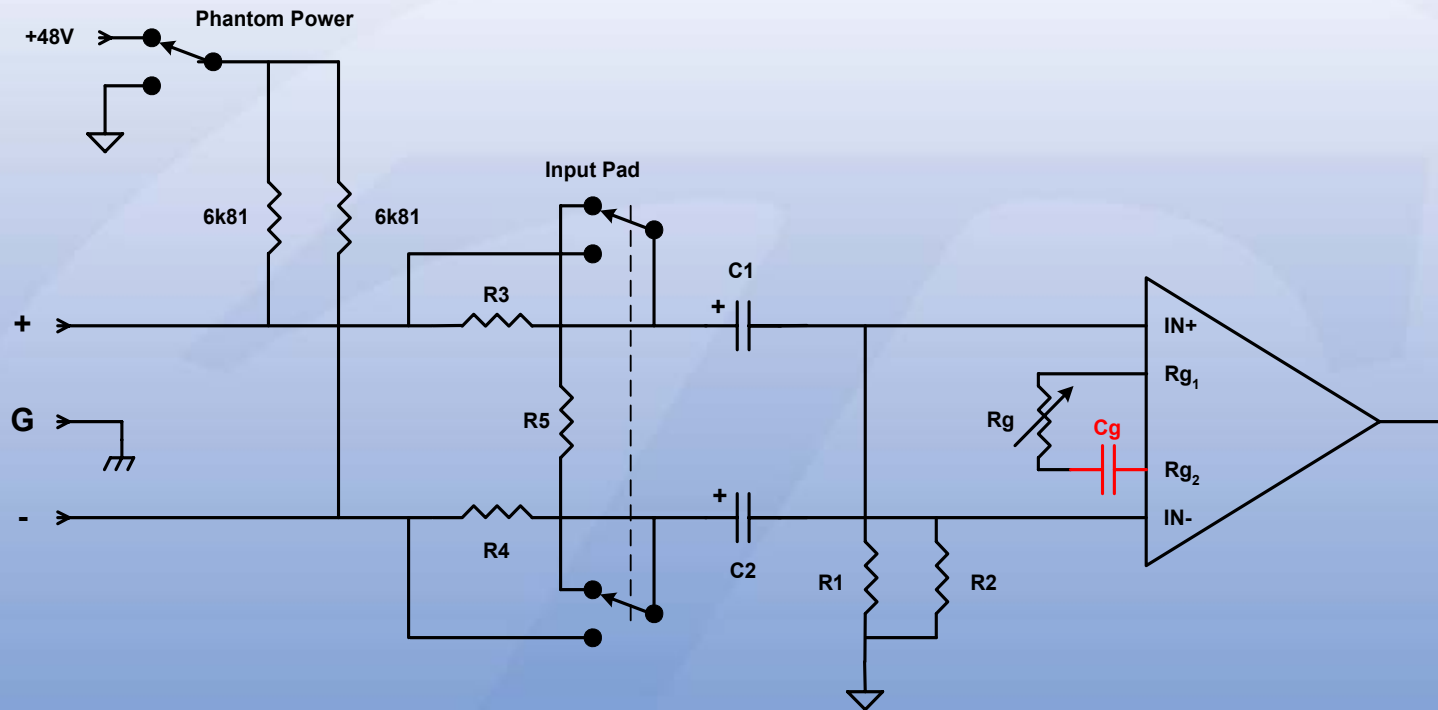


- Changes in gain can result in the DC offset changes at the output of the amplifier
- 2 solutions are available
  - Adding a capacitor (Cg) sets the DC gain to a fixed value and avoids these offset changes
  - A servo-amplifier can also be effective, but we don't have time to discuss them today

# Trade-offs with $C_g$

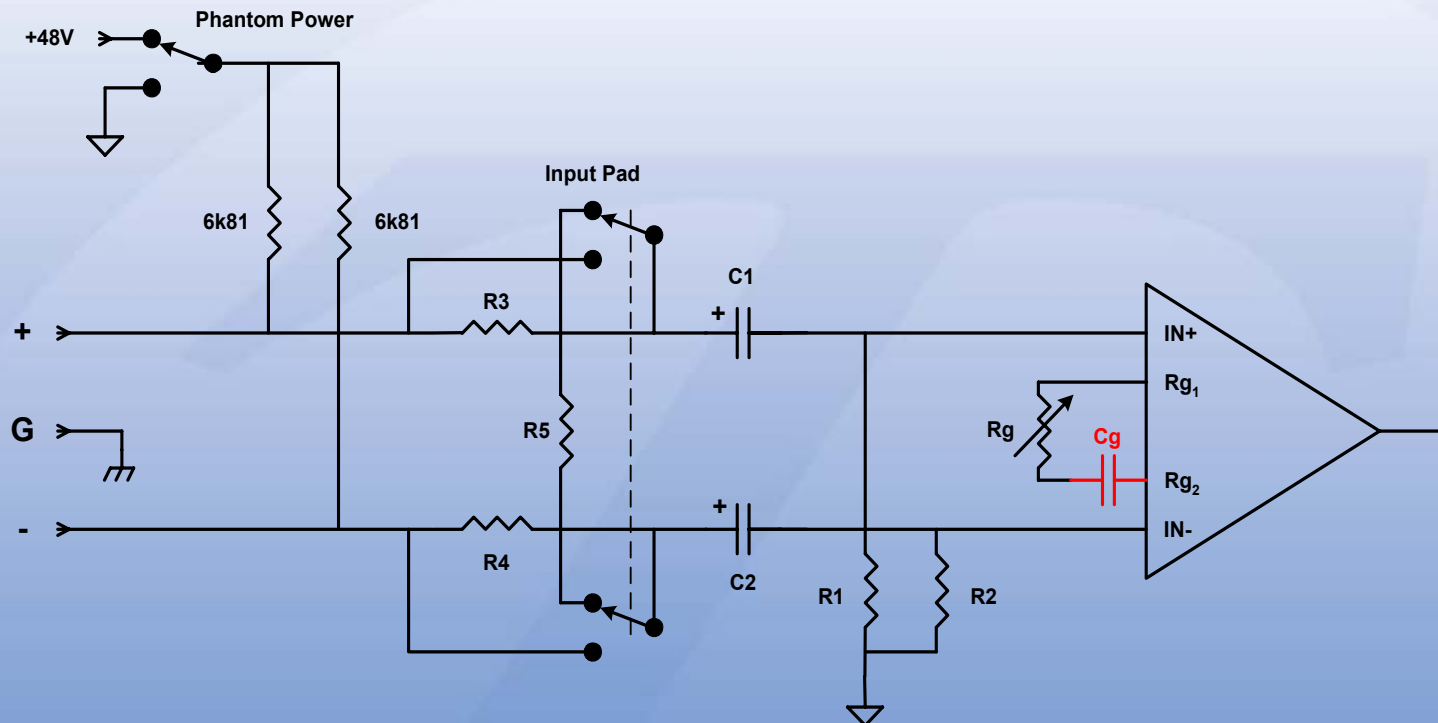


- $R_g$  and  $C_g$  create a high-pass filter in the signal path
- $R_g$  can vary from  $<5$  to  $>10k$  ohms
- $C_g$  must have a very large capacitance to avoid low frequency audio attenuation
  - Worst at highest gain

# Resistor Value Selection

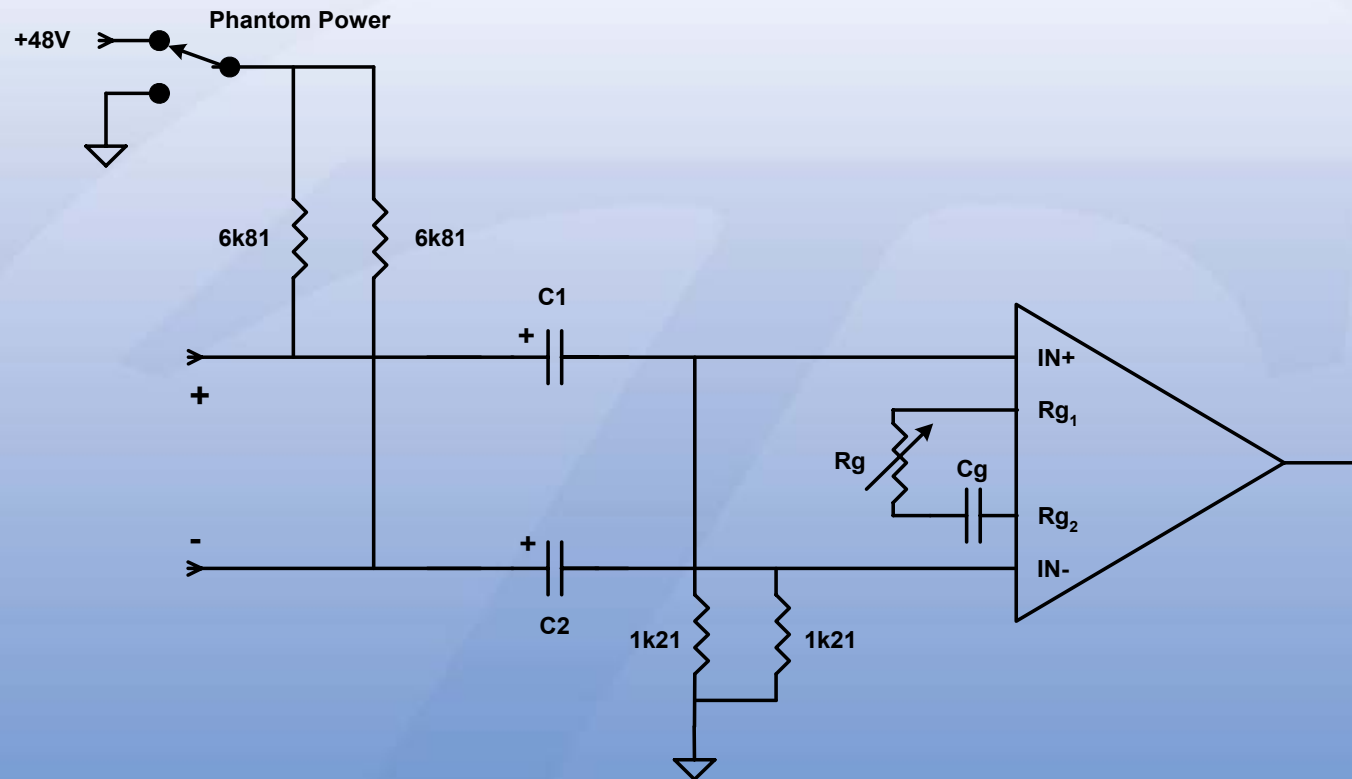


- Microphone are commonly specified for 2 to 3 kohm loads
- Differential input impedance is  $(R1 \parallel 6.81k) + (R2 \parallel 6.81k)$
- Therefore, suitable values for R1 & R2 are between 1172 and 1924 ohms

# Capacitor Value Selection

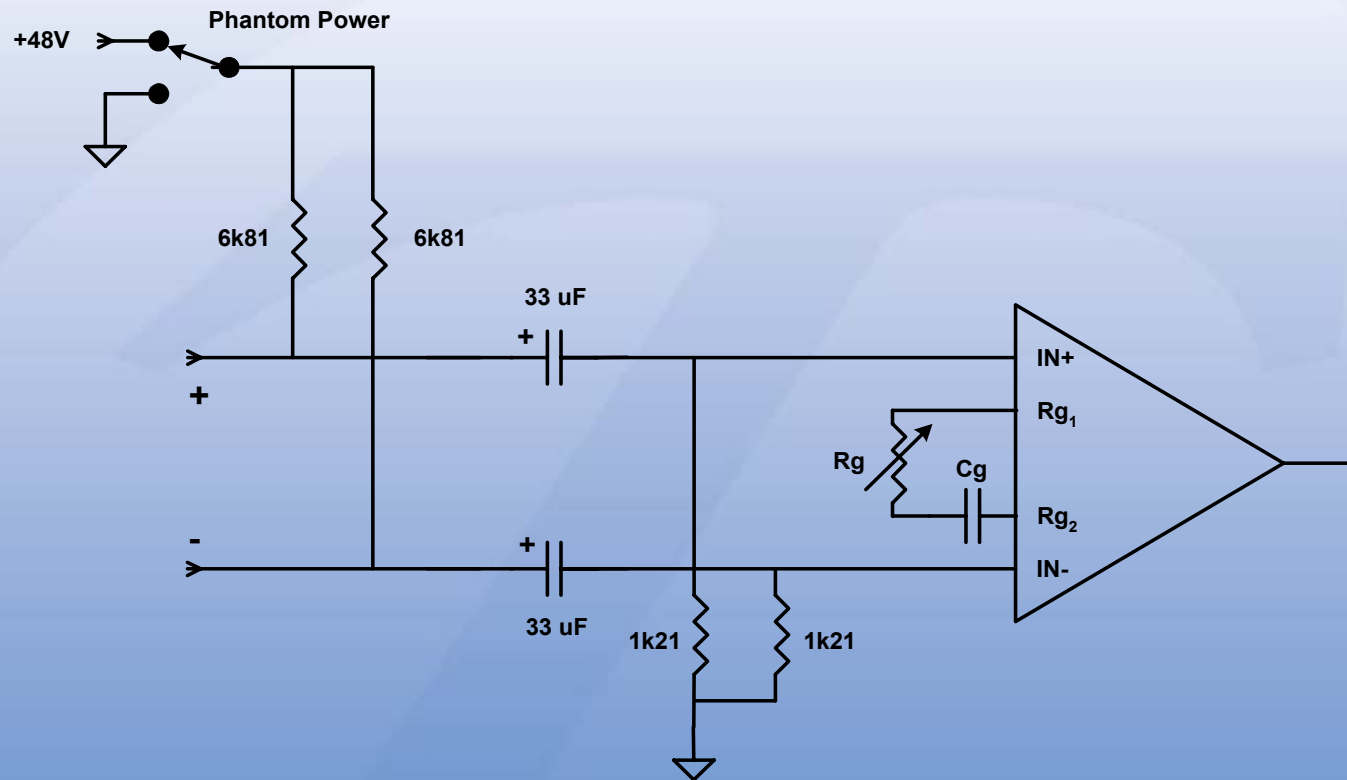

- High-pass filter corner frequency is set by the blocking capacitor and bias resistor and is equal to  $1 / (2 \times \pi \times R \times C)$
- For a 5 Hz corner frequency, the minimum values for C1 & C2 are 26 uF
- The next largest standard value is 33 uF
- Results in a nominal corner frequency of about 4 Hz

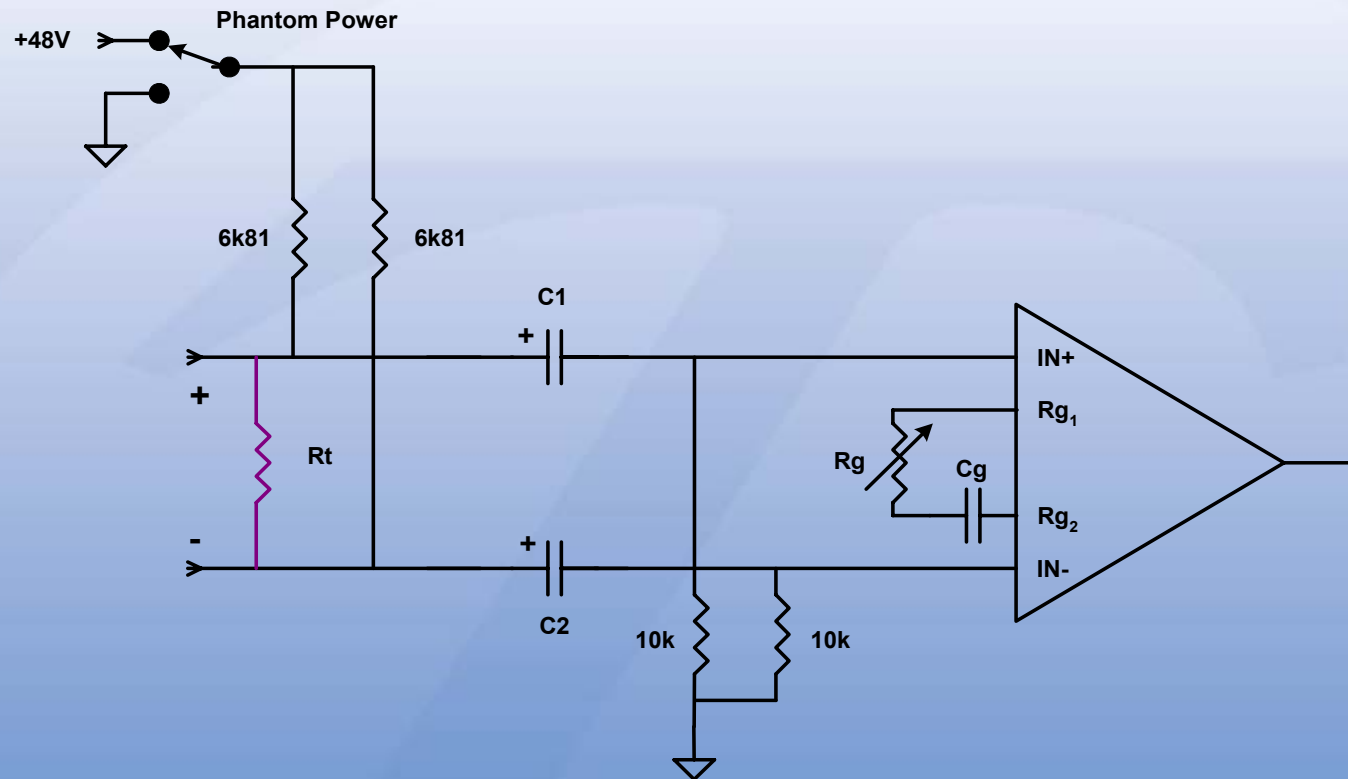
# Alternative Resistor-Capacitor Value Selection



- $C_1$  and  $C_2$  can be made smaller if bias resistors are made larger
- $R_{in}$  is defined by  $R_t$
- However,  $C_1$  and  $C_2$  convert  $1/f$  noise to  $1/f^2$  noise
- 10k resistors contribute thermal noise and current noise  $\ast R$




# Common Mode Rejection (CMRR)

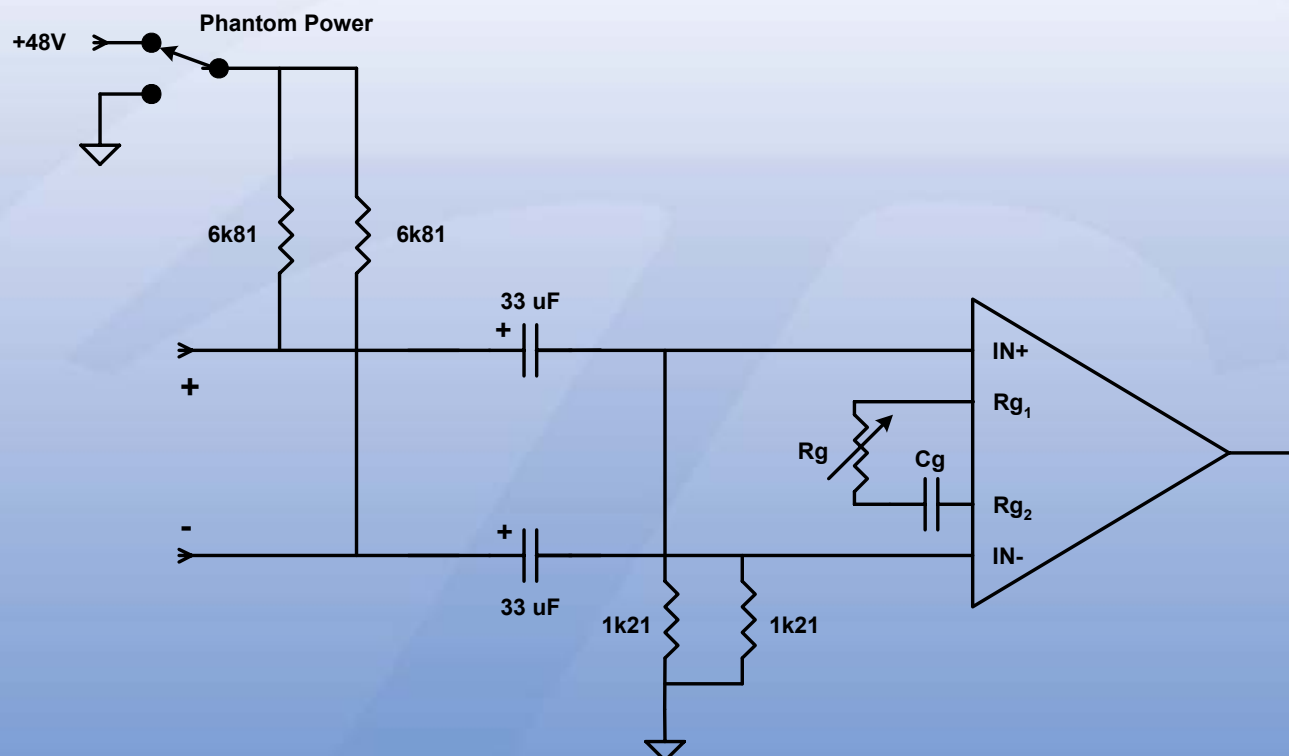


- Common-mode to differential conversion results from mismatches in:
  - 6.81 k resistors
  - 1.21 k resistors
- Low frequency CMRR affected by capacitor mismatch

# U-Pad Attenuator

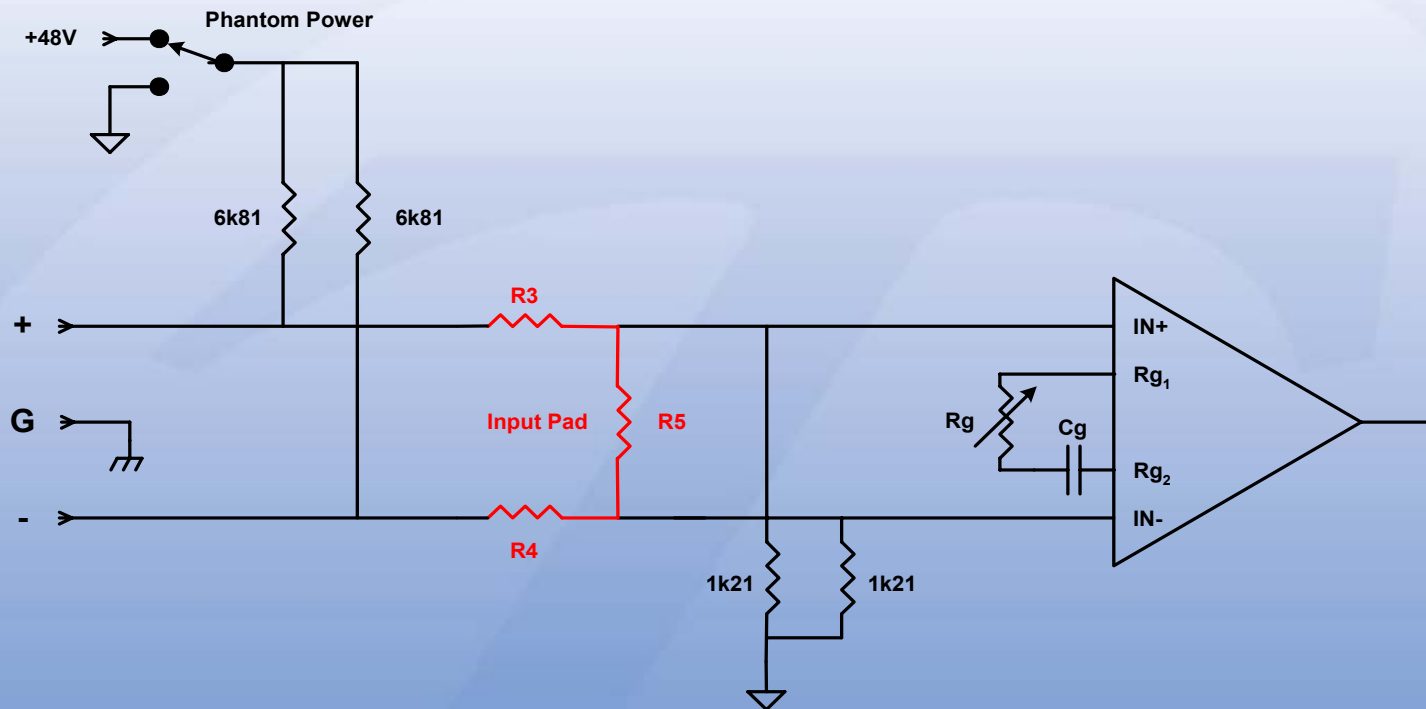


- $Z_{IN}$  with and without pad can be closely matched
- Can be designed for any attenuation
  - 20dB is typical
- Noise performance is degraded
- Better noise, less headroom with less attenuation

## Example -20 dB Input Pad

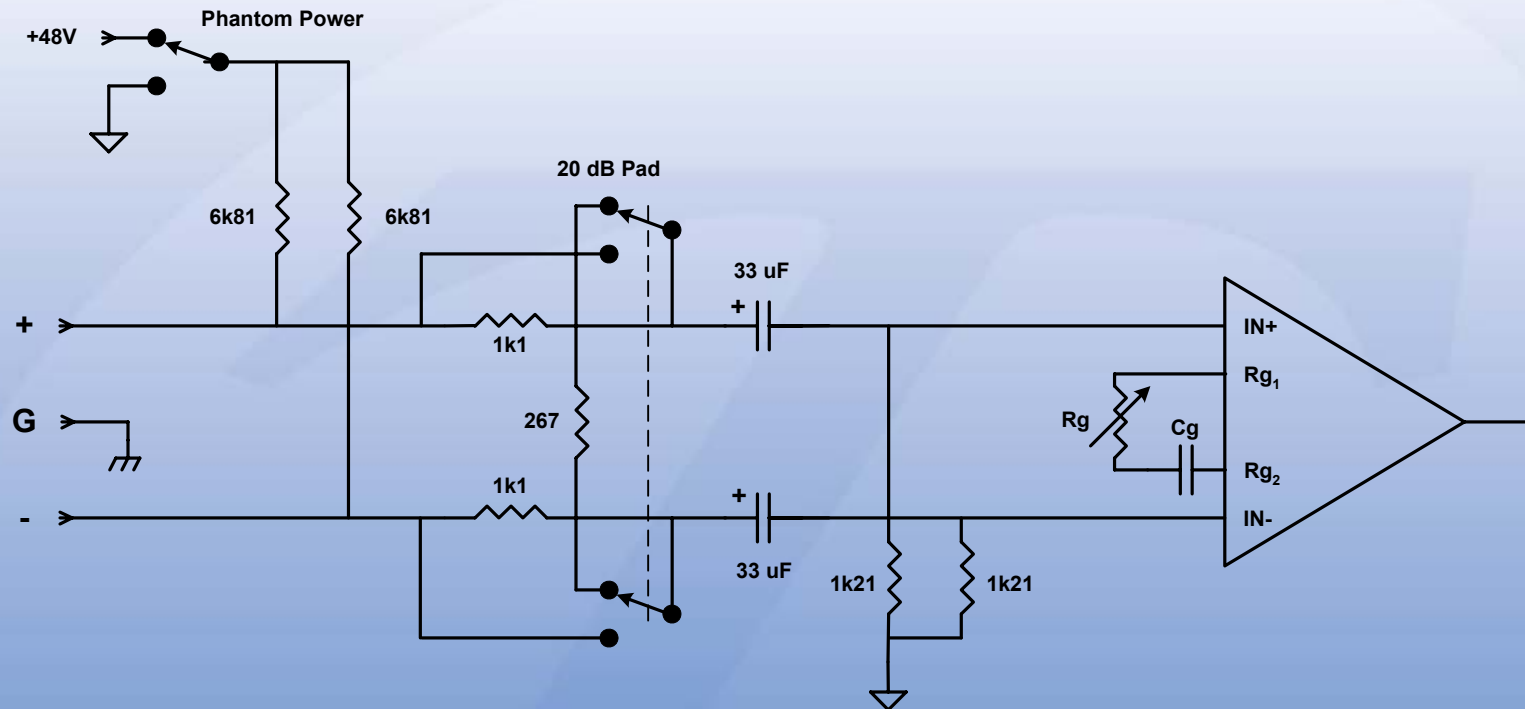

- $Z_{IN}$  with and without pad is approximately 2k
- 20 dB Attenuation
- Pad output impedance is approximately 240 ohms
- See THAT Design Note DN-140 for details and alternatives

# RFI Protection

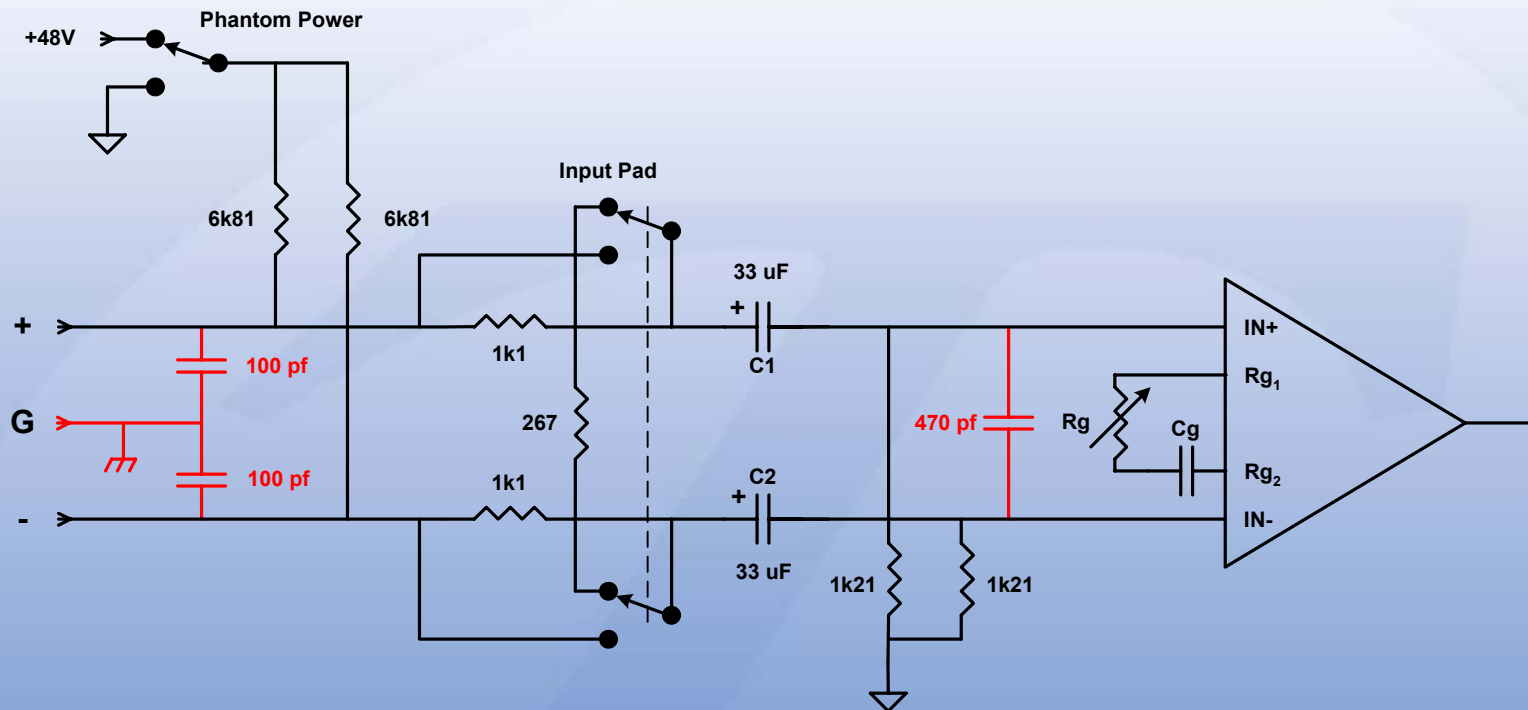

**RFI protection is required in any practical design**


**100 pf caps at the input connector attenuate differential and common-mode RFI**

**470 pf cap at amplifier input pins reduces differential high frequencies from both internal and external sources**

# Phantom Power Faults


- **Shorting input pins to ground with phantom turned on**
  - 33uF coupling caps C1 & C2 start charged to 48V
  - Positive end of C1, C2 connect to ground
  - Negative end of C1, C2 driven to -48V!
- **The shorting sequence can vary**
  - “Single-ended”: One input to ground
  - “Common-mode”: both inputs to ground simultaneously
  - “Differential”: One input to ground, then the other
  - Differential is worst
- **Big currents flow as C1, C2 discharge**
  - Currents over 3 *amperes* flow in the capacitors

# Phantom Fault Protection

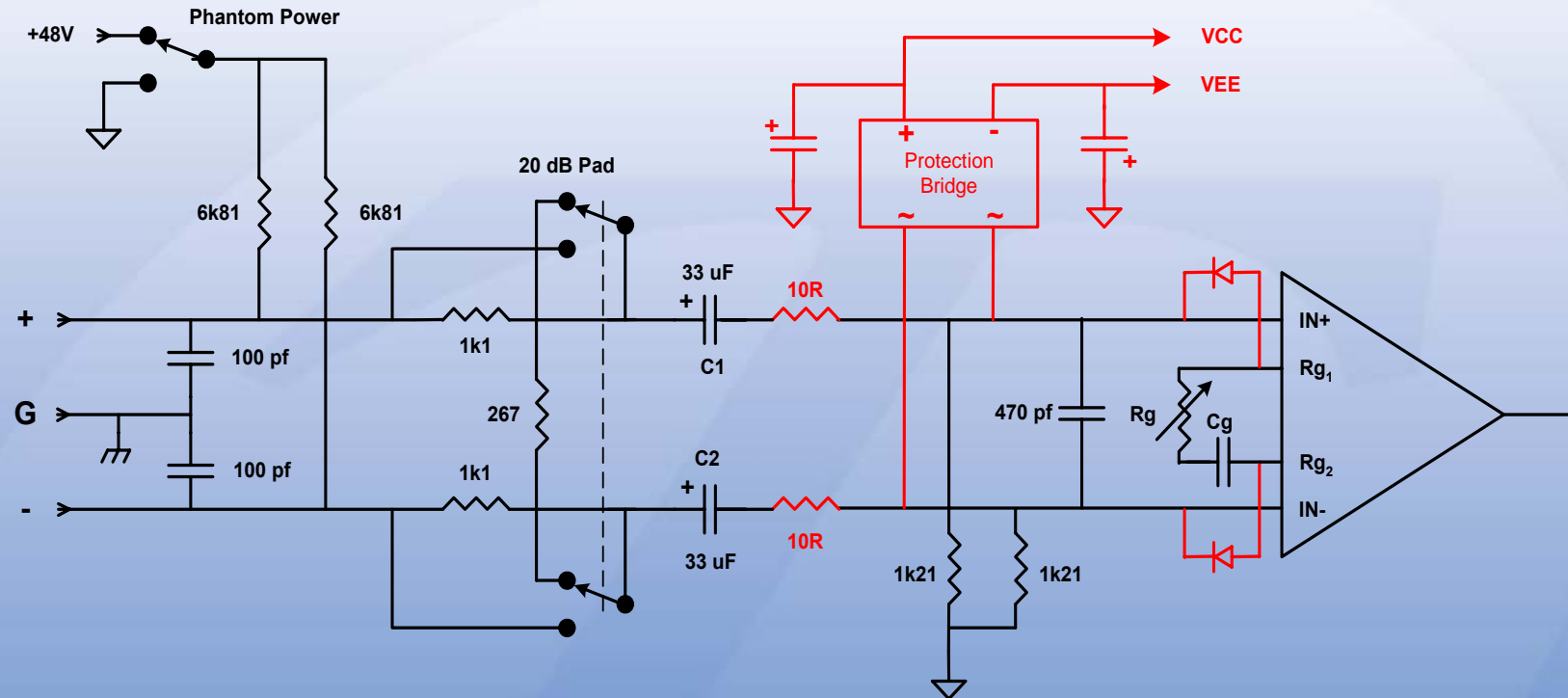

- Limit the current with small value resistors
- Direct fault currents away from the amplifier inputs
  - Input diodes provide a conduction path which bypasses the amplifier
  - This current varies with gain setting
- Diode bridge directs fault current to rails
  - Consider impact on supply rails
  - Minimize supply transient with capacitance

# Complete Microphone Preamp

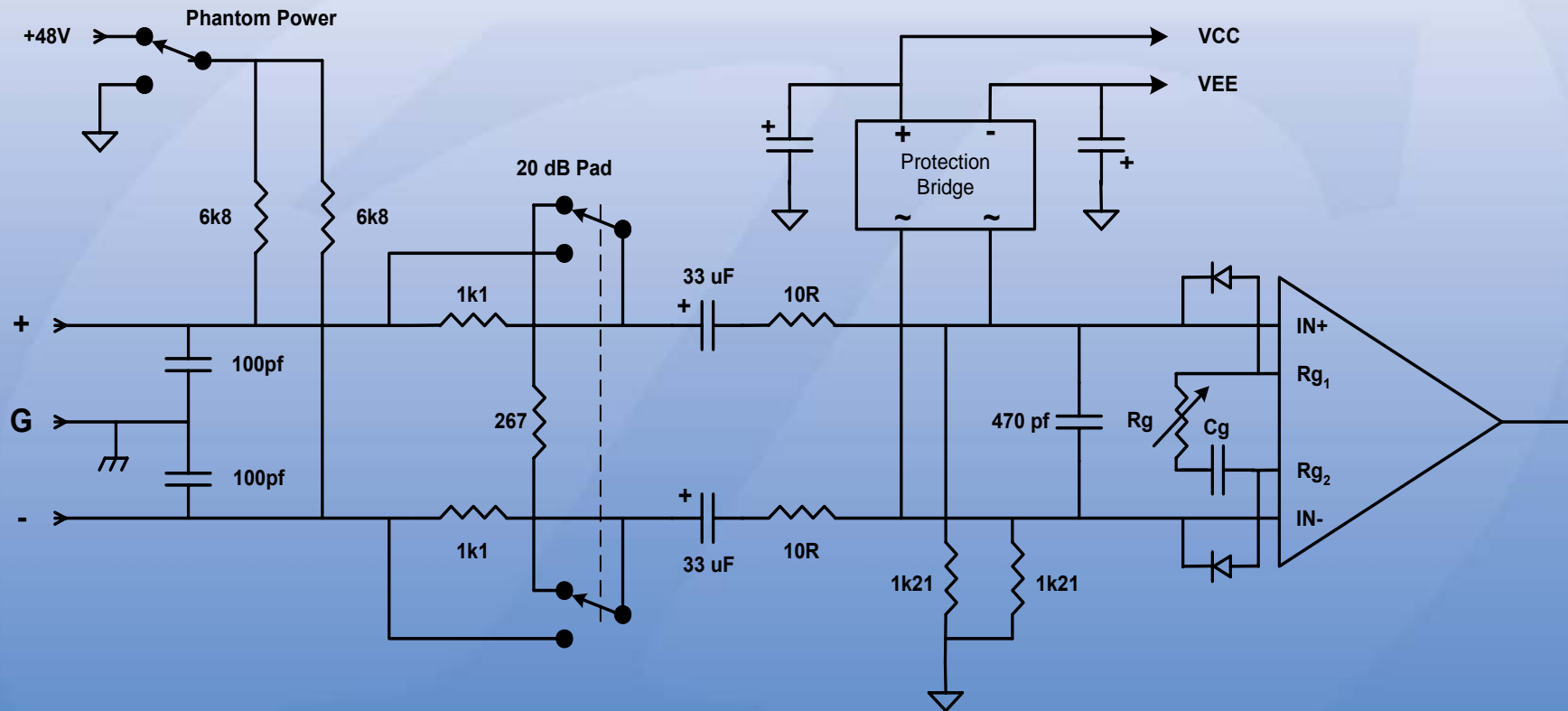

# References and Additional Information

- THAT Corp *“THAT 1510/1512”* data sheet
- THAT Corp *“THAT 1570 & 5171”* data sheets,
- THAT Corp *“Design Note 140”*
- THAT Corp *“Design Note 138”*
- THAT Corp *“Analog Secrets Your Mother Never Told You”*
- THAT Corp *“More Analog Secrets Your Mother Never Told You”*
- *“The 48 Volt Phantom Menace Returns”* Audio Engineering Society Preprint from the 127<sup>th</sup> AES Convention, Oct 2009
- *“The 48 Volt Phantom Menace”* Audio Engineering Society Preprint from the 110<sup>th</sup> AES Convention, May 2001

**All THAT Corp references are available at [thatcorp.com](http://thatcorp.com)**




# ***Amplifier Topologies***

***What's inside the triangle?***


# Scope

- We will concentrate on topologies that allow a wide range of gain with a single control.
- The goal is to balance the requirements for low distortion and low noise at both ends of the gain range.

# Simple Mic Preamp Schematic

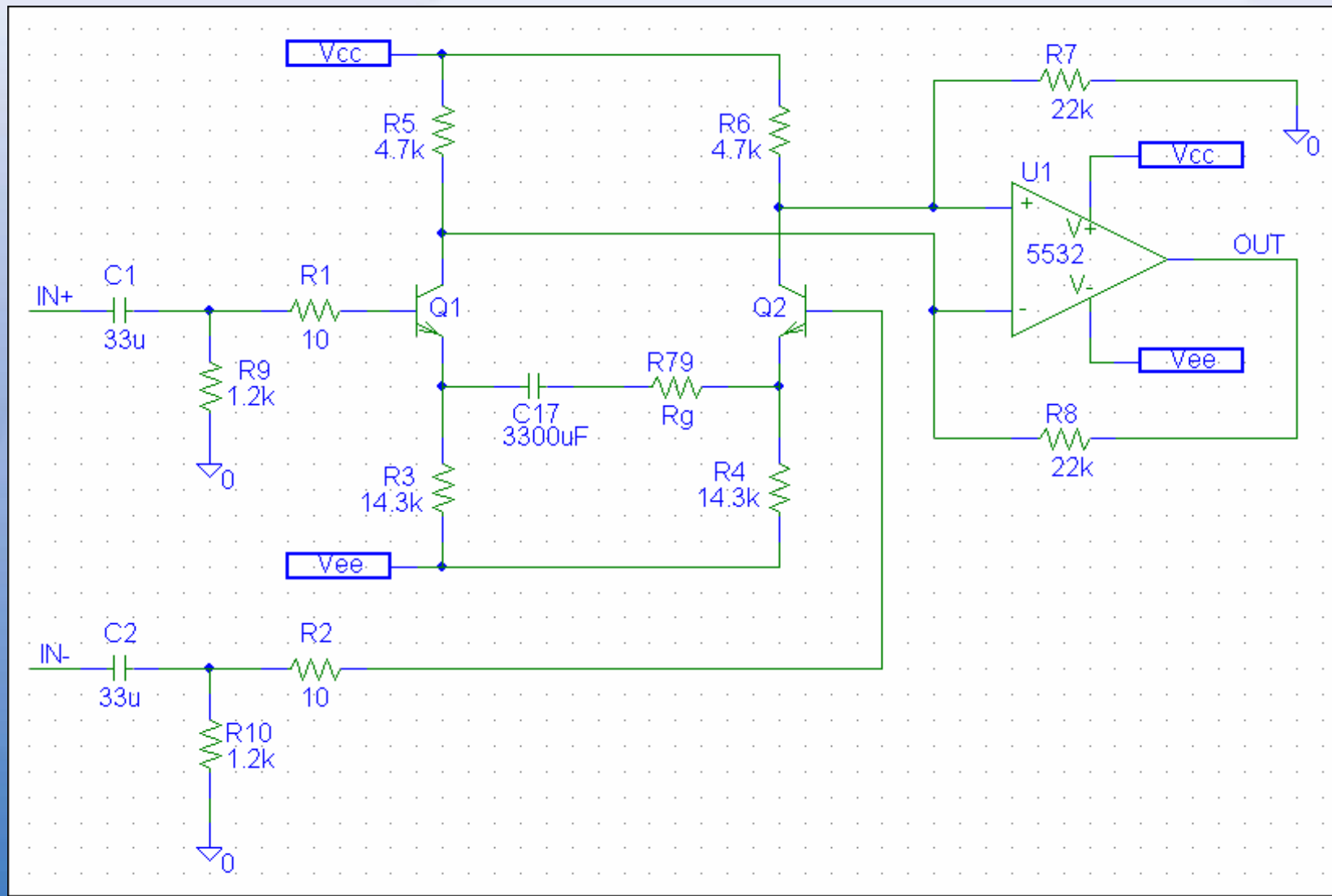


# Simple Mic Preamp

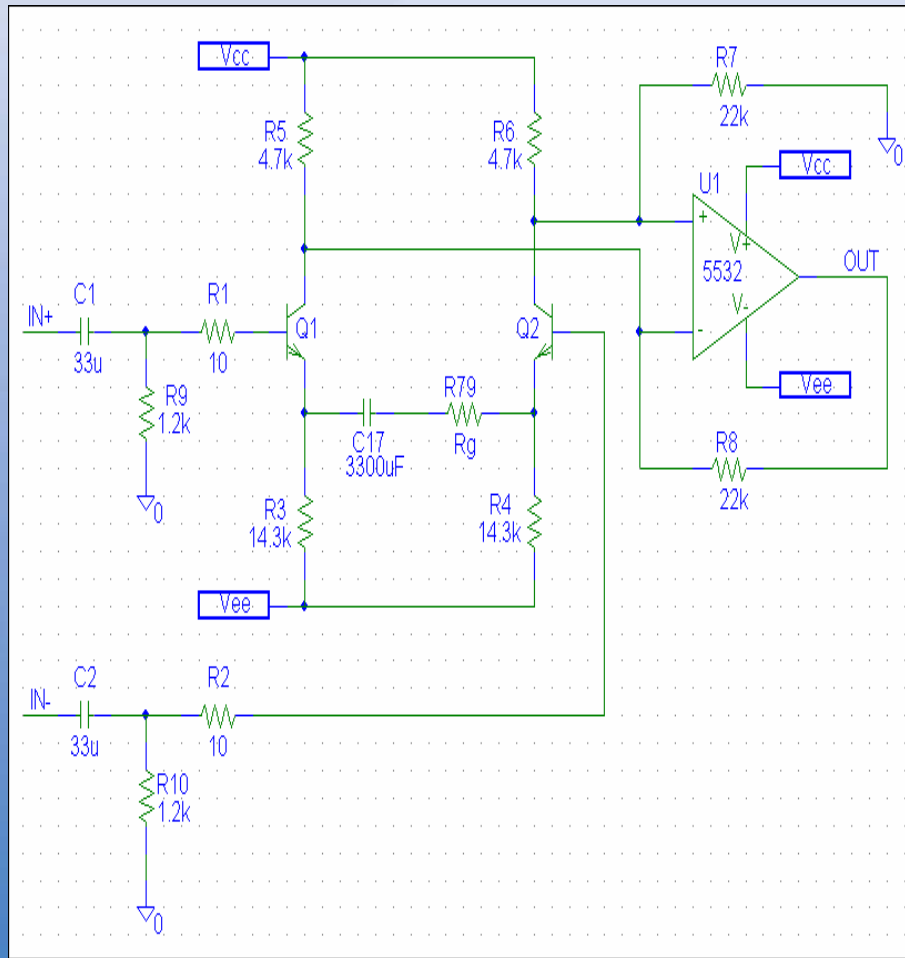


- $I_c = 1 \text{ mA}$  per input transistor, set by  $(|V_{EE}| - V_{BE})/14.3k$
- $\text{Diff Gain} = 22k/(r_e + R_g/2 || 14.3k)$
- where  $r_e = 1/g_m = KT/ql_C = 26 \text{ ohms}$
- But – “ $r_e$ ” is current dependent!
- Minimum gain =  $22k/14.3k = 3.7 \text{ dB}$

# Simple Mic Pre THD Performance

## THD vs. Gain, 1 kHz, +20 dBu Out

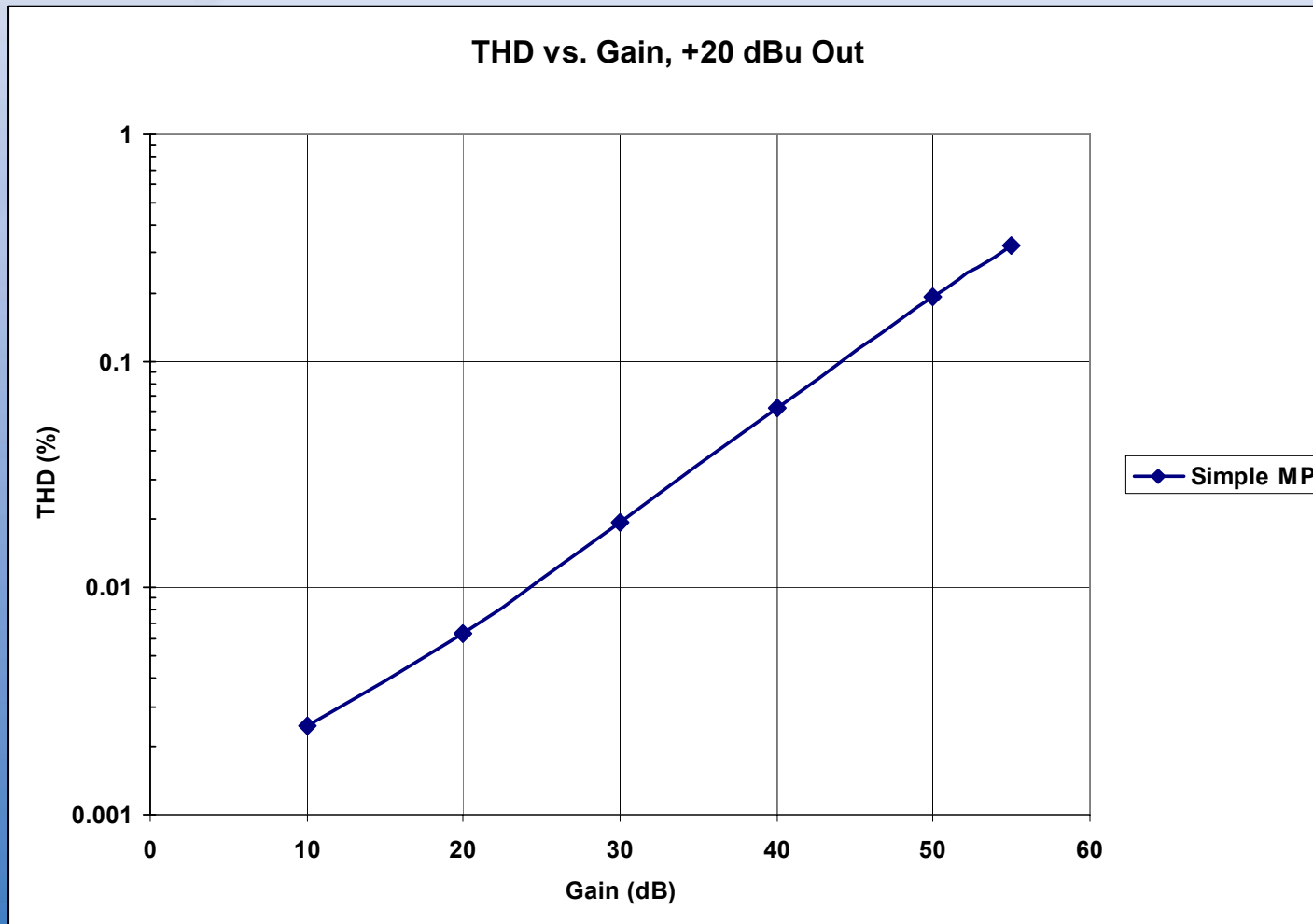

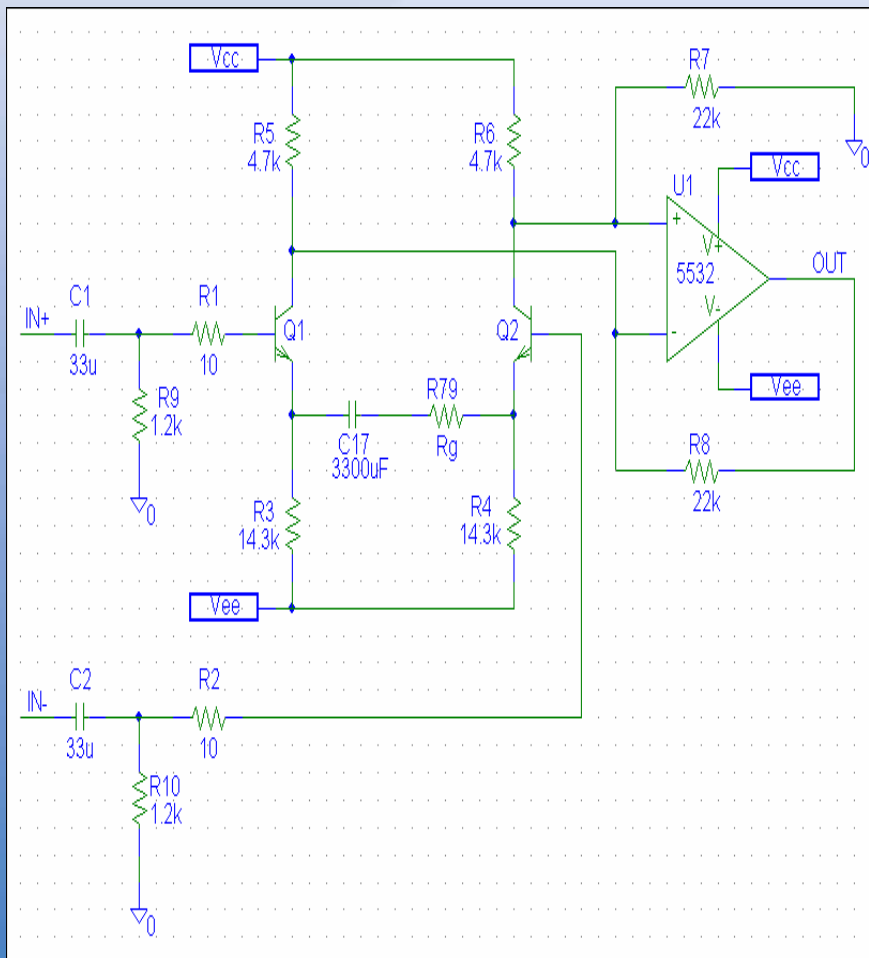
# High-Gain Noise Sources of Simple Mic Preamp



- Input noise at high gains dominated by:
- $Q_1, Q_2 I_C$  Shot Noise (RTI)  $= \frac{2\sqrt{qI_C}}{g_m} = \sqrt{4kTr_e}$
- $Q_1, Q_2 r_b$  Thermal Noise  $= \sqrt{8kTr_b}$
- $R_1, R_2, R_g$  Thermal Noise  $= \sqrt{4kT(R_1 + R_2 + R_g)}$

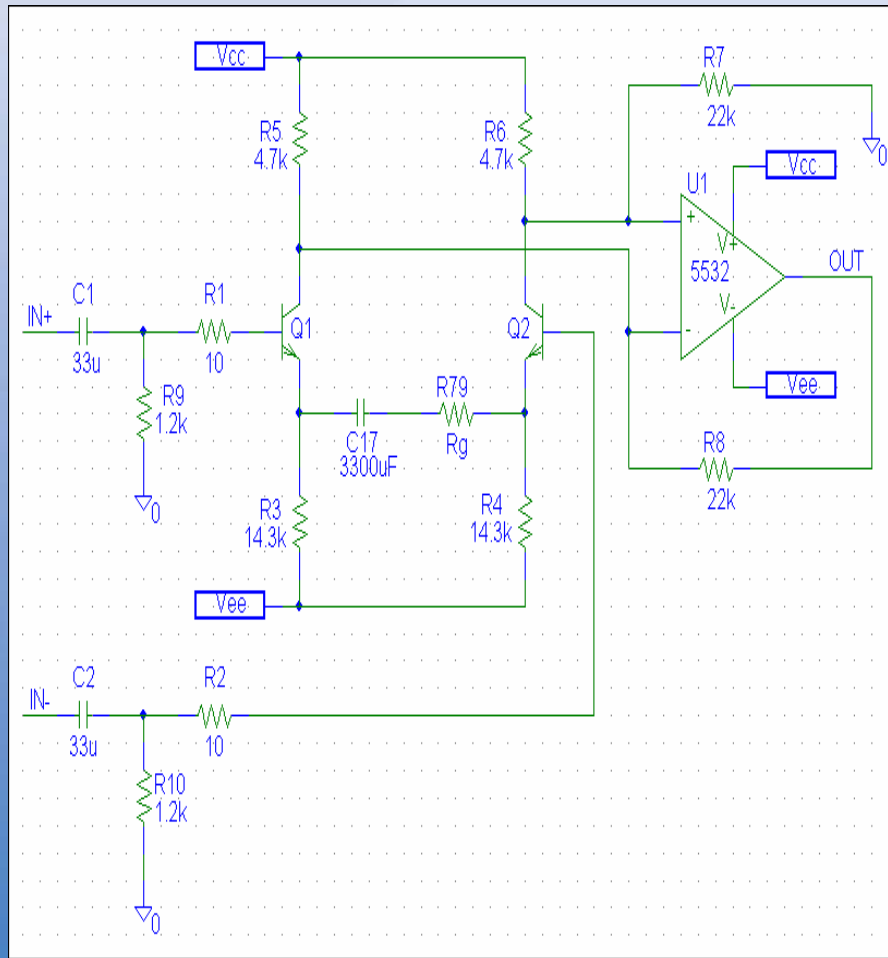
# Low-Gain Noise Sources of Simple Mic Preamp



- Input noise at low gains dominated by:
- Thermal Noise of  $R_5$  and  $R_6$
- Thermal Noise of:  


$$R_g \parallel (R_3 + R_4)$$
- $Q_1, Q_2$   $I_B$  shot noise across  $\frac{R_g \parallel (R_3 + R_4)}{2}$
- EIN of U1

# Noise Performance of Simple Mic Preamp

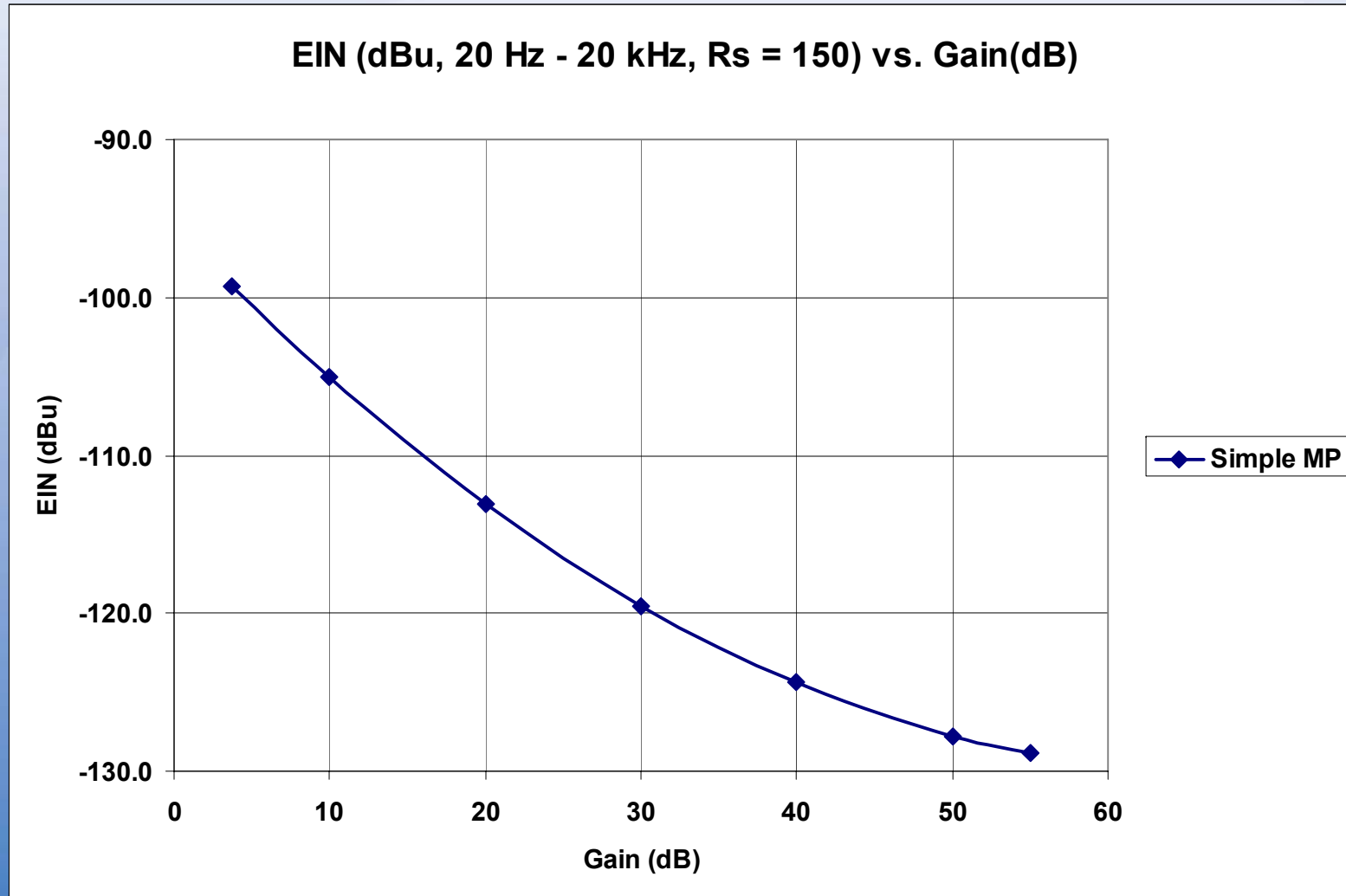



# CMRR Performance of Simple Mic Preamp

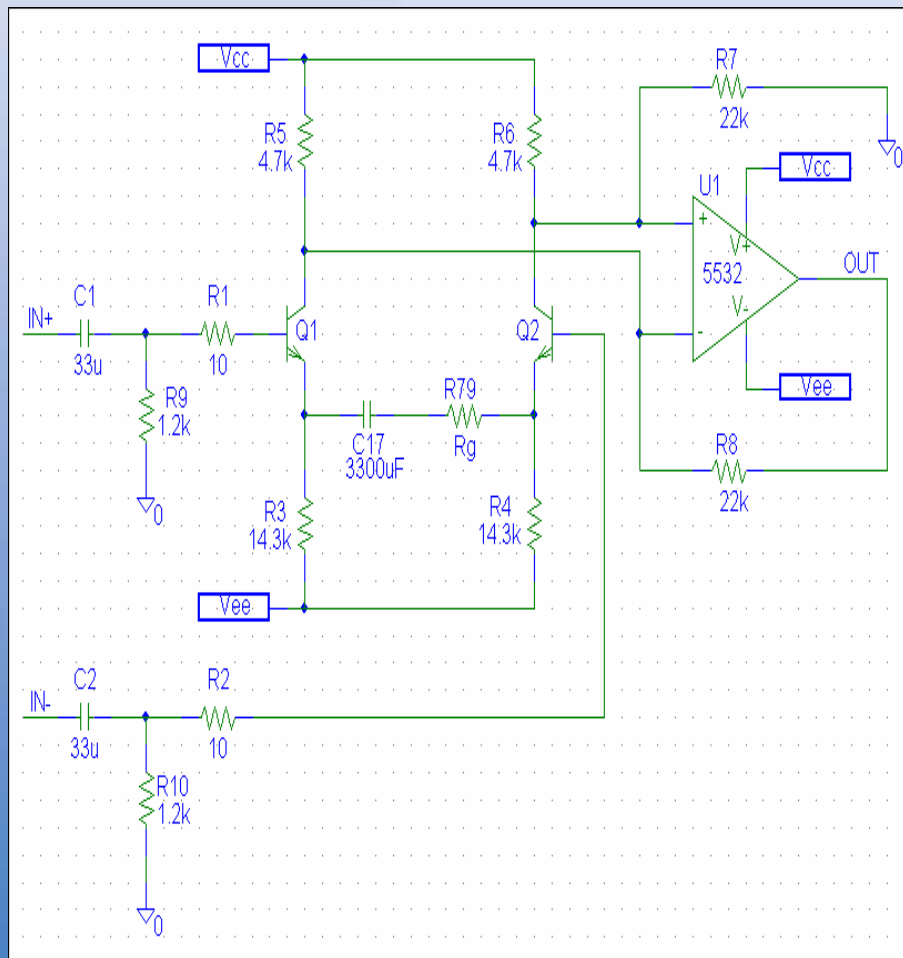


- CM to differential conversion can occur due to mismatches in:
- $R_3$  and  $R_4$
- $R_5$  and  $R_6$
- $R_7$  and  $R_8$
- $R_9$  and  $R_{10}$
- $Q_1$  and  $Q_2$


# Simple Mic Preamp

- 2 Transistors and 1 Opamp
- Very Low Cost
- Marginal Performance

# Complementary Feedback Pair Mic Preamp

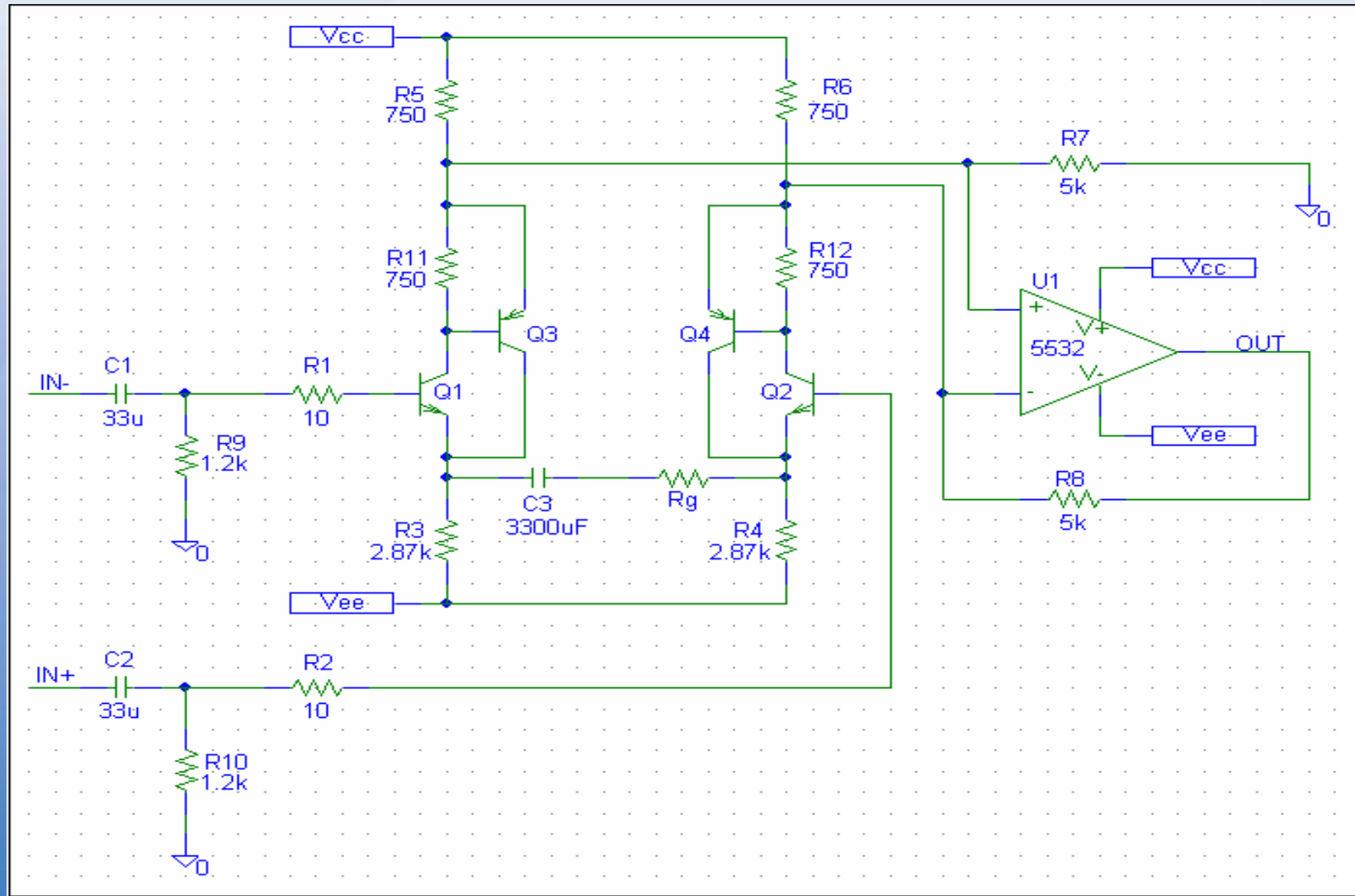


# CFP Mic Preamp

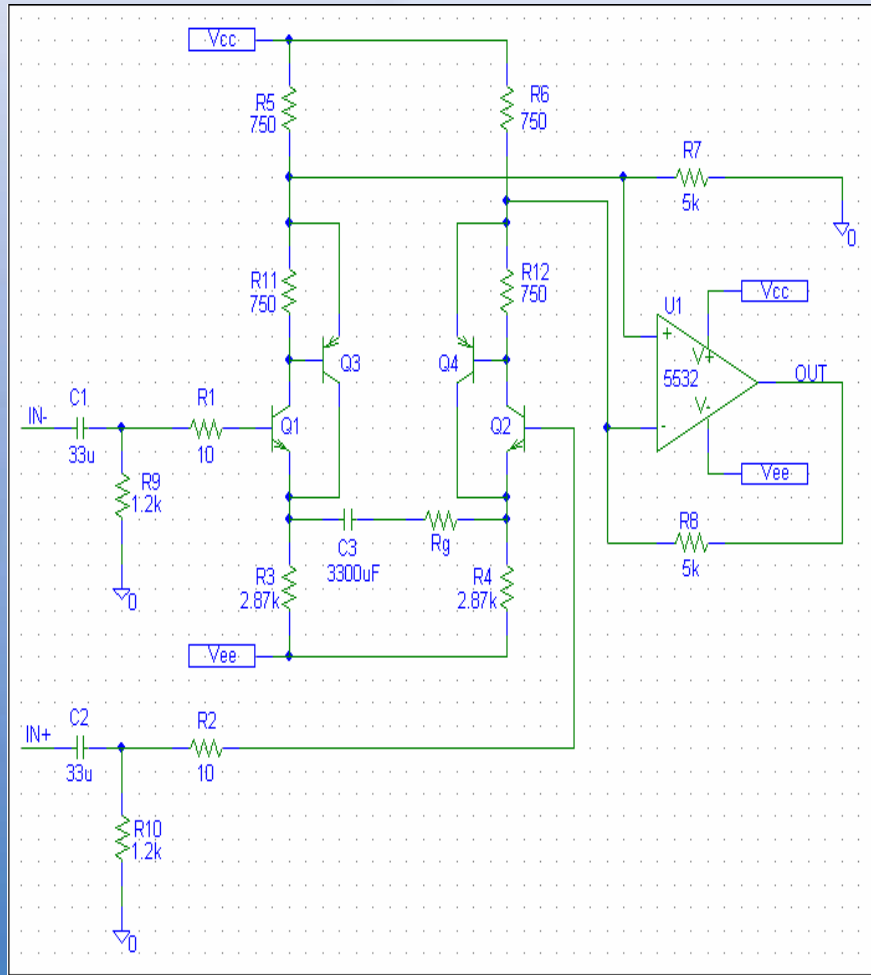

- Input devices are each a compound transistor (Complementary Feedback Pair)
- NPN Input  $I_c$  set by  $V_{be}/750$  ohms (1 mA each)
- NPN  $I_c$  + PNP  $I_c$  set by  $(|V_{ee}| - V_{be})/2k87$  (5 mA per side)


# CFP Mic Preamp

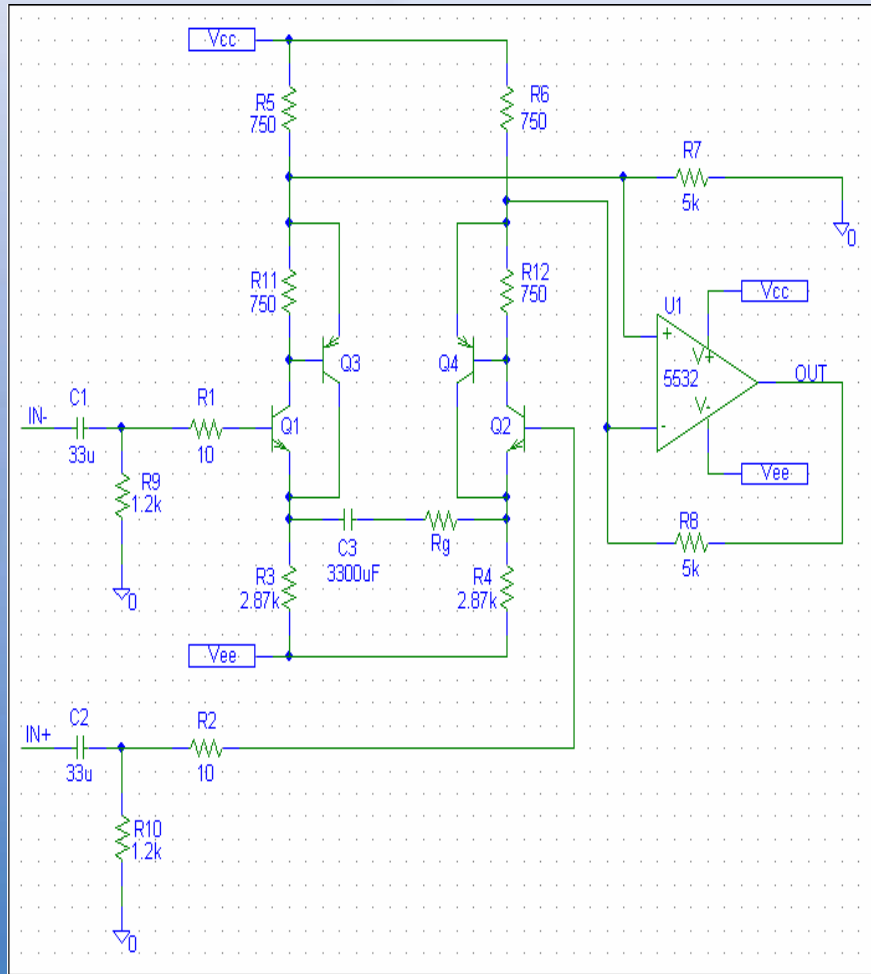


- Output impedance at NPN emitters is  
now:  $r_o = \frac{1}{g_m(1+\beta_{PNP} \cdot \frac{R_{11}}{r_{\pi PNP} + R_{11}})}$
- Still current dependent, but much lower
- Gain =  $5k/(r_e/74 + Rg/2 || 2.87k)$
- Minimum Gain =  $5k/2.87k = 4.8 \text{ dB}$

# THD Performance of CFP Mic Preamp

## THD vs. Gain, 1 kHz, +20 dBu Out

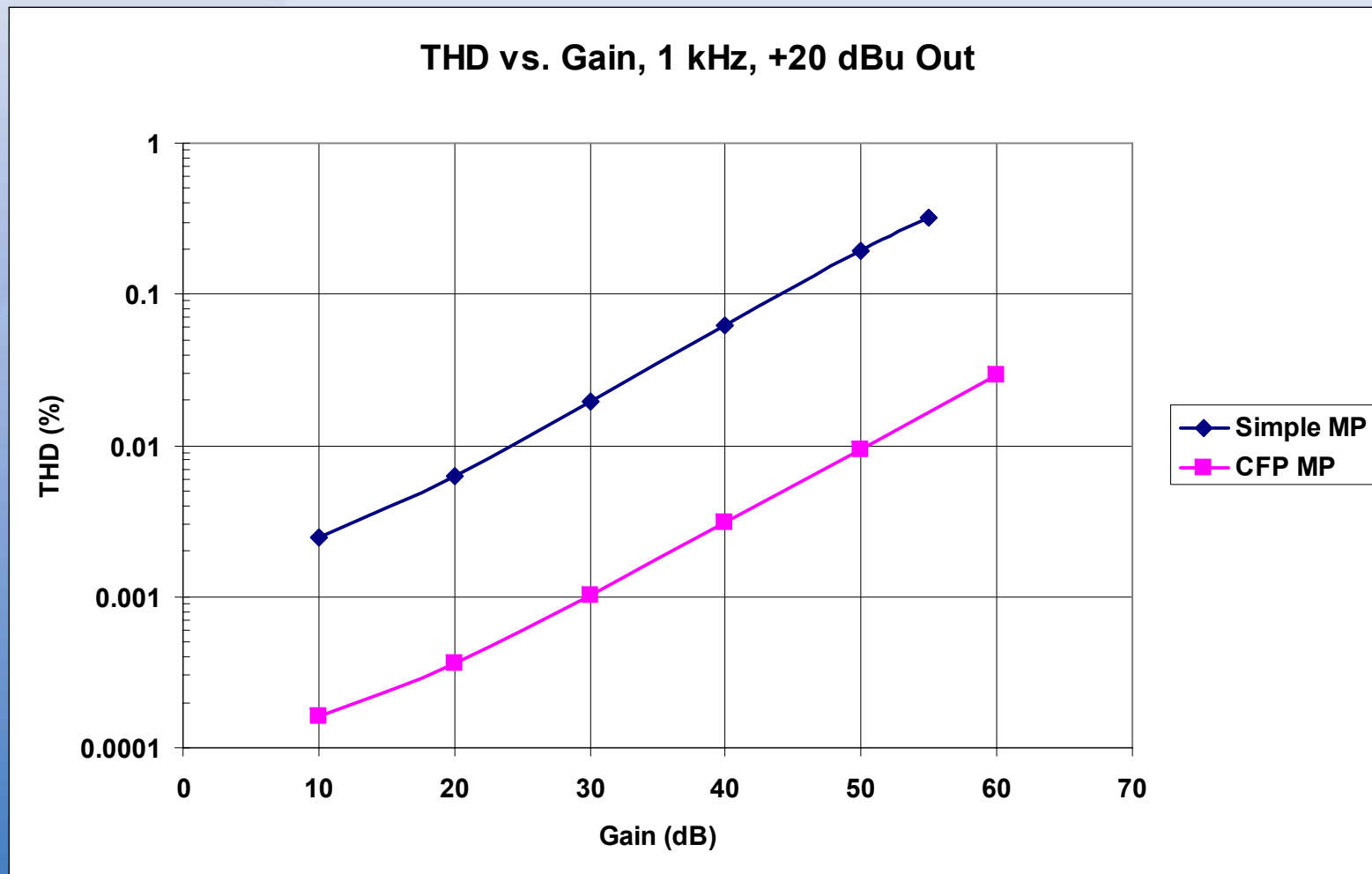

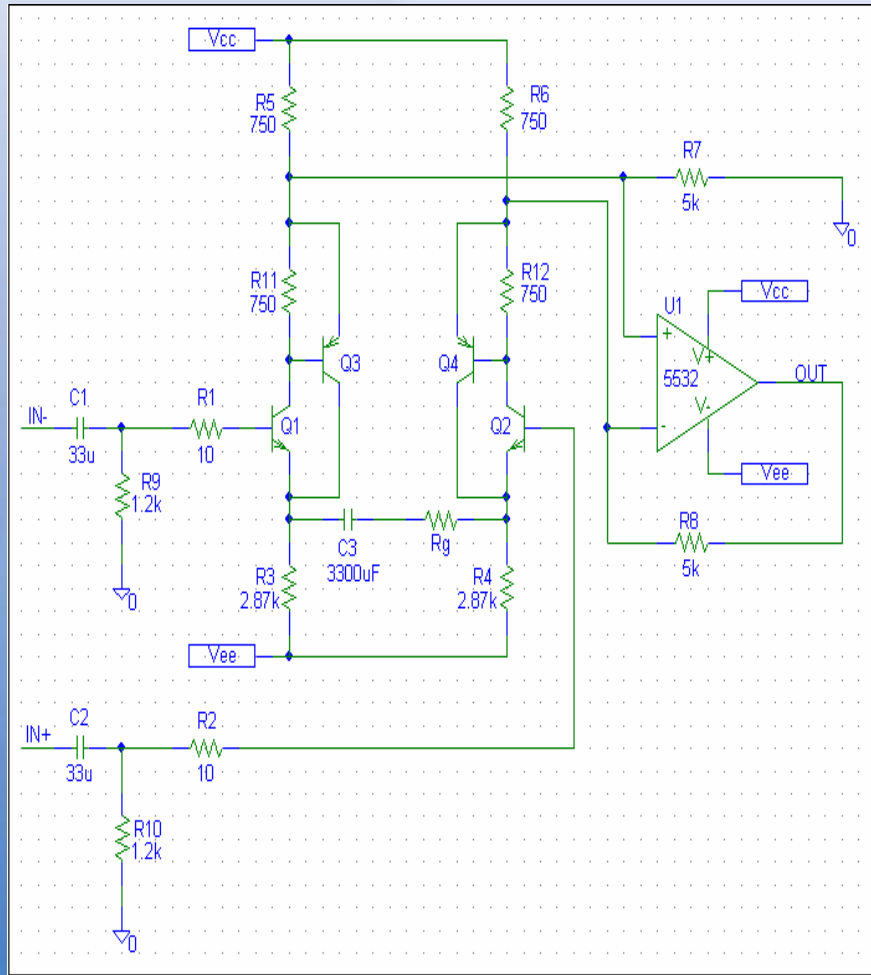
# High-Gain Noise Sources of CFP Mic Preamp



- Input noise at high gains dominated by:
- $Q_1, Q_2 I_C$  Shot Noise (RTI)  $= \frac{2\sqrt{qI_C}}{g_m} = \sqrt{4kTr_e}$
- $Q_1, Q_2 r_b$  Thermal Noise  $= \sqrt{8kTr_b}$
- $R_1, R_2, R_g$  Thermal Noise  $= \sqrt{4kT(R_1 + R_2 + R_g)}$

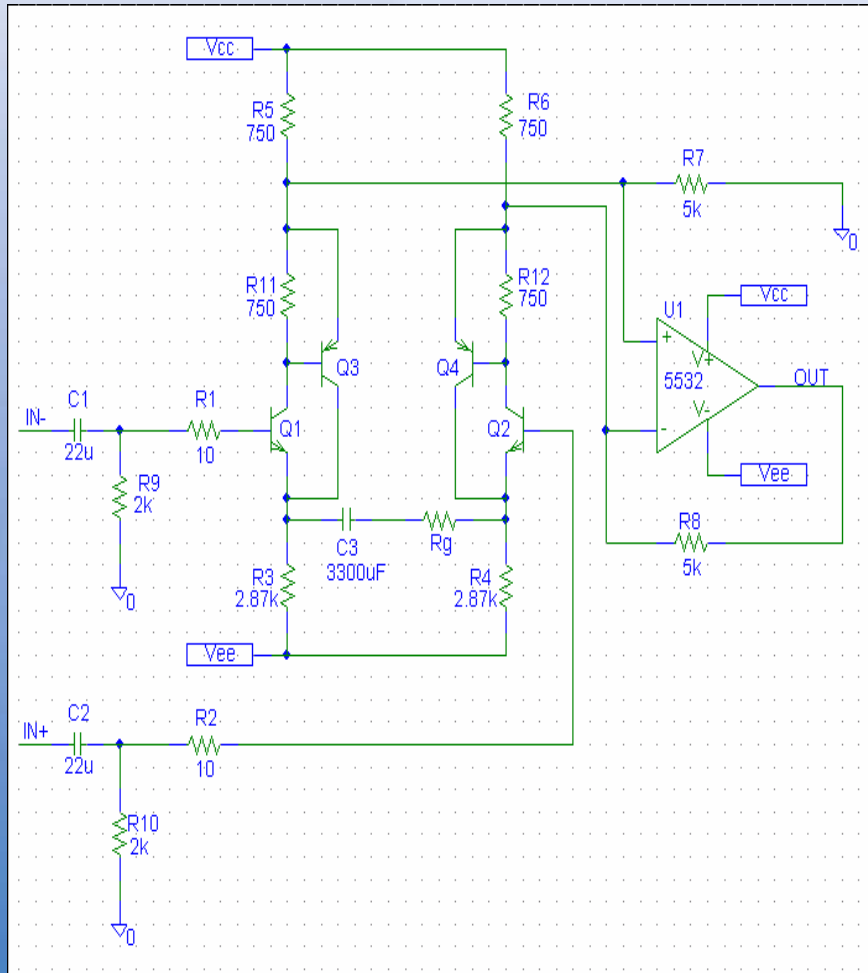
# Low-Gain Noise Sources of CFP Mic Preamp




- Input noise at low gains dominated by:
- Thermal Noise of  $R_5$  and  $R_6$
- EIN of U1
- Thermal Noise of  $R_g \parallel (R_3 + R_4)$
- $Q_1, Q_2 I_B$  shot noise across  $\frac{R_g \parallel (R_3 + R_4)}{2}$



# Noise Performance of CFP Mic Preamp

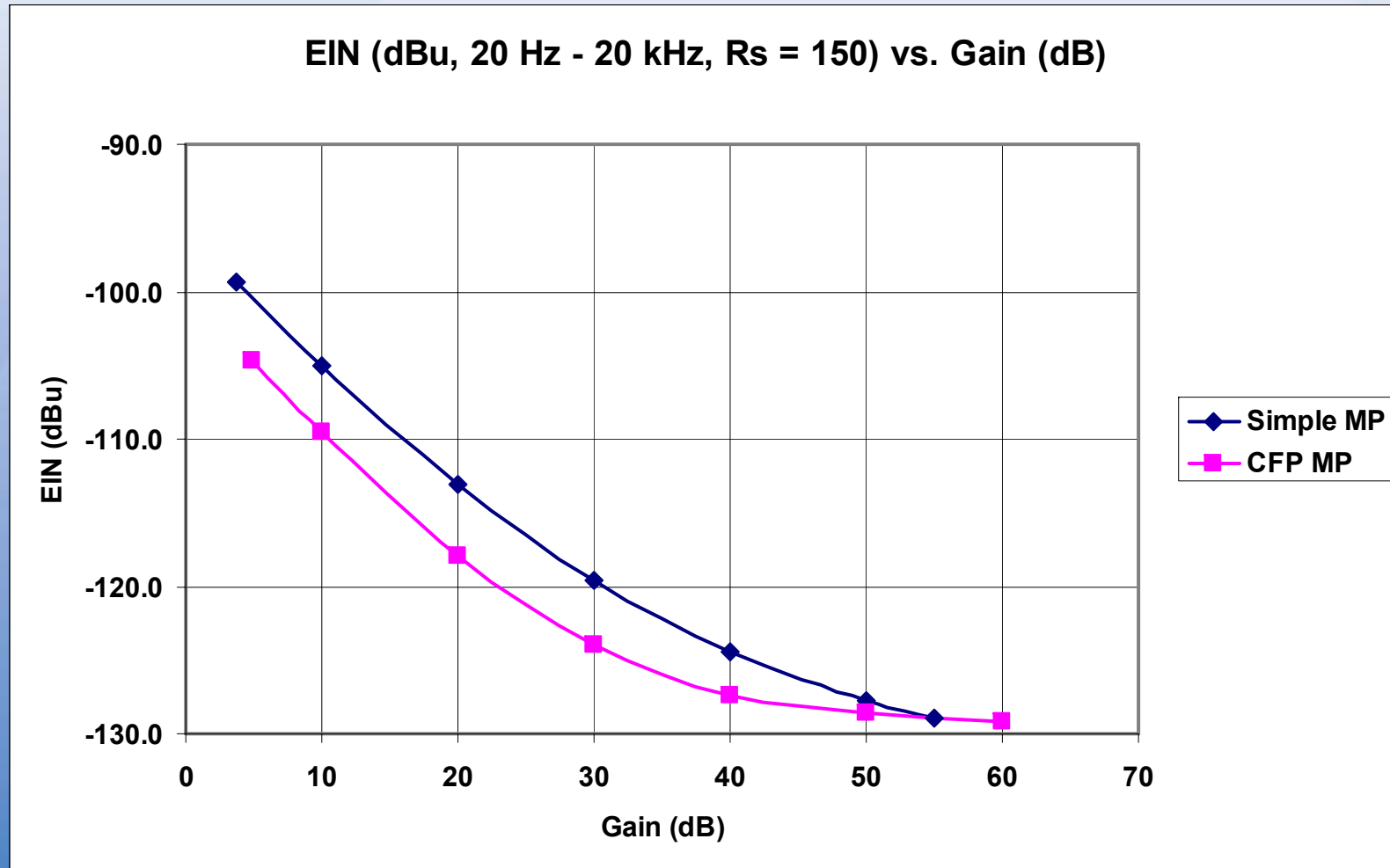

# CMRR Performance of CFP Mic Preamp

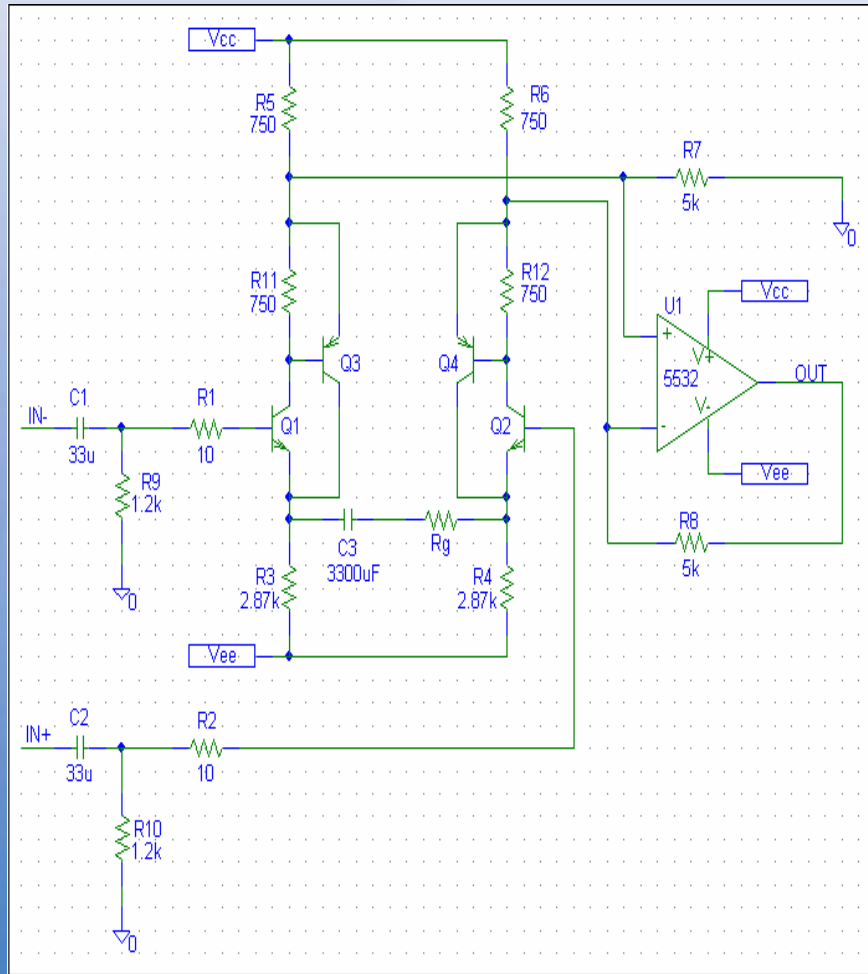

- CM to Diff conversion can occur due to mismatches in:
- $R_3$  and  $R_4$
- $R_5$  and  $R_6$
- $R_7$  and  $R_8$
- $R_9$  and  $R_{10}$
- $R_{11}$  and  $R_{12}$


# CFP Mic Preamp

- Performance is improved over Simple Mic Preamp
- Distortion performance still not terrific at high gains
- Power consumption is high to get that performance
- Cost is modest


# Current Feedback Instrumentation Amp

- Topology used in most integrated mic preamp ICs including ADI - SSM2019, TI - INA103, INA163, INA217, THAT – 1510, 1512, 1570 and possibly others
- Scott Wurcer – AD524 IEEE Paper 12/82
- Graeme Cohen AES Paper – “Double Balanced Microphone Amplifier” 9/84

# Basic CFIA Mic Preamp Schematic

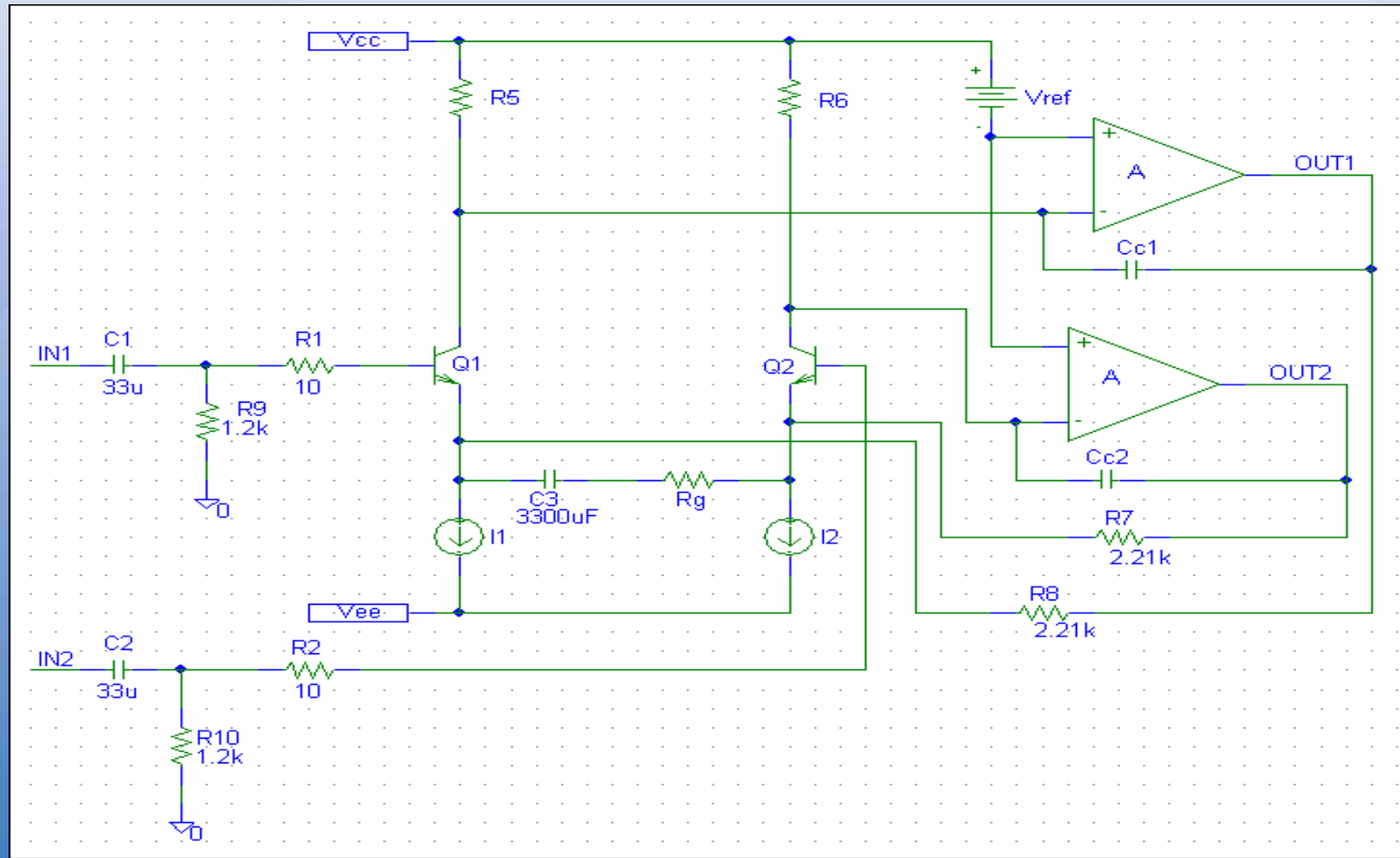


# Basic CFIA Mic Preamp

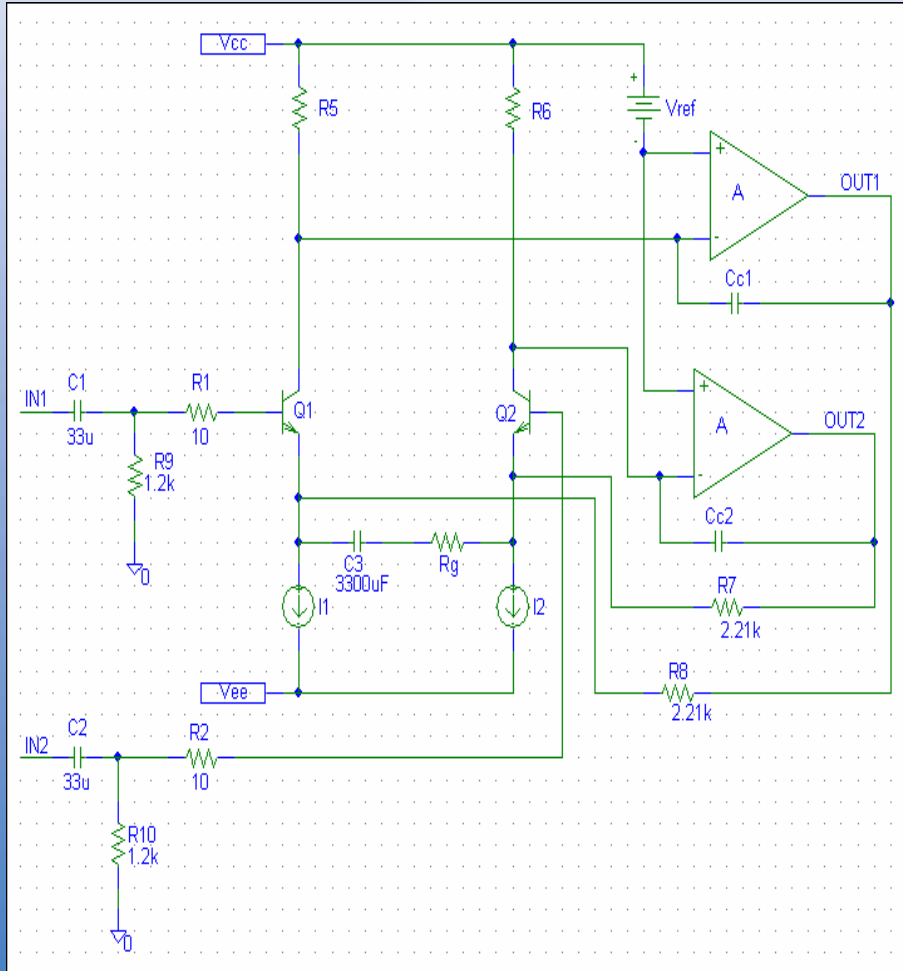


- Input Transistor  $I_c = V_{ref}/R_5$
- Current Sources  $I_1$  and  $I_2$  are for “bias current cancellation” only
- Gain =  $1 + (2R_7/R_g)$
- Min. gain = 0 dB

# What's "Current Feedback"?

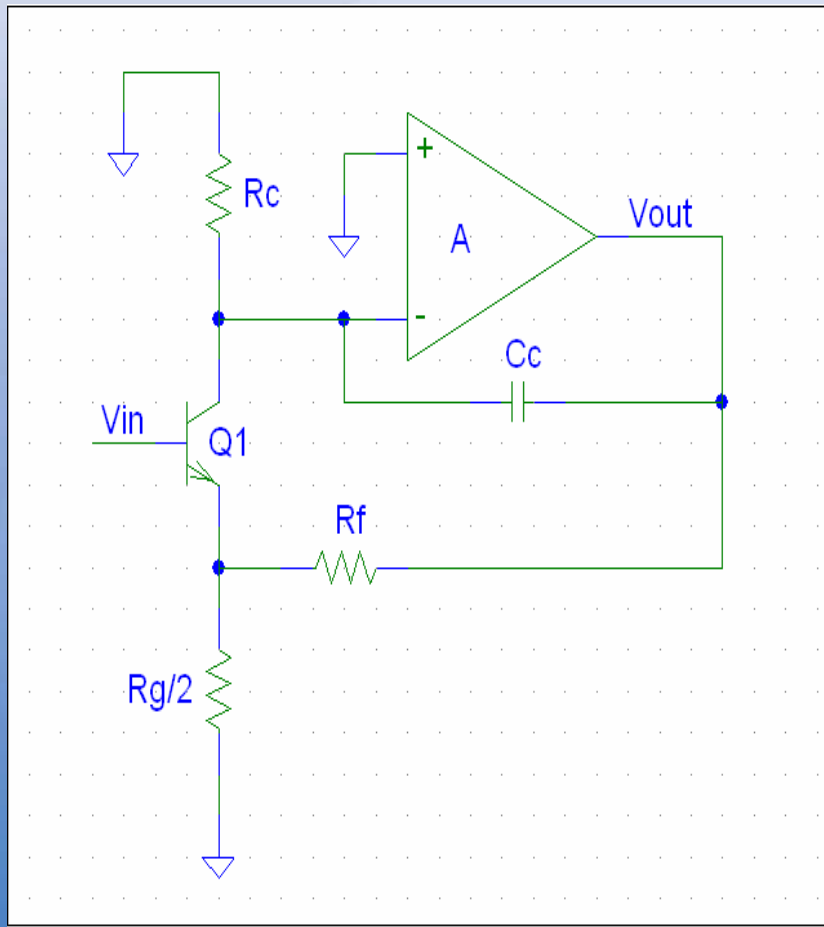

- Closed loop bandwidth stays substantially constant with closed loop gain until  $r_e$  becomes a significant factor
- $Cc$  charging current is not limited

# “Half Circuit” of CFIA

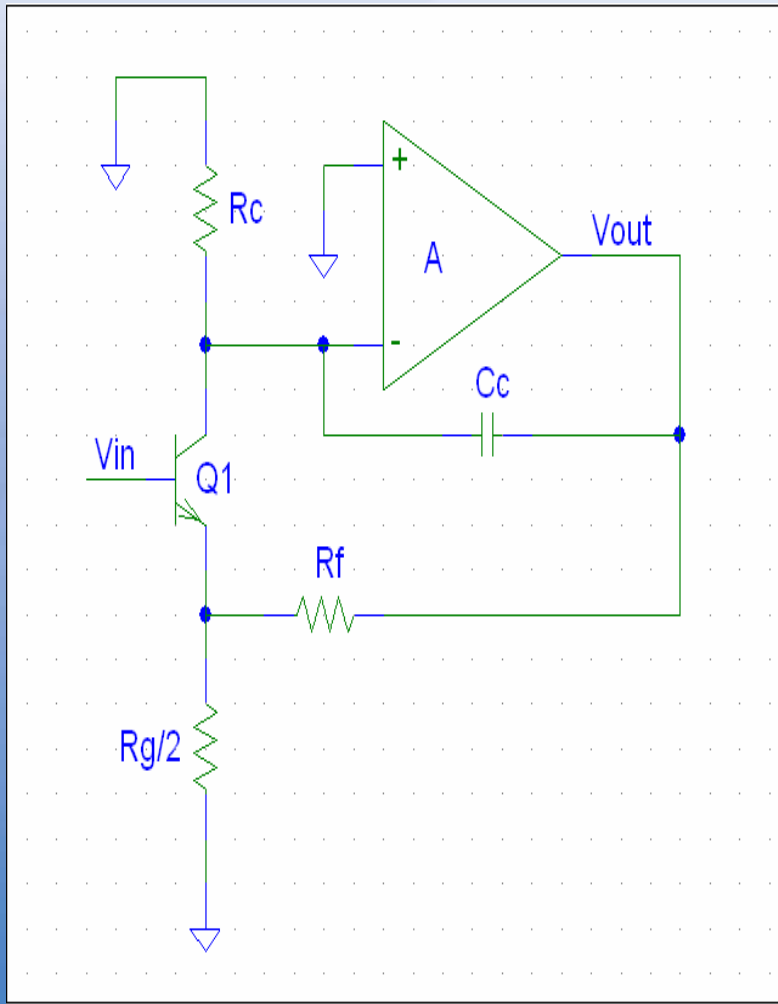

$$\frac{V_{out}}{V_{in}} = \frac{\frac{R_C \cdot A}{[r_e + (R_F \parallel R_G/2)](R_C C_M S + 1)}}{1 + \frac{R_C \cdot A}{[r_e + (R_F \parallel R_G/2)](R_C C_M S + 1)} \cdot \frac{R_G}{2R_F + R_G}} = \frac{A}{1 + A\beta}$$

Where  $C_M = C_C(A+1)$ ,  $r_e = 1/g_m$


For  $r_e \ll (R_F \parallel R_G/2)$ :

$$\frac{V_{out}}{V_{in}} = \frac{\frac{R_C \cdot A}{(R_F \parallel R_G/2)(R_C C_M S + 1)}}{1 + \frac{R_C \cdot A}{R_F(R_C C_M S + 1)}} = \frac{A}{1 + A\beta}$$

**Note that the loop transmission  $A\beta$  is independent of the closed loop gain if  $r_e$  is much less than the feedback network impedance**



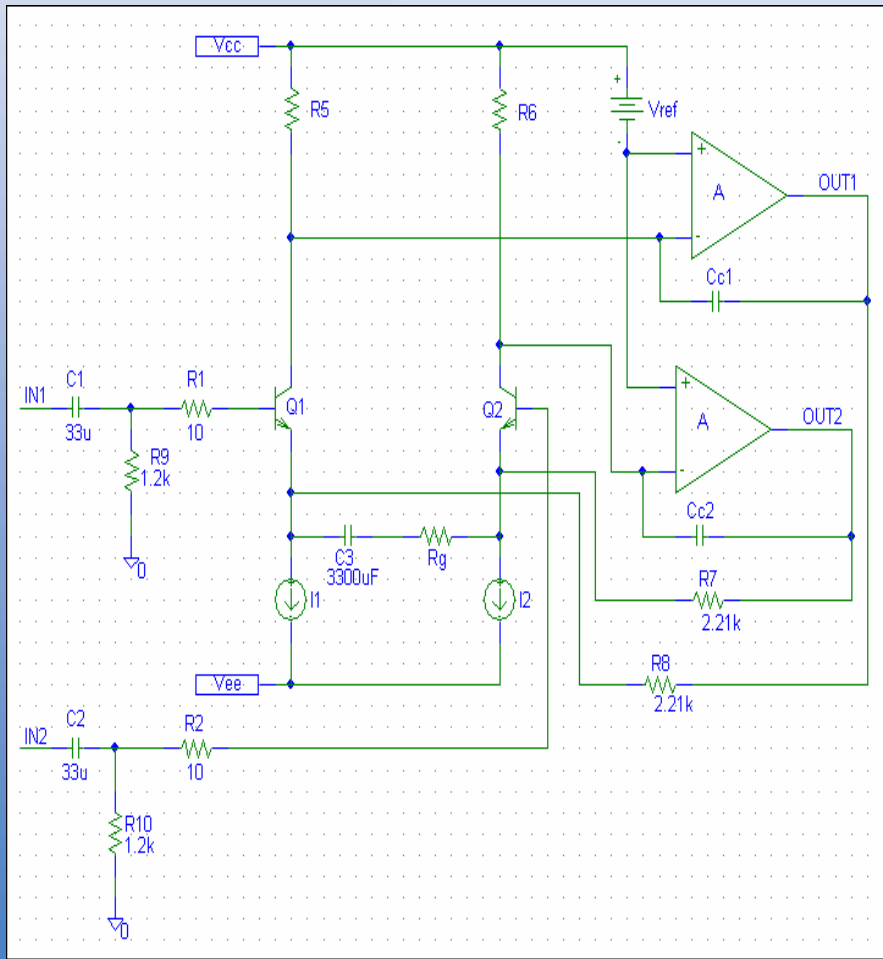
# High-Gain Noise Sources of CFIA Mic Preamp




- Input noise at high gains dominated by:
- $Q_1, Q_2 I_C$  Shot Noise (RTI)  $= \frac{2\sqrt{qI_C}}{g_m} = \sqrt{4kTr_e}$
- $Q_1, Q_2 r_b$  Thermal Noise  $= \sqrt{8kTr_b}$
- $R_1, R_2, R_g$  Thermal Noise  $= \sqrt{4kT(R_1 + R_2 + R_g)}$
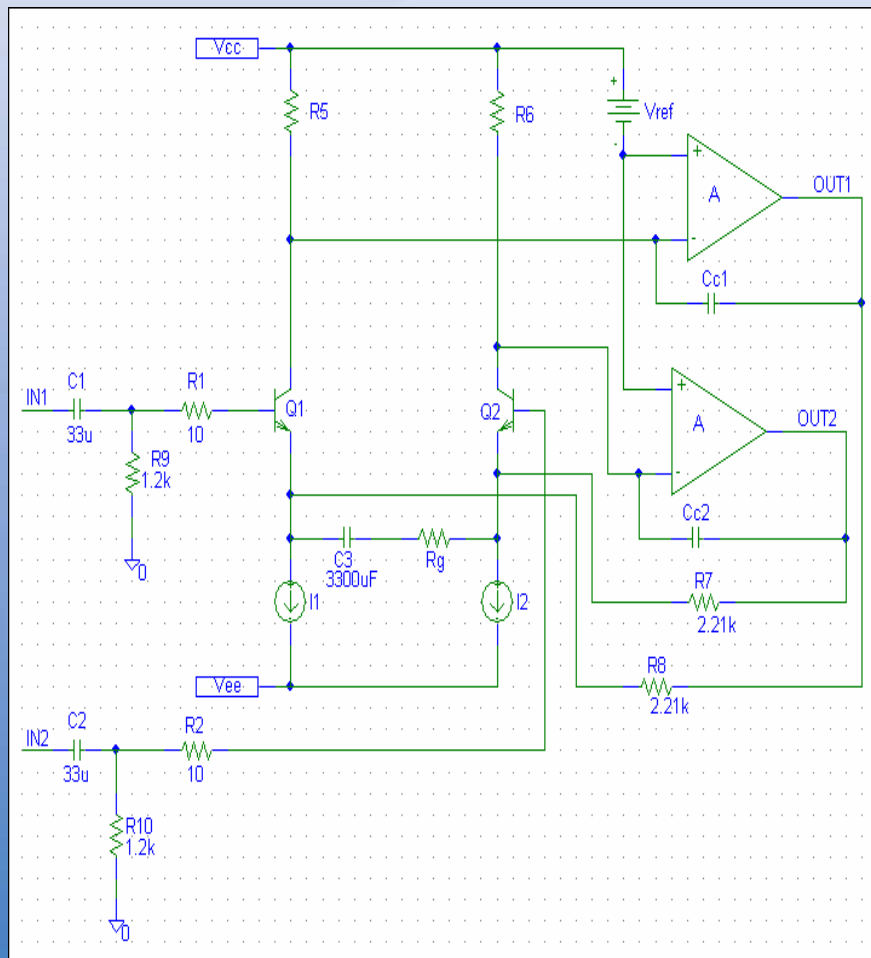
# Low-Gain Noise Sources of CFIA Mic Preamp




- Input noise at low gains dominated by:
- Thermal Noise of  $R_5, R_6$
- Noise of  $I_1, I_2$
- Thermal Noise of  $R_g \parallel (R_7 + R_8)$
- $Q_1, Q_2 I_B$  shot noise across  $\frac{R_g \parallel (R_7 + R_8)}{2}$
- EIN of U1, U2

# CMRR Performance of CFIA Mic Preamp

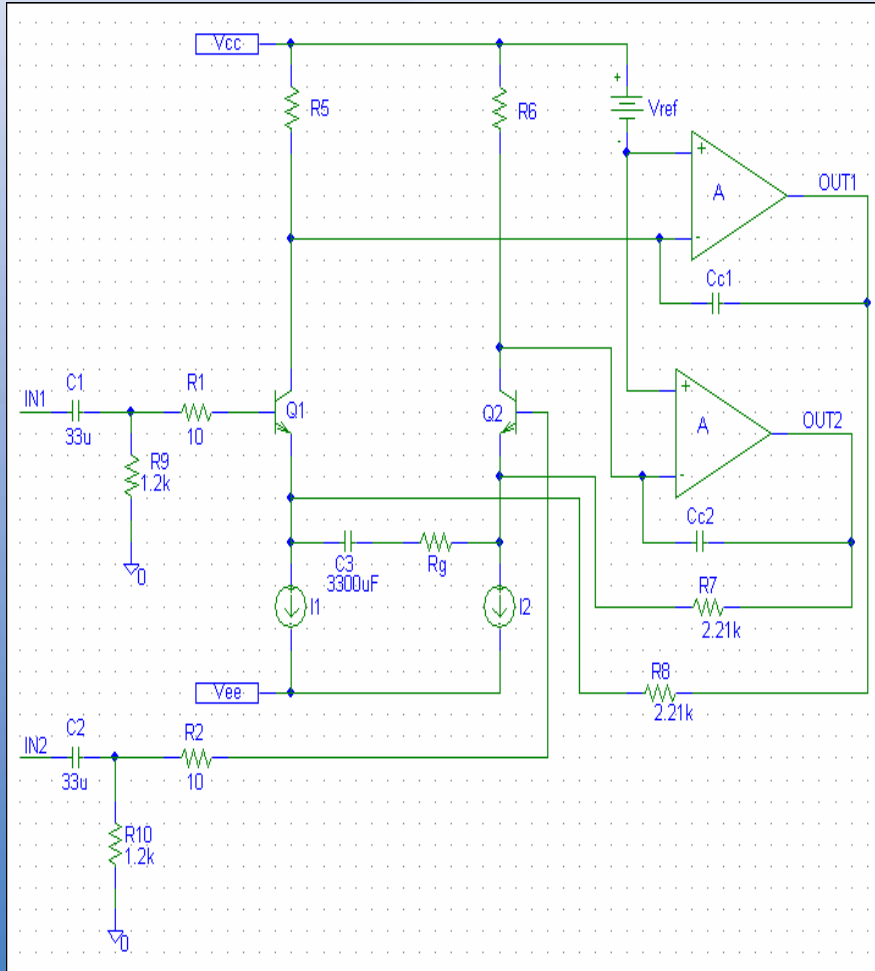


- Unity CM Gain to OUT1 – OUT2
- CMRR = Differential Gain
- CM to Diff conversion can occur due to mismatches in transistors

# Refinements to the CFIA

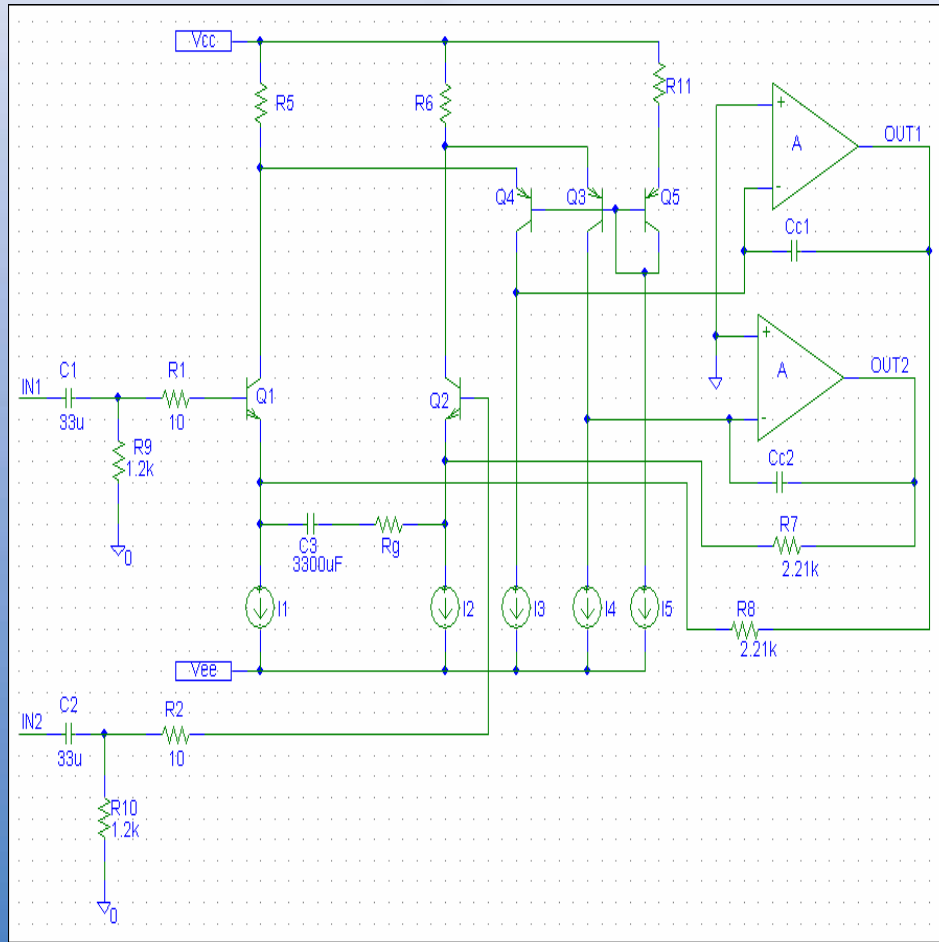


- Early effect and  $C_{cb}$  mismatch in the current source transistors can also contribute to THD at low gains
- Cascoding helps here at the expense of some input CM range
- A Folded Cascode can minimize the noise contribution of the integrator stages and  $R_5$  and  $R_6$  while minimizing the impact on input CM range
- At this level of complexity an IC makes sense and the good device matching helps performance

# A Real Example THAT's 1570 CFIA

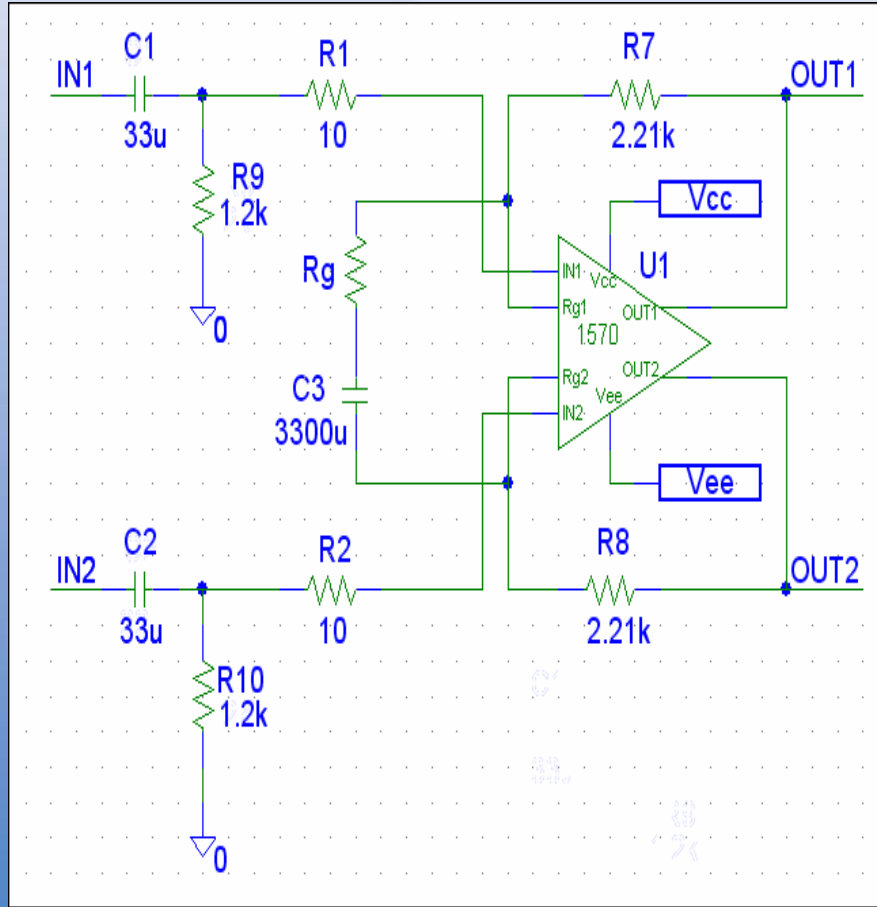


- An integrated circuit current-feedback instrumentation amplifier front end
- Utilizes the techniques described on the previous slide.
- Compensated for  $R_F$  values down to 2 kohm

# 1570 Bandwidth vs. Gain

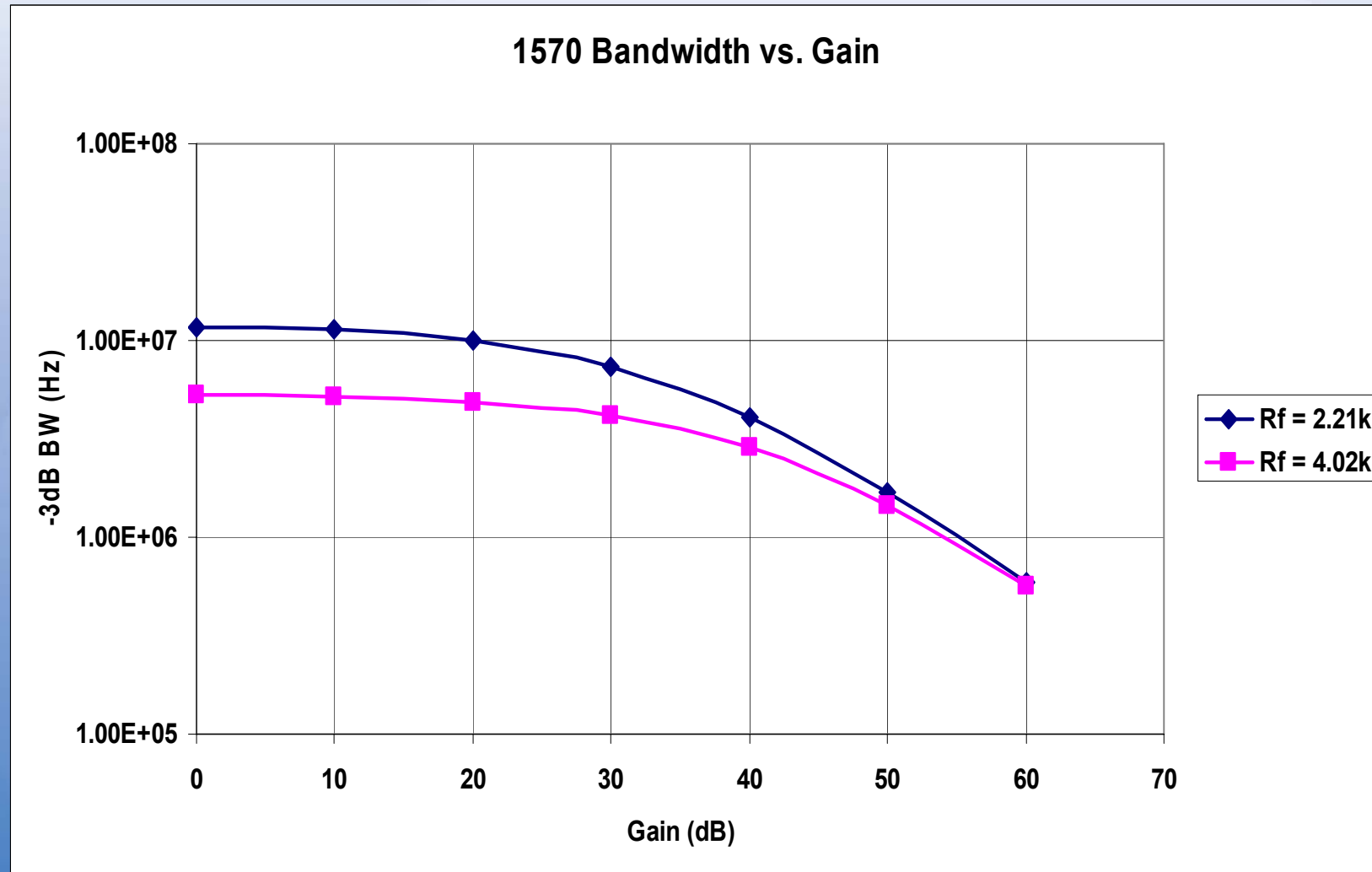

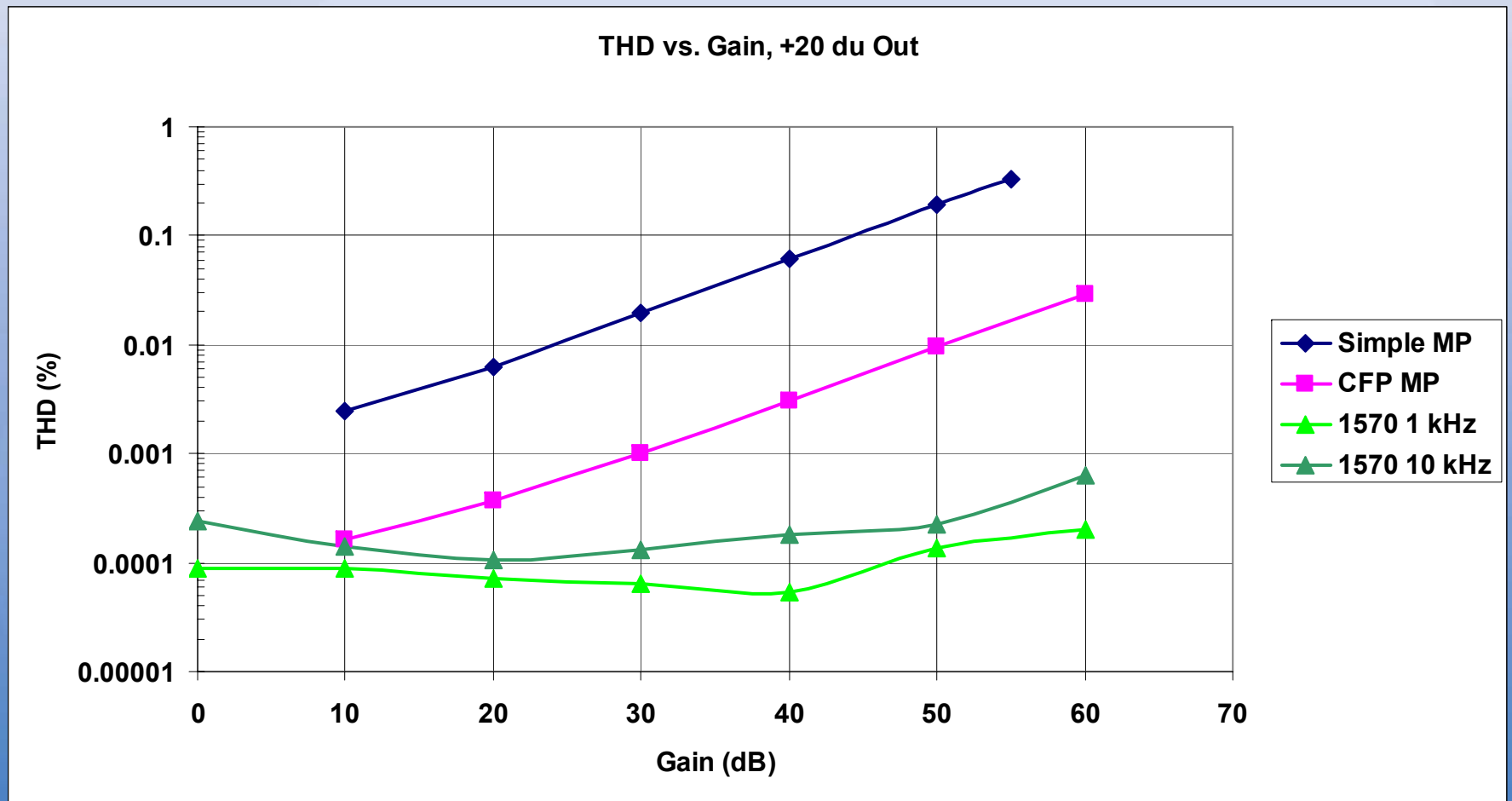
# THD Performance of 1570 Mic Preamp

THD vs. Gain, +20 dBu Out,  $R_f = 2.21k$




# Noise Performance of 1570

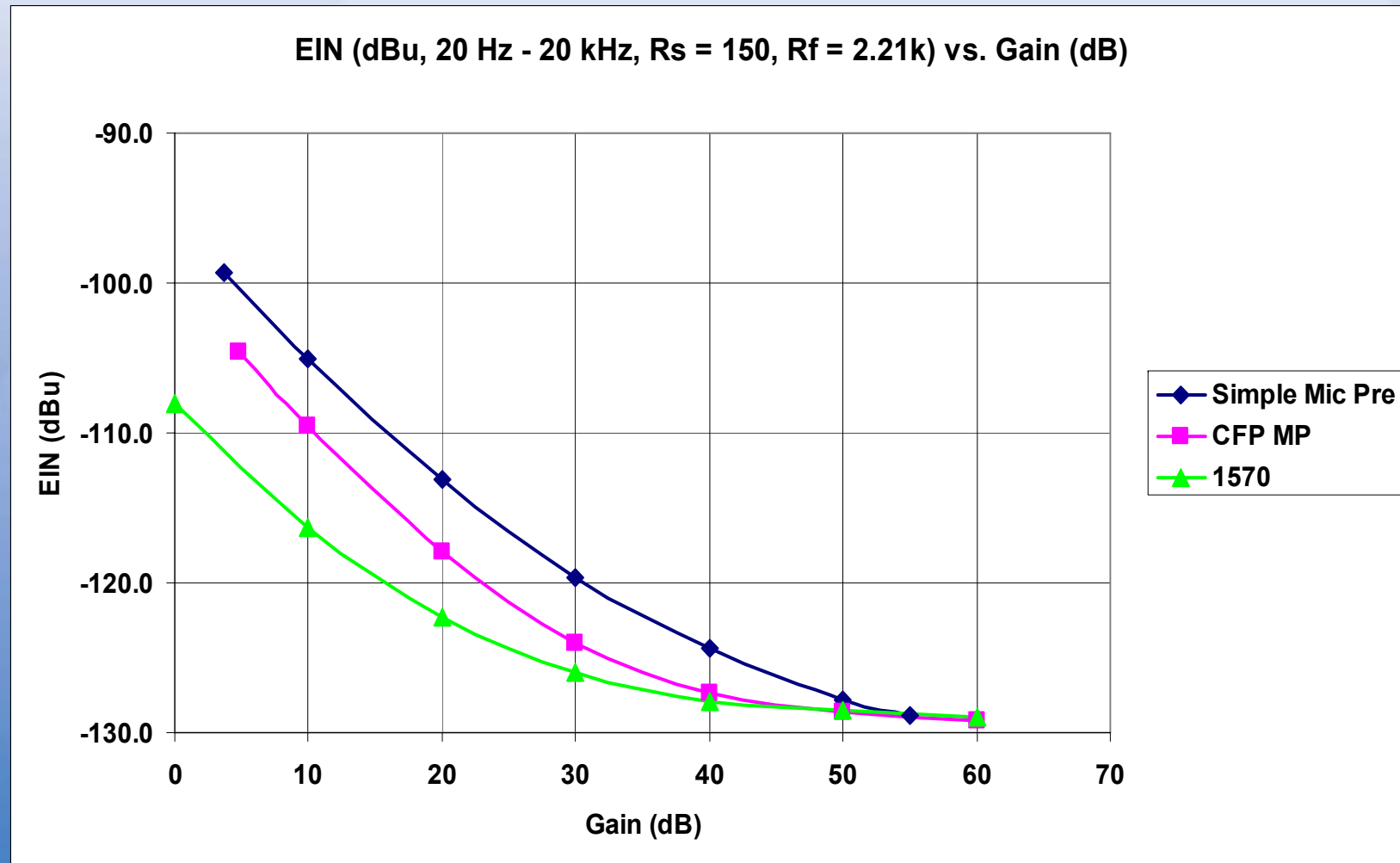



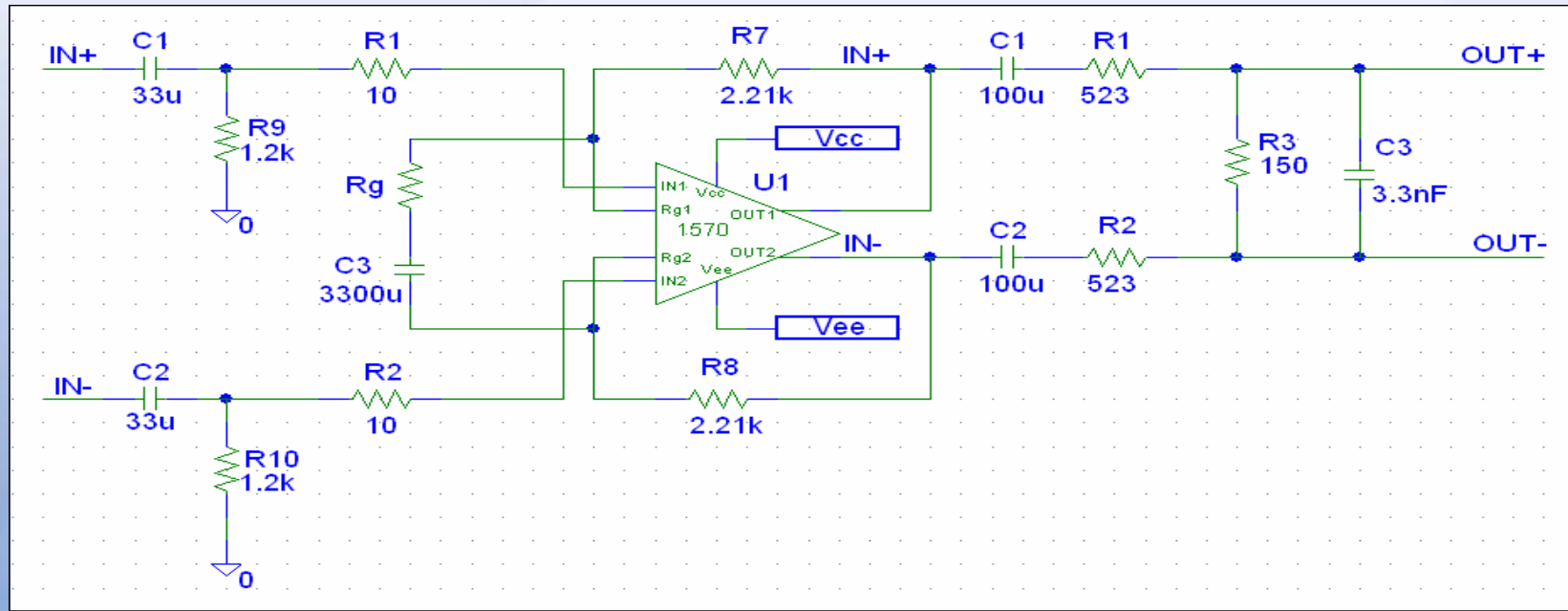
# Utilizing the Differential Output to Drive A/D Converters




- The cheap and simple way:
- Rely on the A/D converter for CMRR at low gains
- Converter CM input range might be an issue as the pad does not attenuate CM signals

# Birt Circuit

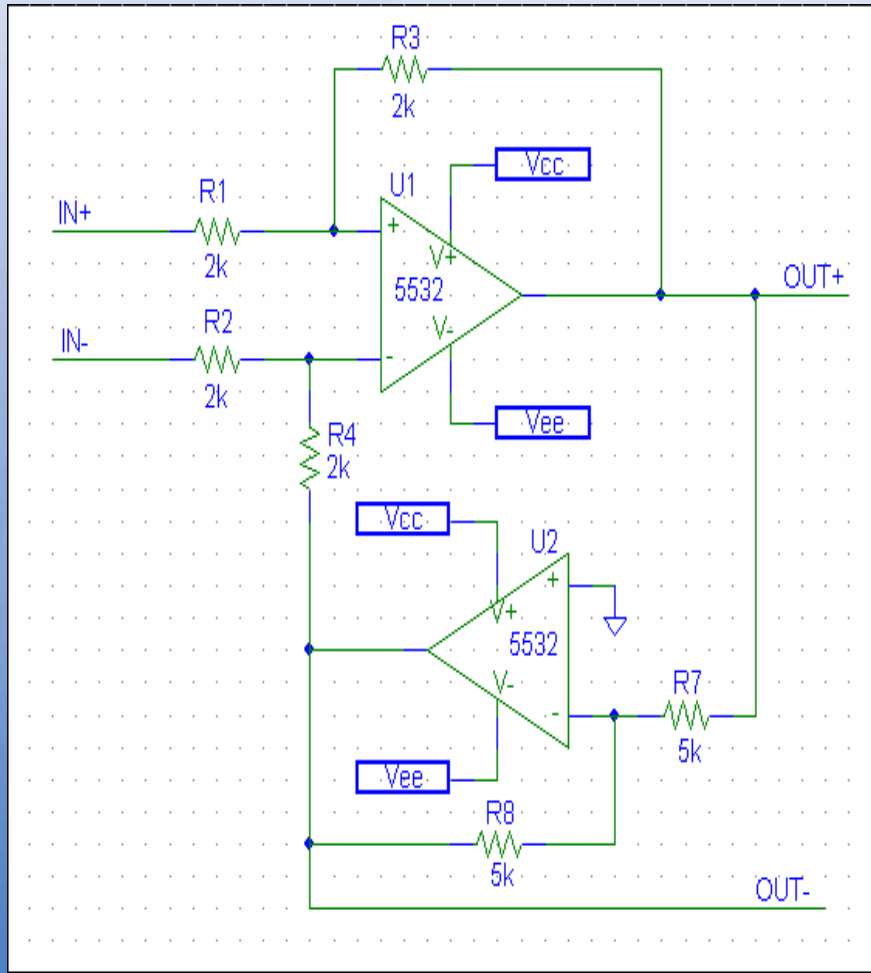


- David Birt, 1990
- Provides CMRR
- $\text{Gain} = R_3/R_1$
- Provides a convenient input for a CM DC reference voltage
- U2 input offset and noise appear as CM at  $\text{OUT+} - \text{OUT-}$
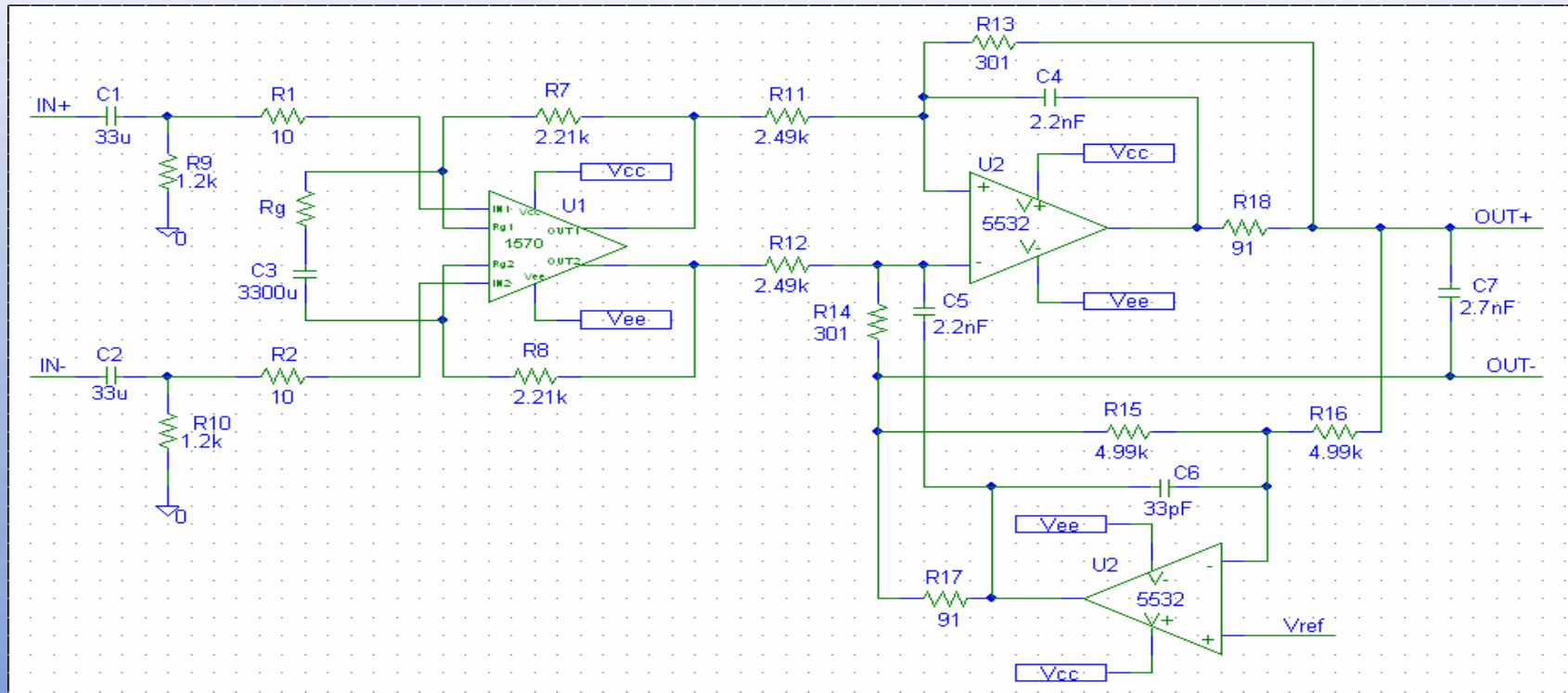
# Birt Circuit Applied to 1570 and A/D Drive




- The resistor ratios provide 18 dB of attenuation before the A/D
- The feedback networks enable capacitive load driving with low audio-band output impedance
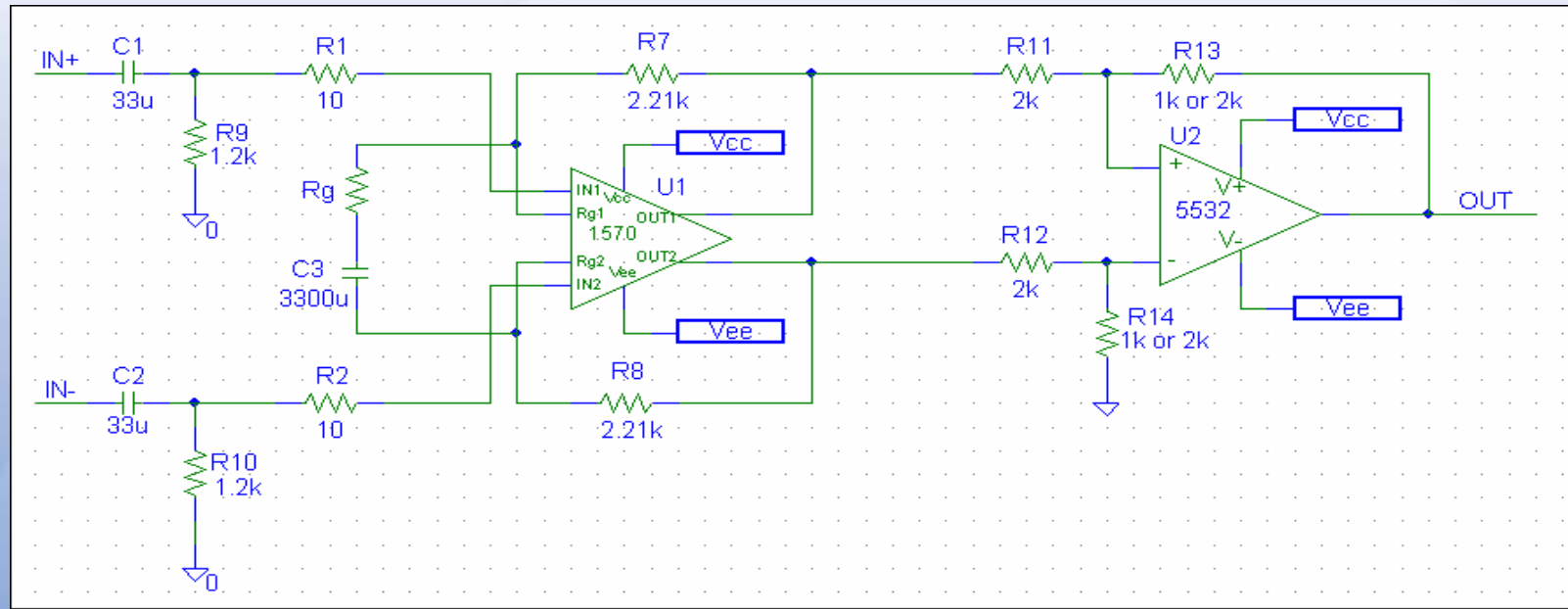
# Converting Differential Output to Single-Ended




- The traditional 4-resistor differential amplifier works fine
- At low gains, the noise of this stage can become important
- Resistor matching controls the CMRR
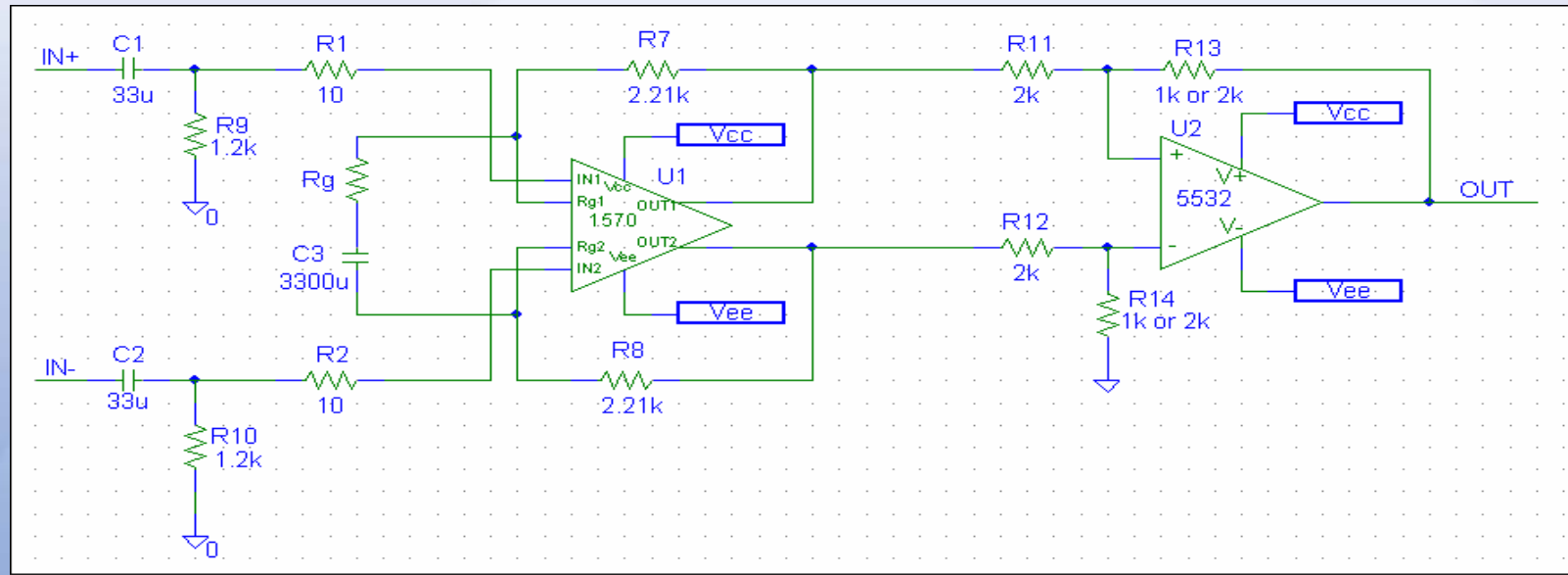
# Differential to Single-Ended Conversion



- What should the gain of the diff amp be?
- If  $G=1$ , we leave headroom on the table
- If  $G=.5$ , we take advantage of all of the swing capability of the differential output
- For the case of  $G=.5$ , the front end gain is always 6 db higher
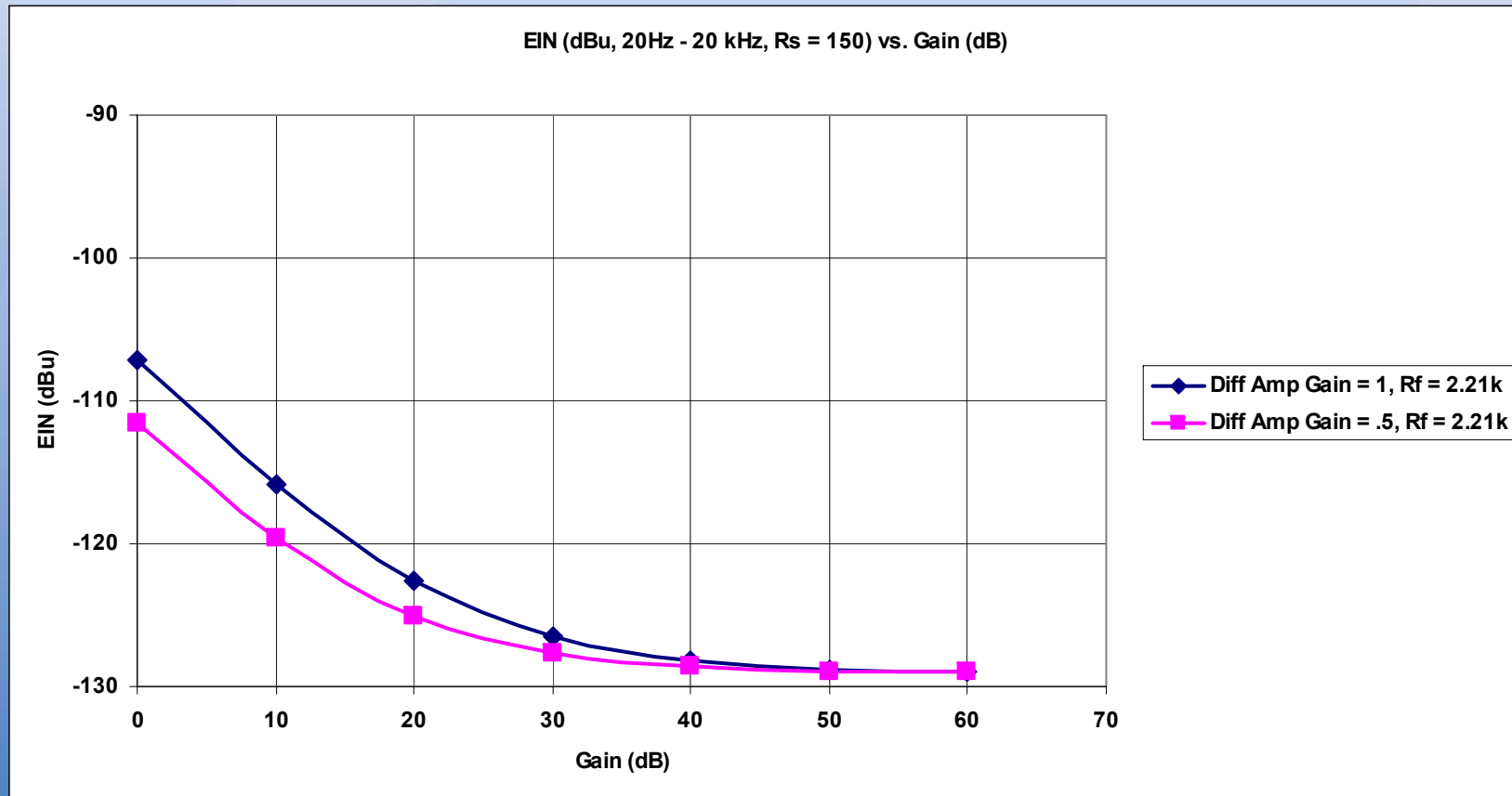
# 1570 + Differential Amplifier Noise vs. Gain Performance



## Conclusions

- Microphone preamplifiers with a wide gain range controlled by a single resistance involve tradeoffs between low-gain noise and high-gain distortion performance
- The current-feedback instrumentation amplifier is capable of good performance at both extremes
- An integrated approach can provide excellent performance in very small PCB area at moderate cost

# Amplifier References

- David Birt, “Electronically Balanced Analogue-Line Interfaces,”  
Proceedings of the Institute of Acoustics, Vol. 12, Part 8 (1990)**
- Graeme John Cohen, “Double Balanced Microphone Amplifier”, 1984  
Audio Engineering Society Australian Regional Convention, Preprint  
Number 2106, September 1984**
- Graeme John Cohen, “Microphone Amplifier History and Design”,  
presented at the Audio Engineering Society Adelaide Section, August,  
2006**
- Fred Floru, “An Improved Microphone Preamplifier Integrated Circuit”,  
2001 Audio Engineering Society 16<sup>th</sup> UK Conference on Silicon For  
Audio**
- Scott Wurcer, “A Programmable Instrumentation Amplifier for 12-Bit  
Sources”, IEEE Journal of Solid-State Circuits, Volume SC-17, Number  
6, December, 1982**



# Acknowledgements

**Thanks to Steve Green for preparing the  
“Support Circuitry” section.**

**Thanks to Greg Benulis, Rosalfonso Bortoni,  
Fred Floru, Bob Moses, and Les Tyler for their  
assistance in the preparation of this tutorial**



*Questions ?*

**THAT** Corporation