


### One Cycle Control µPFC Circuit Featuring the IR1150S IC


**Operating Conditions:**

<b>Input</b>		<b>Output</b>	
Min Input Voltage:	140 V	Switching Frequency:	50 kHz
Max Input Voltage:	240 V	Hold-up Time:	20 ms
Input AC Frequency:	50 Hz	Choke Ripple Current:	20 %
Start-up Time:	50 ms		
Target Efficiency:	92 %		
		Output Power:	4000 W
		Output Voltage:	360 V
		Output Voltage (min):	286 V
		Output Cap Tolerance:	20 %
		OVP Threshold:	400 V


**Calculation Result:**

<b>Output Conditions</b>		<b>Component Values</b>		
		Ref Des	Std Value	Calc Value
Max Input Power	4,348 W	Cin	3.3 $\mu$ F	2.35 $\mu$ F
Input RMS Current	31.06 A	Lbst	220 $\mu$ H	203 $\mu$ H
Input Peak Current	43.92 A	Cout	4.7 mF	4,184 $\mu$ F
Input Average Current	27.96 A	Output Voltage Rset	20 kOhm	19.8 kOhm
Input Pk Voltage (min)	198 V	Output OVP Rset	19.1 kOhm	19.0 kOhm
Duty Cycle - low line	0.45	Current Sense Res	Rs	0.020 Ohm
Ripple Current	8.78 A	Zero Capacitor	Cz	330 nF
Peak Inductor Current	48.31 A	Gain Resistor	Rgm	4.87 kOhm
V Current Sense	1.00 V	Pole Capacitor	Cp	3.9 nF
Peak Current Limit	50.73 A	Current Sense Filter Capacitor	Csf	1 nF
Input Pk Ovld Current	50.73 A	Current Sense Filter Resistor	Rsf	100 Ohm
<b>Power Distribution</b>		Timing Resistor	Rf	165 kOhm
Power Dissipation Rfb	62.4 mW	Rfb1, Rfb2, Rovp1 and Rovp2 are 499 kOhms each		
Power Diss Rovp	62.3 mW			
Power Rs	19.01 W			

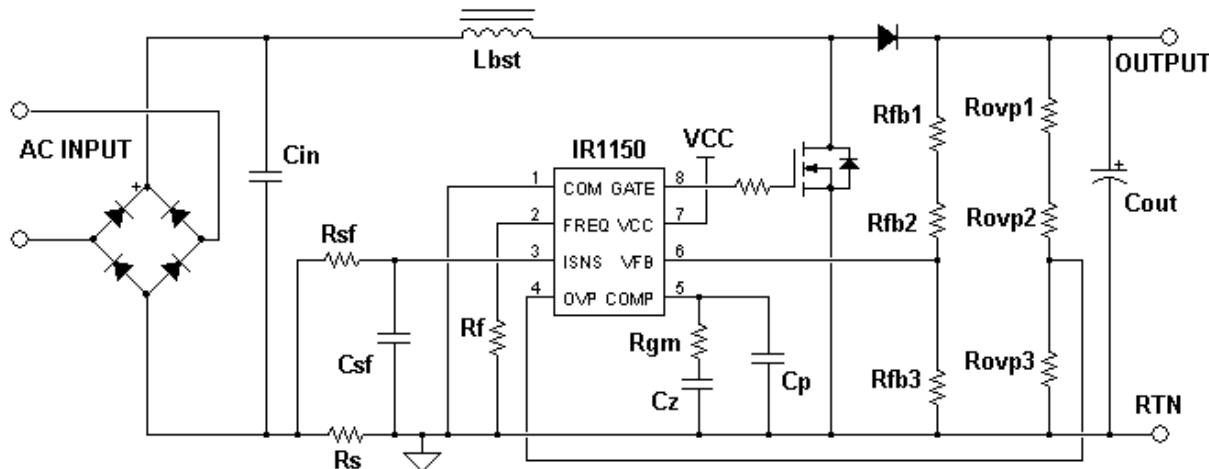


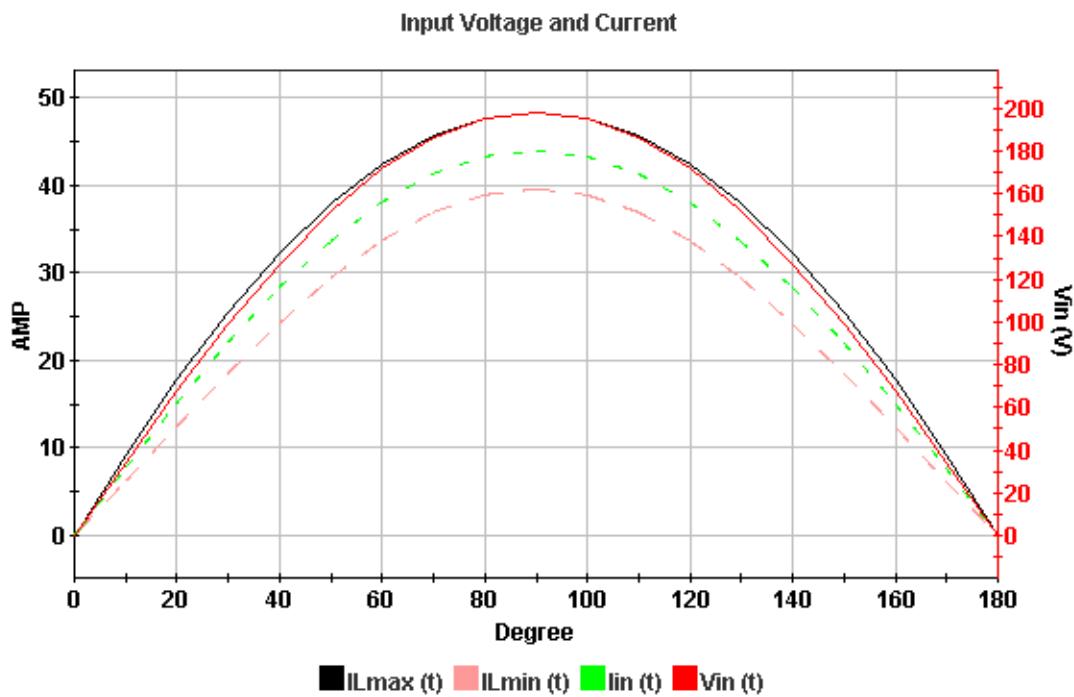


Graph 1: Input voltage and current relationship for this IR1150 power factor correction circuit.

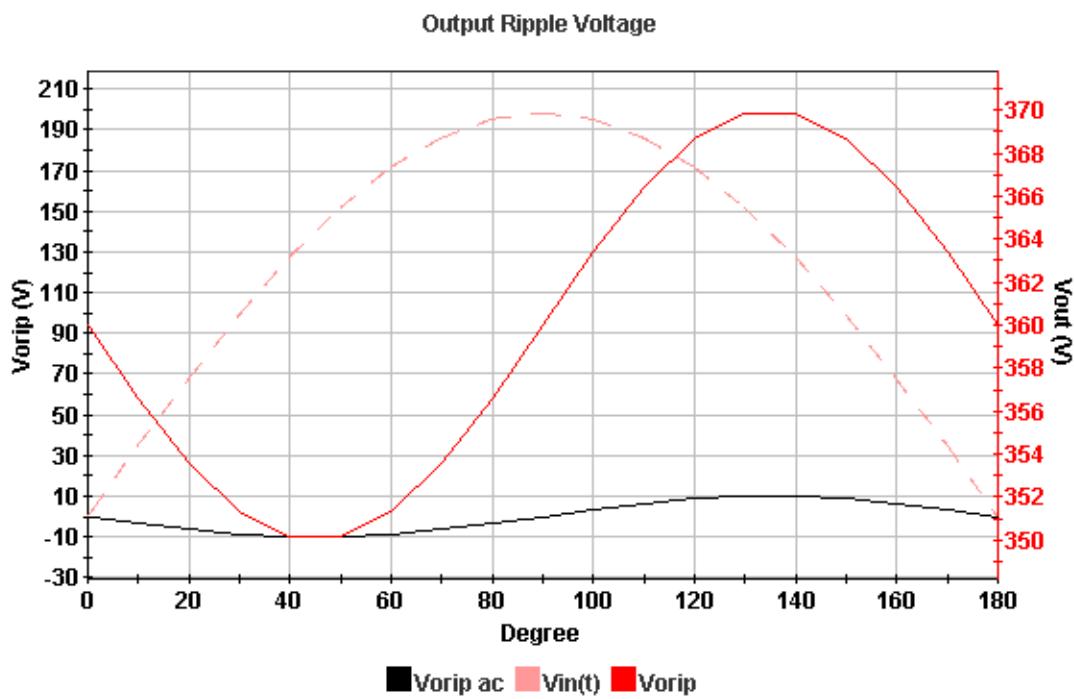


Graph 2: Output voltage ripple amplitude relative to the AC input voltage for this design.

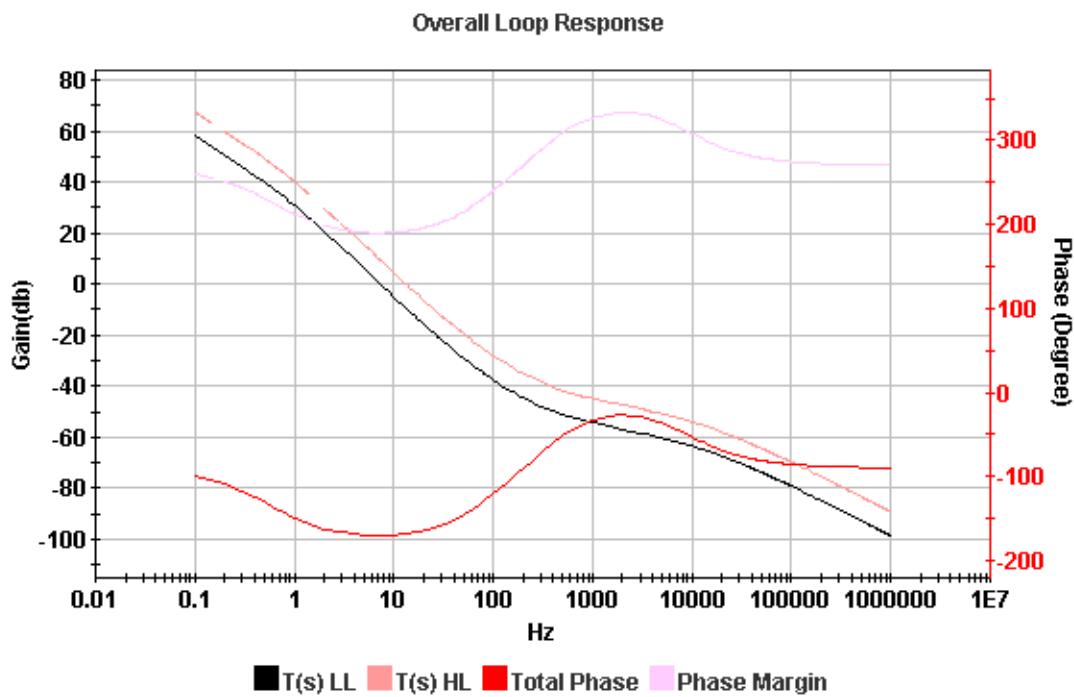

Graph 3: This is the overall feedback loop response of the power factor correction circuit showing phase and gain.

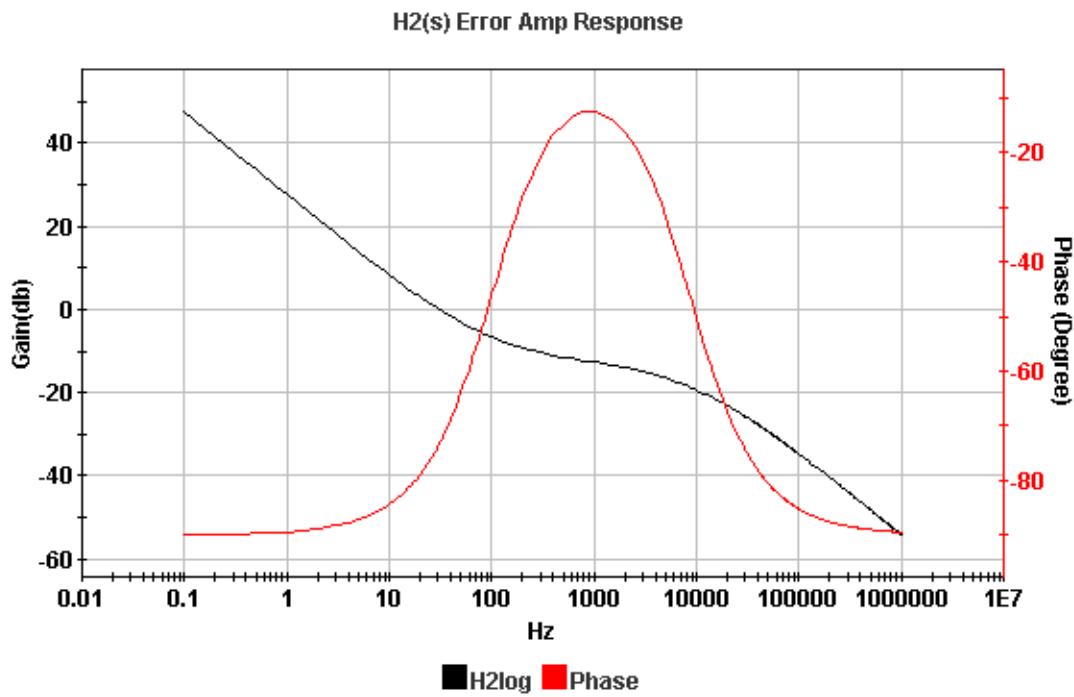

Graph 4: This is the error amplifier response of the power factor correction circuit showing phase and gain.

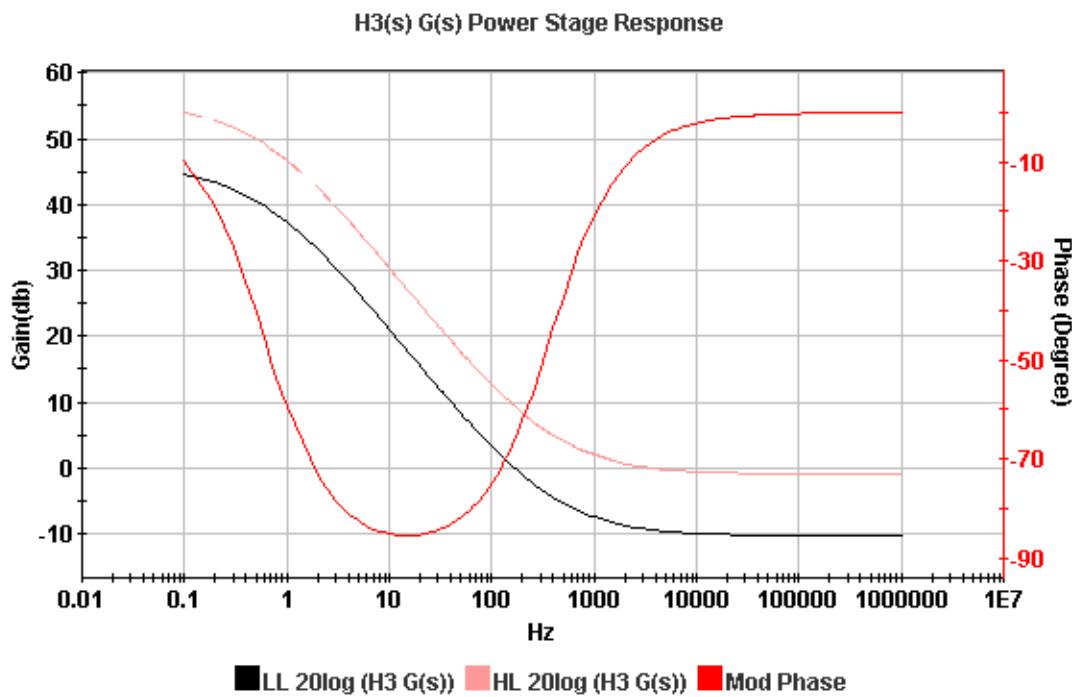

Graph 5: This is the power stage response of the power factor correction circuit showing phase and gain.

Please click [here](#) to send us your comments or suggestions.

[myPowerHome](#)