

Crystal Filter Design with Small Computers

Thinking of making a crystal filter? This computer program will provide excellent results. It even allows calculations for filters that provide large bandwidths.

By Dr. Ulrich L. Rohde,* DJ2LR

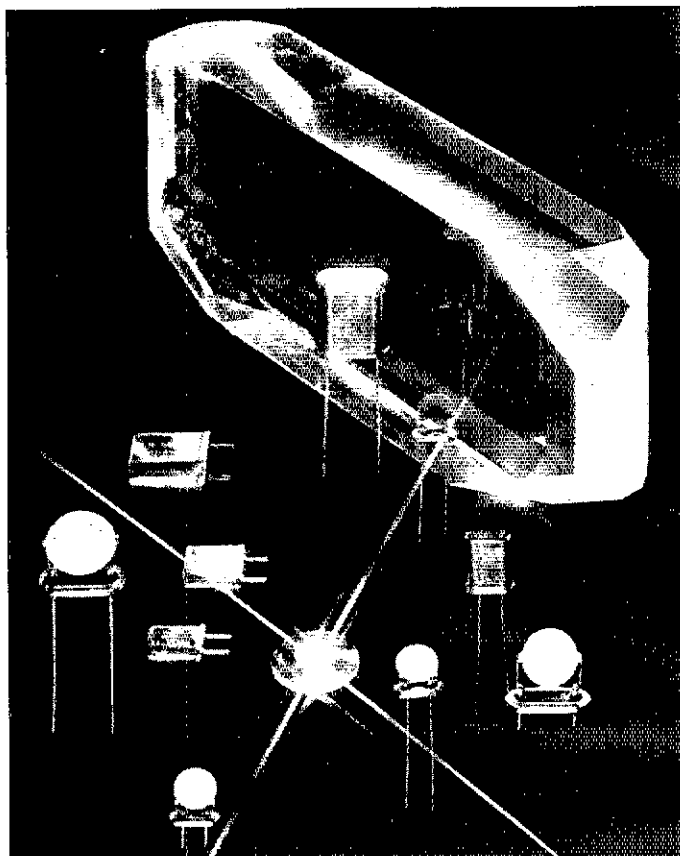


photo courtesy M-Tron Industries, Inc.

Crystal filters are being used where superior selectivity is required and the specific bandwidth may be anywhere from a few hundred hertz up to 100 kHz. Crystal filters, as generally offered, are of the Chebyshev design. These filters, however, frequently exhibit bad ringing and group-delay distortion. A natural question at this point would be, "Is there an alternative and, if so, what is it?" In answer, this article provides information on the use of a small BASIC computer to aid in building more suitable crystal filters. The actual program is shown, along with computer results. In addition, attenuation graphs are provided to illustrate the effects of additional filter poles. The program is written in such a way that it allows the calculations of large-bandwidth crystal filters. Such information has not been available previously.

Standard Filter Design

A half-lattice crystal filter with one crystal appears in Fig. 1. Filters of this type have been designed into receiver circuits, but with rather poor results. By tuning the neutralizing capacitor, C1, a pole can be moved in order to influence the bandwidth and the notch depth.

Fig. 2A presents the attenuation perfor-

mance of a single-crystal 300-kHz filter. The notch at the right is set by the neutralizing capacitor. Attenuation in excess of 100 dB is possible.

The close-in performance of the single-crystal filter can be seen in Fig. 2B while Fig. 2C is a graph of the overall performance. If the pole is removed far enough, as in Fig. 2C, the selectivity improves greatly on the left side and the filter action becomes symmetrical. In reality, though, such filters do not offer outstanding performance. Consequently, they are seldom used today.

A typical ssb filter has a total of six crystals. How a filter of this type behaves is indicated by Fig. 2D. In practice, the ultimate rejection would be limited to 120 dB.

Crystal filters are found frequently in up-conversion receivers like the DJ2LR HF-1030. Fig. 2E shows the performance

of a typical circuit of this nature. If the filter is improperly tuned, a performance similar to that in Fig. 2F can be expected. At times, such an adjustment may be useful to suppress a mixing product or an image if a 60-dB attenuation on the other side is sufficient.

In practice, we should evaluate those performances when we are working with a crystal filter design and then calculate the parameters of the particular crystal filter in which we are interested. This can be done with the aid of the program.

Table 1 contains a list of program information covering a wide variety of possible bandwidths for a universal crystal filter. The basic configuration for such a crystal filter appears in Fig. 3. It consists of three tuned transformers constructed with small pot cores suitable for high-frequency application. A pot core recommended for this application is Siemens' type 4.6 × 4.1 (mm), no. B65495-K0005-A017 for lower-frequency use. For the region around 10 MHz, the core material K65495-K00016-A001 is satisfactory.¹

Computer-Aided Design of a Crystal Filter

Lines 1 through 20 in the program of

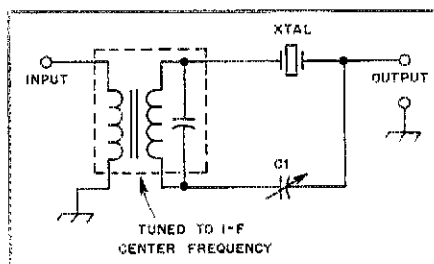


Fig. 1 — A half-lattice crystal filter circuit.

*52 Hillcrest Dr., Upper Saddle River, NJ 07458

¹Details on Siemens' pot cores are found in the Siemens book, *Ferrites Soft-Magnetic Material Data Book 1979/80*, p. 98. This book is available from the Siemens Corporation, 186 Wood Ave. S., Iselin, NJ 08830, tel. 201-494-1000.

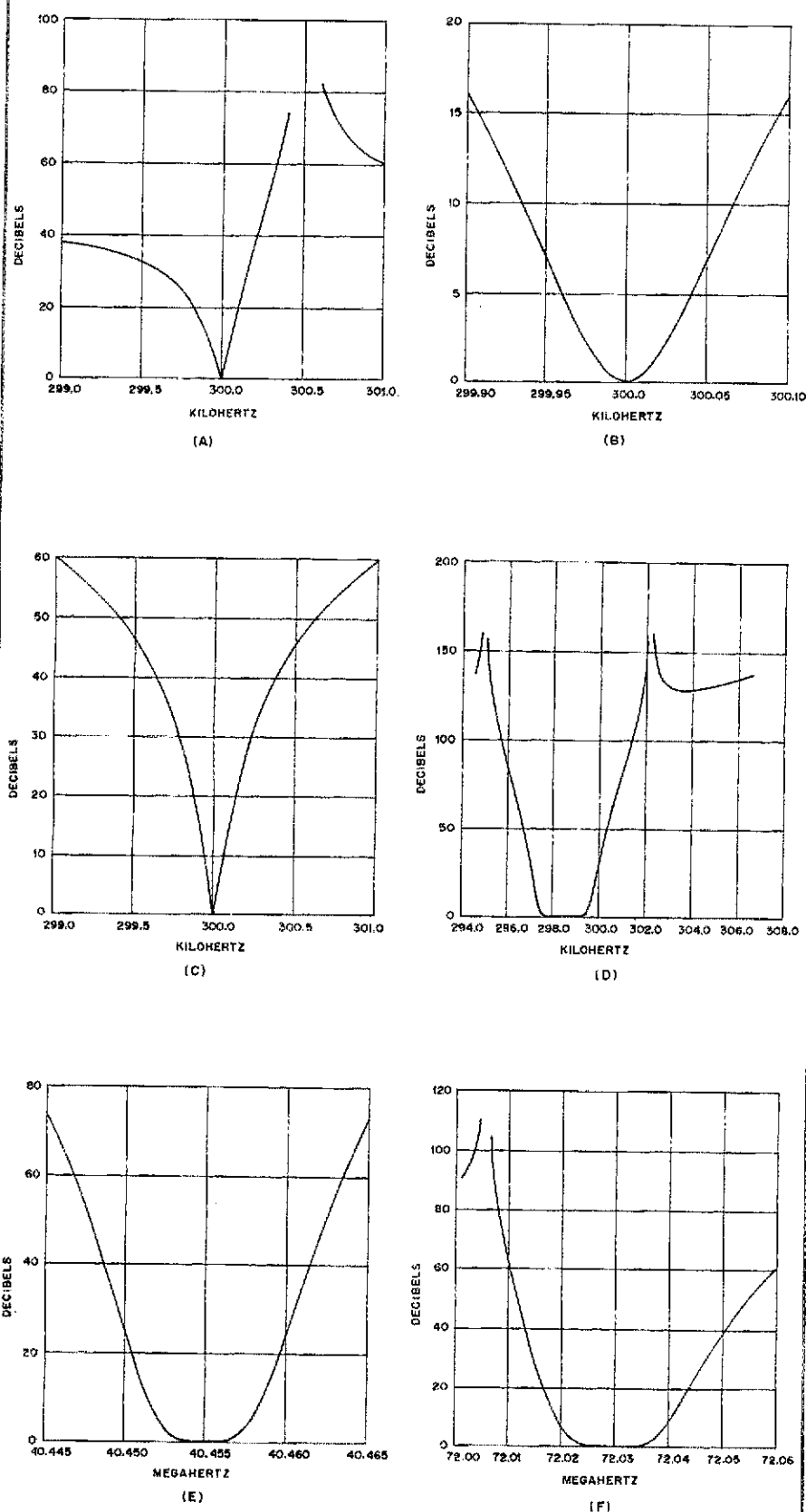


Fig. 2 — Crystal filter responses. The amplitude response of the crystal filter in Fig. 1 with C1 set to generate a pole 500-Hz above center frequency is shown at A. The close-in performance of this same filter is indicated at B, while the overall response is represented in C. In the latter case, the pole is tuned considerably away from the center frequency. At D the amplitude response of a six-crystal single-sideband filter at 300 kHz. A Chebyshev six-crystal filter at 40.455 MHz is represented by the curve at E. The curve at F is for the amplitude response of a 72.03-MHz crystal filter with an attenuation pole on the left side.

Table 1 activate the user-definable keys available on the Tektronix 4051/52 computers. After initiation of the program, it will start on line 100 and ask whether the results should be displayed on the screen or on the printer. Most of the hobby computers on which this program will run have printer-definable ports that have to be addressed. The address to which the information is routed is V5.

In line 200, the computer will ask the center frequency. In line 230, it will ask the bandwidth while in line 250 it will request the crystal inductance.

Fig. 4 shows the inductance in relation to a function of frequency for a crystal that can be manufactured. The highest possible inductance for L1 should always be selected without sacrificing performance in a manner that would lead to spurious response. A minimum Q of 80,000 (100,000 is better) for the crystal is desired for narrow bandwidths. If you start building a crystal filter and order the crystal from a company like Bliley, a firm experienced in crystal and filter manufacturing, you will do well to have them verify these two parameters.

At line 260, the computer will ask you for the capacitance of the holder. You can generally presume that the HC-18/U holder is rated at 1.5 pF, with the larger HC-6/U unit having a capacitance of 6 pF.

On line 280, you will finally be asked what filter response you desire. Various types of responses are available. If selectivity is the prime object, a Chebyshev filter should be chosen. Where constant group delay and therefore low fm distortion are required, a flat delay is important. For perfect pulse response, either the linear phase filter or the Gaussian response should be chosen.

Amateurs who desire additional general information on filter theory will find Zverev's *Handbook of Filter Synthesis*, published by John Wiley and Sons, particularly useful. The "look-up" tables I refer to in this computer program are taken from his book. In this publication, Zverev briefly elaborates on the difficulties in building crystal filters that have a large bandwidth in comparison to the center frequency. A typical problem, for instance, is one concerning a 10- to 20-kHz-bandwidth filter designed for 10 MHz. Because Zverev seems to avoid giving clear design rules for such filter circuitry, additional guidelines are needed. This is where the computer program fills in, for it incorporates the necessary "spreading inductance" which will cure the problem.

Another good source of general filter information is the ITT book *Reference Data for Engineers*, fifth edition, chapters 7, 8 and 9. Inasmuch as many readers may be less interested in precise theory, preferring just to build some filters, none of the mathematics is repeated. Fig. 5 is a graph

with the different response curves shown in comparison with each other.

Computerized Tuned-Circuit Information

After you have responded to the query in the filter program concerning the type of filter you wish to have, the computer will use the "look-up" table as provided by line 890 and 1290. The aim of this part of the program is to calculate the component values of lines 380 through 580. You can delete lines 140 and 590, a screen-erase command for the Tektronix computer. Lines 600 through 840 transfer the characteristic values to the printer or the screen. Lines 600 to 650 print, respectively, the header, the center frequency, the bandwidth, the inductance, the internal impedance and the external reference capacitance. Other information includes the input impedance that is printed in line 660 with the required inductance, the capacitance in line 700, and the output values in line 670 together with line 710.

Lines 680 and 690 determine the tuned circuit for the middle of the range. In order to obtain the right crystal from the manufacturer, the four frequencies required are printed on lines 720 through 750. A six-digit accuracy is desirable when these crystals are ordered. Line 800 gives the reference input voltage for a second computer program to determine the actual band-pass characteristic. Lines 820 through line 840 verify that all tuned circuits are on the center frequency.

When aligning the filters, do realize that any mistuning of the input stages will result in poles as shown in Figs. 2A, 2D and 2F. In order to get sharper skirts at times, it is desirable to use poles like these. They can always be determined experimentally. The procedure is to set all three tuned circuits precisely on the center frequency with the crystals inserted.

For those amateurs who do not have a computer, some calculations of interest also are shown in the tables. Table 2 shows the Butterworth, Chebyshev, flat-delay crystal filter, linear-phase crystal filter and Gaussian response filter for a 250-Hz bandwidth. The Chebyshev response should really be avoided because of ringing. The optimum choice probably is the flat-delay or linear-phase approach.

As we take a look at the filters of Table 2, we see that 9 MHz has been selected for the center frequency with a 250-Hz bandwidth. The present inductance is 200 mH. All other values are self-explanatory.

My calculations for single-sideband filters for both upper and lower sidebands are shown in Table 3. For perfect low distortion, the flat-delay versions should be preferred.

In cases where further selectivity is required, two of those crystal filters can be cascaded either directly with a 1-dB resistive matching pad in between or a transistor stage with 3 to 4 dB gain and heavy feedback. Finally, for those in-

Table 1

Wide Bandwidth Filter Design Program

```

1 GO TO 100
4 RUN 280
8 PAGE
9 GO TO 200
20 LIST 1290, 2000
100 INIT
110 SET KEY
120 DIM C(13)
130 CS=""
140 PAGE
150 PRINT "*** CRYSTAL FILTER PROGRAM *** J__J__"
160 REM COPY-RIGHT RESERVED
170 REM ULRICH L. ROHDE, PH.D., SC.D.
180 PRINT "DO YOU WANT OUTPUT AT SCREEN (32) OR PRINTER (41)?"
190 INPUT V5
200 PRINT "WHICH CENTER FREQUENCY DO YOU WANT?"
210 INPUT F0
220 PRINT "WHICH BANDWIDTH DO YOU WANT?"
230 INPUT B0
240 PRINT "WHICH INDUCTANCE DO YOU HAVE?"
250 INPUT L
260 PRINT "WHAT HOLDER CAPACITANCE DO YOU HAVE?"
270 INPUT C(9)
280 PRINT "WHICH FILTER TYPE DO YOU WANT, BUTTERWORTH,"
290 PRINT "CHEBYSHEV, FLAT DELAY, LIN. PHASE, GAUSS RESP. (B,C,F,L,G)?"
300 INPUT AS
310 IF AS="" THEN 1290
320 IF AS="B" THEN 890
330 IF AS="C" THEN 970
340 IF AS="F" THEN 1050
350 IF AS="L" THEN 1130
360 IF AS="G" THEN 1210
370 RETURN
380 R0=PI*L*B0
390 C0=1/(2*B0*PI*F0*L)
400 Q0=150000*B0/F0
410 R1=R0*(K2+2+(1/Q1-1/Q0)*2)/(1/Q1-1/Q0)
420 R2=R0*(K2+2+(1/Q4-1/Q0)*2)/(1/Q4-1/Q0)
430 C(1)=C0*K2/(K2+2+(1/Q1-1/Q0)*2)-2*C(9)
440 C(8)=C(1)+2*C(9)
450 GO TO 1300
460 C(2)=C0*K2/(K2+2+(1/Q4-1/Q0)*2)-2*C(9)
470 C(10)=C(2)+2*C(9)
480 GO TO 1340
490 C(11)=C0/K2-4*C(9)
500 C(3)=1/(2*PI*F0*(L1+L2))+C(11)
510 F1=F0-B0/2*(K2+K1)
520 F2=F0-B0/2*(K2-K1)
530 F3=F0-B0/2*(K2+K3)
540 F4=F0-B0/2*(K2-K3)
550 C(4)=1/(4*PI*F1*L1)
560 C(5)=1/(4*PI*F2*L2)
570 C(6)=1/(4*PI*F3*L3)
580 C(7)=1/(4*PI*F4*L4)
590 PAGE
600 PRINT @V5:FS;"J__"
610 PRINT @V5:F0="";F0
620 PRINT @V5:B0="";B0
630 PRINT @V5:L="";L
640 PRINT @V5:R0="";R0
650 PRINT @V5:C0="";C0
660 PRINT @V5:RIN="";R1
670 PRINT @V5:ROUT="";R2
680 PRINT @V5:CK="";C(3)
690 PRINT @V5:LK="";L1
700 PRINT @V5:CS;L1;"GIN="";C(12)
710 PRINT @V5:DS;L2;"GOUT="";C(13)
720 PRINT @V5:F1="";F1
730 PRINT @V5:F2="";F2
740 PRINT @V5:F3="";F3
750 PRINT @V5:F4="";F4
760 PRINT @V5:CS1="";C(4)
770 PRINT @V5:CS2="";C(5)
780 PRINT @V5:CS3="";C(6)
790 PRINT @V5:CS4="";C(7)
800 V0=(R1+R2)/R1
810 PRINT @V5:V0="";V0
820 W0=1/(2*PI*SQR(L1*(C(12)+C(1))))
830 W1=1/(2*PI*SQR(L2*(C(13)+C(2))))
840 PRINT @V5:"POLE FREQUENCIES ARE ";W0;" ";W1

```

```

850 CALL "WAIT",1
860 PRINT @V5:"J _J _J _"
870 GO TO 280
880 END
890 Q0 = 100
900 FS = "BUTTERWORTH RESPONSE 4TH ORDER CRYSTAL FILTERJ_"
910 Q1 = 1.0457
920 Q4 = 1.0457
930 K1 = 0.7369
940 K2 = 0.5413
950 K3 = 0.7369
960 GO TO 380
970 Q0 = 1000
980 FS = "CHEBYSHEV RESPONSE 4TH ORDER CRYSTAL FILTER 0.01DB RIPPLEJ_"
990 Q1 = 1.8258
1000 Q4 = 1.8258
1010 K1 = 0.6482
1020 K2 = 0.5446
1030 K3 = 0.6482
1040 GO TO 380
1050 Q0 = 1000
1060 FS = "MAXIMALLY FLAT DELAY 4TH ORDER CRYSTAL FILTERJ_"
1070 Q1 = 0.2334
1080 Q4 = 2.2404
1090 K1 = 2.5239
1100 K2 = 1.1725
1110 K3 = 0.6424
1120 GO TO 380
1130 Q = 1000
1140 FS = "LINEAR PHASE 4TH ORDER CRYSTAL FILTER 0.05DEG PHASE ERRORJ_"
1150 Q1 = 0.4934
1160 Q4 = 0.7182
1170 K1 = 1.632
1180 K2 = 0.7181
1190 K3 = 0.7391
1200 GO TO 380
1210 Q0 = 1000
1220 FS = "GAUSSIAN RESPONSE 4TH ORDER CRYSTAL FILTERJ_"
1230 Q1 = 0.2747
1240 Q4 = 0.4083
1250 K1 = 2.2792
1260 K2 = 0.7553
1270 K3 = 0.9896
1280 GO TO 380
1290 END
1300 CS = "TUNED INPUT L1 ="
1310 C(12) = 1.0E-11*1.0E+8/F0
1320 L1 = 1/((2*PI*F0)*2*(C(12)+C(1)))
1330 GO TO 460
1340 DS = "TUNED INPUT L2 ="
1350 C(13) = 1.0E-11*1.0E+8/F0
1360 L2 = 1/((2*PI*F0)*2*(C(13)+C(2)))
1370 GO TO 490

```

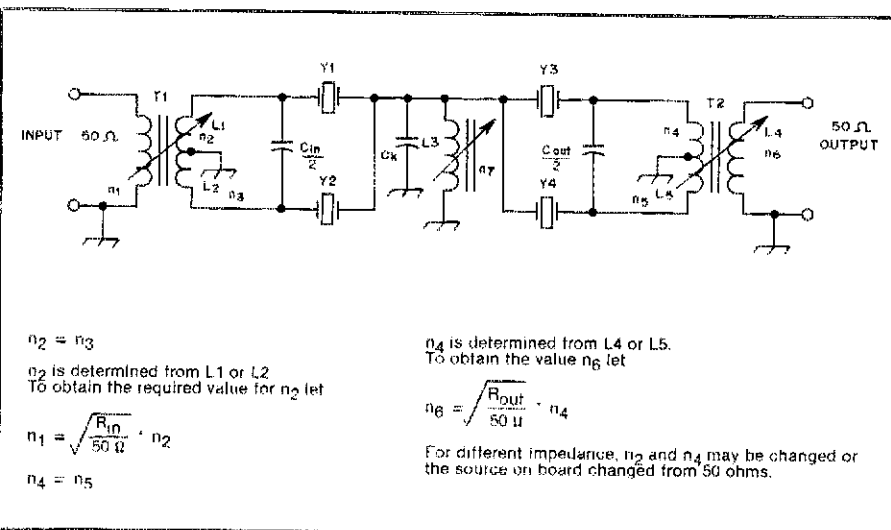


Fig. 3 — A four-crystal filter circuit. The Input and output impedances are determined by the turns ratio of the input and output transformers. Also shown are the calculations for this filter.

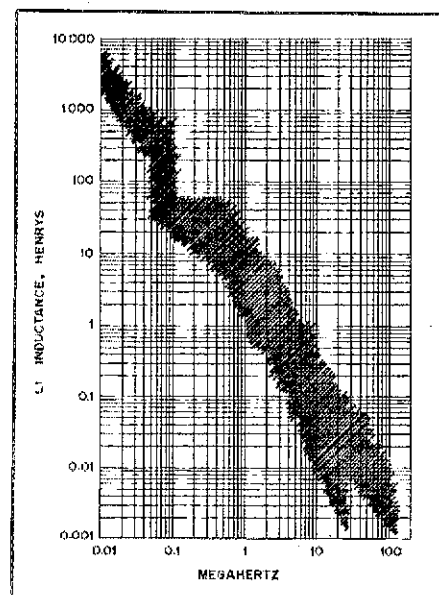


Fig. 4 — This graph shows the relationship of inductance and frequency for a particular crystal selected as a test example.

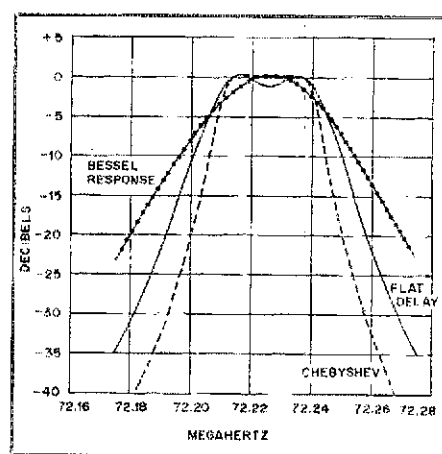


Fig. 5 — The Bessel, flat-delay and Chebyshev responses are represented by this composite graph. The Chebyshev response provides the steepest skirts, while the Bessel response has the poorest amplitude curve.

interested in constructing a double-conversion receiver, the parameters for a 41-MHz crystal filter are provided in Table 4. Table 5 is a Gaussian response filter designed for use in a radar receiver.

In Summary

This short presentation on how to design and build crystal filters with the aid of a small computer should encourage experimentation with various types of filters. In the past, wideband filters like the 72.225-MHz, 31-kHz bandwidth filter of Table 5 required special computer programs. Now this unique program can solve the design problem for an extremely wide bandwidth range.

Table 2

Calculations for Some Large-Bandwidth Filters

| | BUTTERWORTH RESPONSE FOURTH ORDER CRYSTAL FILTER | CHEBYSHEV-RESPONSE FOURTH ORDER CRYSTAL FILTER (0.01dB RIPPLE) | MAXIMALLY FLAT DELAY FOURTH-ORDER FILTER | LINEAR PHASE FOURTH ORDER ORDER CRYSTAL (0.05° PHASE ERROR) | GAUSSIAN RESPONSE FOURTH ORDER CRYSTAL FILTER |
|-------------|--|---|--|--|---|
| F0 = | 90000000 | 90000000 | 90000000 | 90000000 | 90000000 |
| B0 = | 250 | 250 | 250 | 250 | 250 |
| L = | 0.2 | 0.2 | 0.2 | 0.2 | 0.2 |
| R0 = | 157.079632679 | 157.079632679 | 157.079632679 | 157.079632679 | 157.079632679 |
| C0 = | 1.125790929E-10 | 1.125790929E-10 | 1.125790929E-10 | 1.125790929E-10 | 1.125790929E-10 |
| RIN = | 176.770073394 | 199.739282207 | 688.699716017 | 325.996645717 | 560.476789007 |
| ROUT = | 176.770073394 | 199.739282207 | 1078.92346935 | 251.304525198 | 387.579899958 |
| CK = | 3.856888033E-10 | 4.655256668E-10 | 2.055712309E-10 | 2.806860945E-10 | 2.581716487E-10 |
| LK = | 1.702249344E-6 | 1.180935302E-6 | 2.706242448E-6 | 2.407155723E-6 | 2.716479143E-6 |
| TUNED INPUT | | | | | |
| L1 = | 1.702249344E-6 | 1.180935302E-6 | 2.706242448E-6 | 2.407155723E-6 | 2.716479143E-6 |
| CIN = | 1.111111111E-10 | 1.111111111E-10 | 1.111111111E-10 | 1.111111111E-10 | 1.111111111E-10 |
| L2 = | 1.702249344E-6 | 1.180935302E-6 | 1.553941872E-6 | 2.057891921E-6 | 2.527836771E-6 |
| COUT = | 1.111111111E-10 | 1.111111111E-10 | 1.111111111E-10 | 1.111111111E-10 | 1.111111111E-10 |
| F1 = | 8999840.225 | 8999850.9 | 8999537.95 | 8999706.2375 | 8999620.6875 |
| F2 = | 9000024.45 | 9000012.95 | 9000168.925 | 9000114.2375 | 9000190.4875 |
| F3 = | 8999840.225 | 8999850.9 | 8999773.1375 | 8999817.85 | 8999781.8875 |
| F4 = | 9000024.45 | 9000012.95 | 8999933.7375 | 9000002.625 | 9000029.2875 |
| CS1 = | 1.563654031E-15 | 1.563650322E-15 | 1.563759072E-15 | 1.563700591E-15 | 1.56373032E-15 |
| CS2 = | 1.563590017E-15 | 1.563594013E-15 | 1.563539819E-15 | 1.56355882E-15 | 1.563532327E-15 |
| CS3 = | 1.563654031E-15 | 1.563650322E-15 | 1.563677343E-15 | 1.563661806E-15 | 1.563674303E-15 |
| CS4 = | 1.563590017E-15 | 1.563594013E-15 | 1.563621537E-15 | 1.563597601E-15 | 1.563588337E-15 |
| V0 = | 2 | 2 | 2.5666094297 | 1.77088070844 | 1.69151819943 |
| POLE | | | | | |
| FREQUENCIES | 90000000 90000000 | 90000000 90000000 | 90000000 90000000 | 90000000 90000000 | 90000000 90000000 |

Table 3

Single-Sideband Filter Calculations

| | UPPER SIDEBAND CHEBYSHEV RESPONSE FOURTH ORDER CRYSTAL FILTER 0.01dB RIPPLE | UPPER SIDEBAND MAXIMALLY FLAT DELAY FOURTH ORDER CRYSTAL FILTER | LOWER SIDEBAND CHEBYSHEV RESPONSE FOURTH ORDER CRYSTAL FILTER 0.01dB RIPPLE | LOWER SIDEBAND MAXIMALLY FLAT DELAY FOURTH ORDER CRYSTAL FILTER |
|-------------|---|---|---|--|
| F0 = | 90021.00 | 90021.00 | 89979.00 | 89979.00 |
| B0 = | 2100 | 2100 | 2100 | 2100 |
| L = | 0.03 | 0.03 | 0.03 | 0.03 |
| R0 = | 197.920337176 | 197.920337176 | 197.920337176 | 197.920337176 |
| C0 = | 8.932764334E-11 | 8.932764334E-11 | 8.93693393E-11 | 8.93693393E-11 |
| RIN = | 215.822217917 | 906.264311969 | 215.821952659 | 906.266750613 |
| ROUT = | 215.822217917 | 733.98082547 | 215.821952659 | 733.982678696 |
| CK = | 3.520472927E-10 | 1.836453586E-10 | 3.522137182E-10 | 1.837352494E-10 |
| LK = | 1.611014457E-6 | 2.754931668E-6 | 1.611772269E-6 | 2.756184362E-6 |
| TUNED INPUT | | | | |
| L1 = | 1.611014457E-6 | 2.754931668E-6 | 1.611772269E-6 | 2.756184362E-6 |
| CIN = | 1.110851912E-10 | 1.110851912E-10 | 1.111370431E-10 | 1.111370431E-10 |
| L2 = | 1.611014457E-6 | 1.779138943E-6 | 1.611772269E-6 | 1.779960146E-6 |
| COUT = | 1.110851912E-10 | 1.110851912E-10 | 1.111370431E-10 | 1.111370431E-10 |
| F1 = | 9000847.56 | 8998218.78 | 8996647.56 | 8994018.78 |
| F2 = | 9002208.78 | 9003518.97 | 8998008.78 | 8999318.97 |
| F3 = | 9000847.56 | 9000194.355 | 8996647.56 | 8995994.355 |
| F4 = | 9002208.78 | 9001543.395 | 8998008.78 | 8997343.395 |
| CS1 = | 1.042202704E-14 | 1.042811741E-14 | 1.043176016E-14 | 1.043785906E-14 |
| CS2 = | 1.041887546E-14 | 1.041584337E-14 | 1.042860416E-14 | 1.042556783E-14 |
| CS3 = | 1.042202704E-14 | 1.042353989E-14 | 1.043176016E-14 | 1.043327513E-14 |
| CS4 = | 1.041887546E-14 | 1.042041582E-14 | 1.042860416E-14 | 1.043014668E-14 |
| V0 = | 2 | 1.80989708607 | 2 | 1.80987488308 |
| POLE | | | | |
| FREQUENCIES | 9002100 9002100 | 9002100 9002100 | 8997900 8997900 | 8997900 8997900 |

Table 4

Calculations for a Double-Conversion Receiver 41-MHz Crystal Filter

| CHEBYSHEV RESPONSE FOURTH ORDER CRYSTAL FILTER 0.01dB RIPPLE | CHEBYSHEV RESPONSE FOURTH ORDER CRYSTAL FILTER 0.01dB RIPPLE | CHEBYSHEV RESPONSE FOURTH ORDER CRYSTAL FILTER 0.01dB RIPPLE |
|---|---|---|
| F0 = 4.0455E + 7 | 4.1E + 7 | 7.0455E + 7 |
| B0 = 7000 | 7000 | 7000 |
| L = 0.01 | 0.01 | 0.01 |
| R0 = 219.911485751 | 219.911485751 | 219.911485751 |
| C0 = 1.78895746E-11 | 1.769177415E-11 | 1.027212746E-11 |
| RIN = 240.069542975 | 240.08611077 | 241.401505946 |
| ROUT = 240.069542975 | 240.08611077 | 241.401505946 |
| CK = 6.609534562E-11 | 6.511358011E-11 | 3.465894436E-11 |
| LK = 3.943635932E-7 | 3.893569691E-7 | 2.341082409E-7 |
| TUNED INPUT | | |
| L1 = 3.943635932E-7 | 3.893569691E-7 | 2.341082409E-7 |
| CIN = 2.471882338E-11 | 2.43902439E-11 | 1.419345682E-11 |
| L2 = 3.943635932E-7 | 3.893569691E-7 | 2.341082409E-7 |
| COUT = 2.471882338E-11 | 2.43902439E-11 | 1.419345682E-11 |
| F1 = 4.04508252E + 7 | 4.09958252E + 7 | 7.04508252E + 7 |
| F2 = 4.04553626E + 7 | 4.10003626E + 7 | 7.04553626E + 7 |
| F3 = 4.04508252E + 7 | 4.09958252E + 7 | 7.04508252E + 7 |
| F4 = 4.04533626E + 7 | 4.10003626E + 7 | 7.04553626E + 7 |
| CS1 = 1.548051812E-15 | 1.507165686E-15 | 5.10349971E-16 |
| CS2 = 1.547704578E-15 | 1.506832117E-15 | 5.10284239E-16 |
| CS3 = 1.548051812E-15 | 1.507165686E-15 | 5.10349971E-16 |
| CS4 = 1.547704578E-15 | 1.506832117E-15 | 5.10284239E-16 |
| V0 = 2 | 2 | 2 |
| POLE | | |
| FREQUENCIES 4.0455E + 7 | 4.1E + 7 | 7.0455E + 7 |
| 4.0455E + 7 | 4.1E + 7 | 7.0455E + 7 |

Table 5

Calculations for a 31-kHz Bandwidth Filter

| GAUSSIAN RESPONSE FOURTH-ORDER CRYSTAL FILTER | |
|---|--|
| F0 = 7.2225E + 7 | |
| B0 = 31000 | |
| L = 0.013 | |
| R0 = 1266.0618394 | |
| C0 = 1.740514567E-12 | |
| RIN = 4788.47944845 | |
| ROUT = 3377.92904618 | |
| CK = 7.245912256E-12 | |
| LK = 4.438005914E-7 | |
| TUNED INPUT | |
| L1 = 4.438005914E-7 | |
| CIN = 1.384562132E-11 | |
| L2 = 4.39519567E-7 | |
| COUT = 1.384562132E-11 | |
| F1 = 7.217796525E + 7 | |
| F2 = 7.224862045E + 7 | |
| F3 = 7.219795405E + 7 | |
| F4 = 7.222863165E + 7 | |
| CS1 = 3.740138126E-16 | |
| CS2 = 3.732826402E-16 | |
| CS3 = 3.738067416E-16 | |
| CS4 = 3.734892759E-16 | |
| V0 = 1.705428327 | |
| POLE | |
| FREQUENCIES 7.2225E + 7 | |
| 7.2225E + 7 | |

Strays



John Schmale, K2IZ, N.Y.C./Long Island SCM, towers behind members of the Hall of Science Amateur Radio Club (Queens, New York) after presenting Public Service Commendations to many of them for their dedicated efforts during the recent Italian earthquake disaster. Club members received, relayed, answered or directed more than 1000 messages during the around-the-clock operation that lasted nearly two weeks. (photo by Fred Kahn, WB2TBC)

FIRE AT SEA

□ Last October, the Dutch ship *Prinsendam* caught fire in the Gulf of Alaska, and 533 passengers and crew were forced to abandon ship. Through poor sea conditions, people were lifted by helicopter from their lifeboats to the rescue ships. Alaskan Amateur Radio operators monitoring the situation quickly realized

that their services would be needed. Health-and-welfare nets were organized, and liaisons with the Red Cross, Alaska State Troopers and the Coast Guard were set up.

As the passengers and crew safely arrived on shore, the expected communications crunch developed. Shifting band conditions were a problem. Another

obstacle was passing traffic to foreign countries with whom the U.S. had no third-party agreement. As a result of outstanding cooperation among amateurs and their good on-the-air conduct, over 300 pieces of traffic were successfully passed. Fortunately, there were no fatalities during the rescue; the ship, however, sank. — Don Bush, KL7JFT



From left to right stand Jack van der Zee, radio officer of the *Prinsendam*, Jim Pfister, N6CF, and David Ring, N1EA, radio officers aboard the *Williamsport*, one of the tankers involved in the rescue effort. Jack maintained vital communications in the smoke-filled radio room despite melting cables and dwindling emergency power. Providing an essential link in the communications, Jim and David relayed positions and estimated time of arrivals and kept the distress frequency clear. (photo courtesy David J. Ring Sr.)