

Calculating Crystal Oscillator Circuit Values

INTRODUCTION

Some of the Wolfson Microelectronics chips feature a crystal oscillator circuit, designed to drive an external crystal. This saves cost over a separate crystal oscillator, but some care is needed in selecting the crystal type and the external load capacitors. This Application Note details how to calculate the required parameters.

PARAMETERS OF INTEREST

Crystal manufacturers specify the load capacitance their crystal requires. This is because the load capacitors form part of a tuned resonant circuit. They must be of the correct value so that the circuit oscillates at the correct frequency in the best possible manner i.e. with maximum Q.

A common mistake is to assume that this load capacitance figure refers to the value of the load capacitors C_{L1} and C_{L2} , as seen in Figure 1. It does not. It refers to the capacitance, C_L , which the crystal sees across its terminals, as shown in Figure 2. In a real circuit, it is effectively C_{L1} and C_{L2} in series, in parallel with the chip capacitance, which is C_{XTI} and C_{XTO} in series, as shown in Figure 1. (There is also some PCB track capacitance, but that should be too small to be concerned about.)

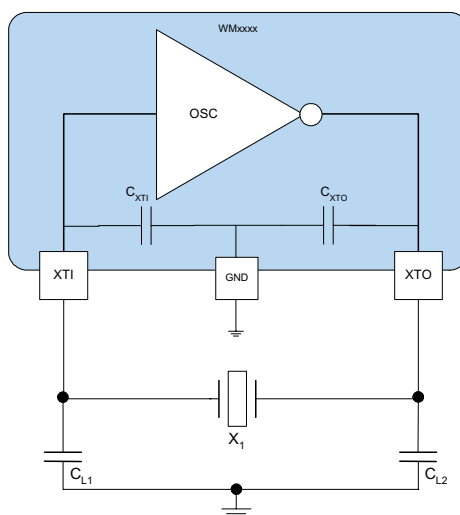


Figure 1 Oscillator Circuit

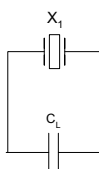


Figure 2 Crystal Specification

The oscillator circuit inside Wolfson chips is also designed to work with a range of load capacitances, so the crystal must be chosen to match this. **If the load capacitances are outside the correct range, the oscillator may take a long time to start up or may not oscillate stably.** Furthermore the circuit is designed to work with fundamental oscillation mode crystals, which are the most common in Wolfson frequencies, not harmonic mode ones.

CALCULATING THE VALUES

The Wolfson oscillator circuit works best with load capacitors in the range 15-22pF. The crystals most readily available favour the higher end of the range, so choose 22pF. The capacitors should have NP0 or COG dielectric.

Please check the datasheet for the XTI and XTO capacitances for your particular chip. For most Wolfson devices, $C_{XTI} = 5\text{pF}$ and $C_{XTO} = 3\text{pF}$.

$$C_L = \frac{C_{L1} \cdot C_{L2}}{C_{L1} + C_{L2}} + \frac{C_{XTI} \cdot C_{XTO}}{C_{XTI} + C_{XTO}}$$

Our recommendation is a crystal with load capacitance specification of ideally 15pF. (Somewhere in the range 12-18pF will be okay in practice.) Some manufacturers call this load capacitance "circuit condition". (This should not be confused with static or shunt capacitance, which is different.) The crystal should be a "fundamental" oscillation type and not a "harmonic" type. It should also be capable of accepting a 500μW drive level from our chip.

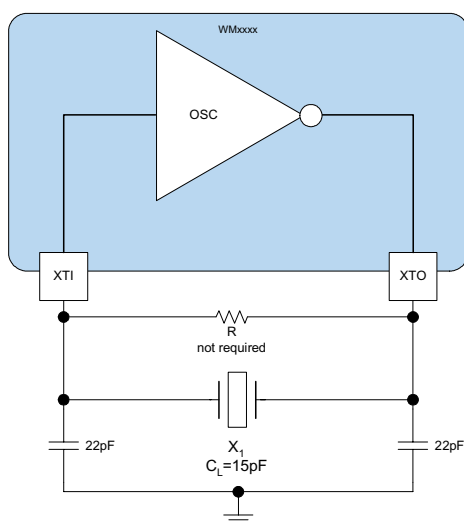


Figure 3 Recommended Values

Please also note some manufacturers show a parallel resistor with their oscillator circuit. This is not required for Wolfson chips.

CRYSTAL PARAMETER	RECOMMENDED VALUE
Oscillation mode	Fundamental (AT cut)
Load capacitance	15pF (12-18pF ok)
Drive level (max.)	500μW or higher

Table 1 Recommended Crystal Parameters

IMPORTANT NOTICE

Wolfson Microelectronics plc (WM) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current. All products are sold subject to the WM terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

WM warrants performance of its products to the specifications applicable at the time of sale in accordance with WM's standard warranty. Testing and other quality control techniques are utilised to the extent WM deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

In order to minimise risks associated with customer applications, adequate design and operating safeguards must be used by the customer to minimise inherent or procedural hazards. Wolfson products are not authorised for use as critical components in life support devices or systems without the express written approval of an officer of the company. Life support devices or systems are devices or systems that are intended for surgical implant into the body, or support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided, can be reasonably expected to result in a significant injury to the user. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

WM assumes no liability for applications assistance or customer product design. WM does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of WM covering or relating to any combination, machine, or process in which such products or services might be or are used. WM's publication of information regarding any third party's products or services does not constitute WM's approval, license, warranty or endorsement thereof.

Reproduction of information from the WM web site or datasheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations and notices. Representation or reproduction of this information with alteration voids all warranties provided for an associated WM product or service, is an unfair and deceptive business practice, and WM is not responsible nor liable for any such use.

Resale of WM's products or services with statements different from or beyond the parameters stated by WM for that product or service voids all express and any implied warranties for the associated WM product or service, is an unfair and deceptive business practice, and WM is not responsible nor liable for any such use.

ADDRESS:

Wolfson Microelectronics plc
Westfield House
26 Westfield Road
Edinburgh
EH11 2QB
United Kingdom

Tel :: +44 (0)131 272 7000

Fax :: +44 (0)131 272 7001

Email :: sales@wolfsonmicro.com