

CIRCLE **522 QUALITY PREAMP** **CUTS COST, SIZE**

WALT JUNG and RICHARD MARKELL

Linear Technology Corp., 1630 McCarthy Blvd.,
Milpitas, CA 95035; (408) 432-1900.

To achieve low noise and 600- Ω (or less) load capability, traditional recording-studio mixing panels use high-cost modular or hybrid amplifiers with matched input-stage transistors and push-pull A-B outputs. Though the expected high performance is achieved, the solution is large and expensive. An alternative approach uses a low-input-noise audio op amp added to a high-quality class-A buff-

er amp. The resulting circuit forms a variable-gain, transformer-coupled microphone preamp. The preamp is equal to the discrete design in performance, and superior in cost, size, and overall complexity.

IC U_1 is a low-noise LT1115 audio op amp that's operated in a class-A mode by J_1 , a 2-mA current source (*Fig. 1*). U_1 's output is buffered by U_2 , an LT1010 buffer amp. U_2 can be adjusted to supply a class-A stand-

ing current by the 49.9- Ω resistor at the Boost pin, and is capable of very low open-loop distortion.¹ U_3 , an LT1097 precision op amp, is configured as a dc servo to null output offsets that can cause distortion in the output transformer, T_2 . T_1 is carefully selected to match R_n , the LT1115's characteristic noise resistance.² Both transformers should be properly shielded and grounded for optimum performance in this low-level application.


Using the gain control, the circuit's overall gain can be adjusted from 12 to 50 dB. The distortion and frequency-response, plotted at an operating gain of 20 dB, illustrate the circuit's performance (Fig. 2). The risetime of the preamp approximates the Bessel response characteristic, now favored by specialists in the audio field. For top performance, the circuit should be operated with well-bypassed, low source-impedance power supplies. □

¹Jung, W.G., R.N. Markell, "Low


Distortion Video Buffer," *ELECTRONIC DESIGN*, March 9, 1989.

²Jung, W.G., *Audio IC Op-Amp*

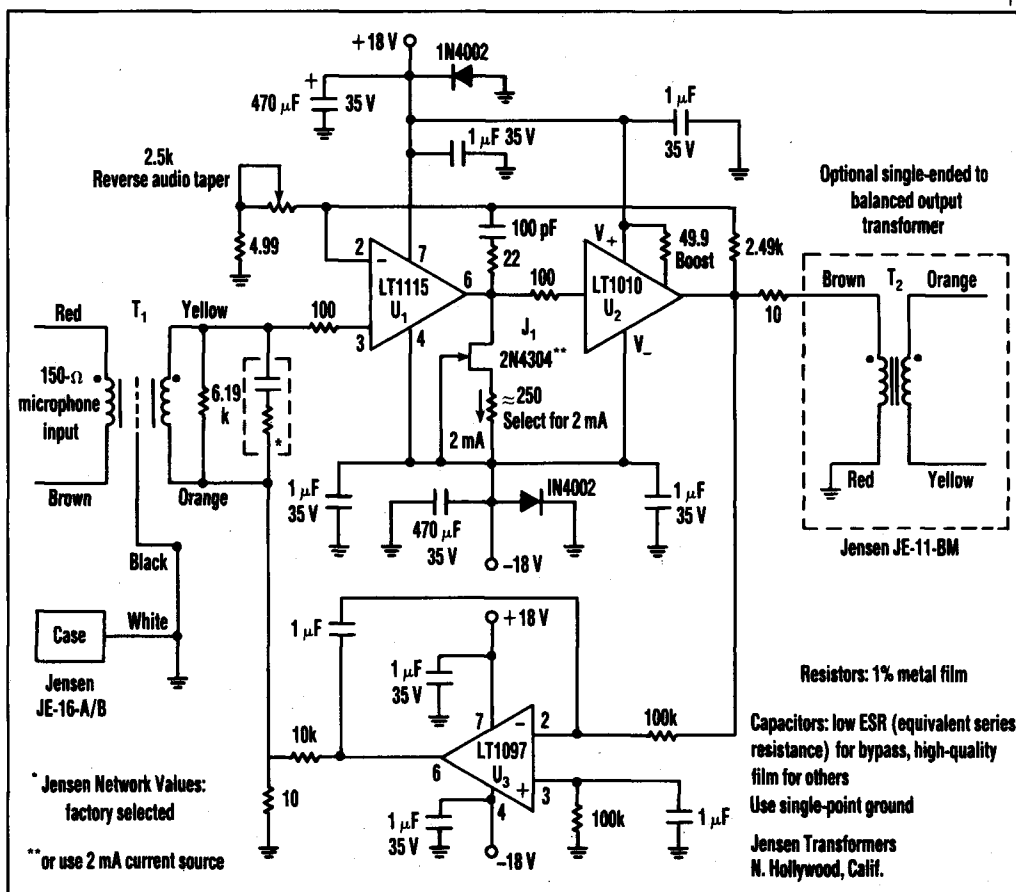Applications, Third Edition, Howard W. Sams and Co., Indianapolis, Ind., 1987.




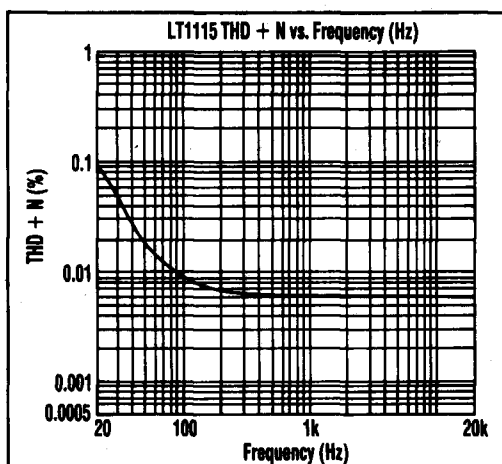1. A LOW-INPUT NOISE AUDIO OP AMP (LT1115) is coupled with a class-A buffer amp (LT1010) to form a variable-gain, transformer-coupled microphone preamp. By altering the gain control, the circuit's overall gain can be adjusted from 12 to 50 dB.



(a)

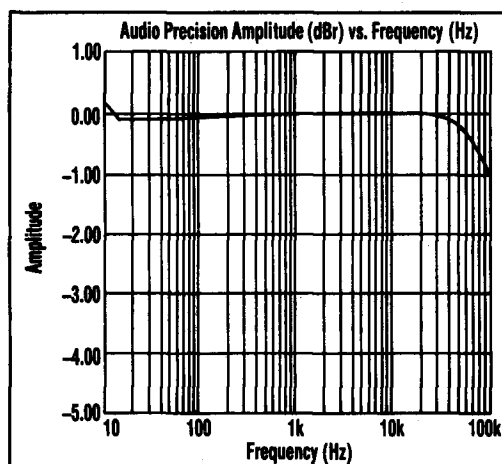$V_s = \pm 18 \text{ V}$
 $V_{in} = 0.95 \text{ V rms}$
 $R_L = 600 \Omega$
 $R_s = 150 \Omega$
 $T_A = 25^\circ \text{C}$



(b)

2. THE CIRCUIT'S TOTAL HARMONIC DISTORTION (THD) plus noise is plotted against frequency (a). A second plot shows the circuit's frequency response (b). Both plots illustrate an operating gain of 20 dB with a balanced input-output.